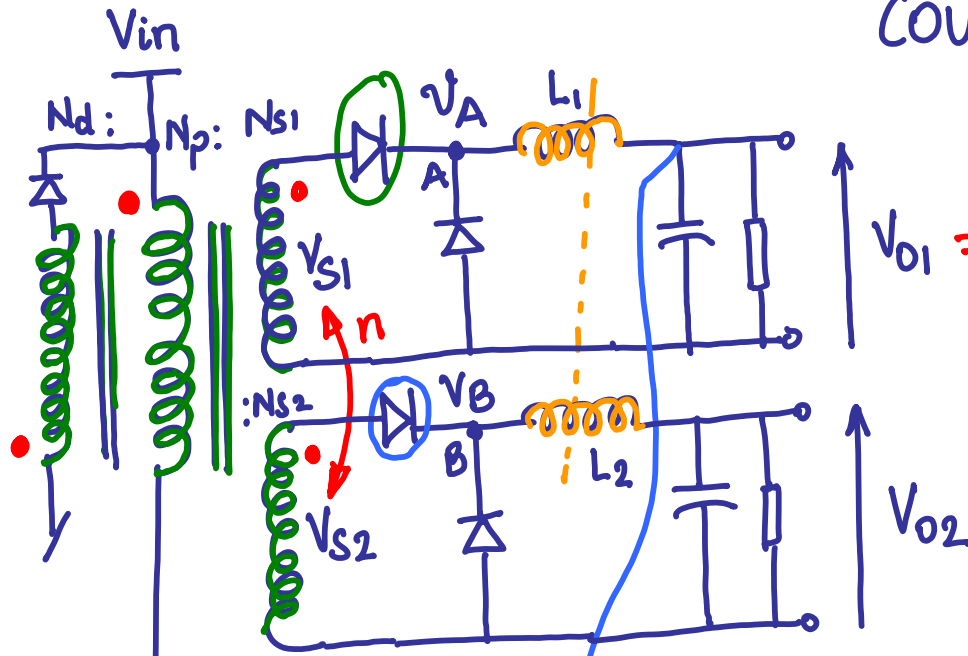


- Coupled Inductor
- Magnetic Amplifier method.

# COUPLED INDUCTOR METHOD



$$V_{o1} = V_A - V_{L1}$$

$$\frac{V_{s2}}{V_{s1}} = n = \frac{N_{s2}}{N_{s1}}$$

$$n = \frac{N_{L2}}{N_{L1}}$$


$$V_{o2} = V_B - V_{L2}$$

$$V_B = n V_A$$

$$V_{L2} = n V_{L1}$$



$$V_{o2} = n V_A - n V_{L1} = n (V_A - V_{L1})$$

$$\underline{V_{o2} = n V_{o1}}$$

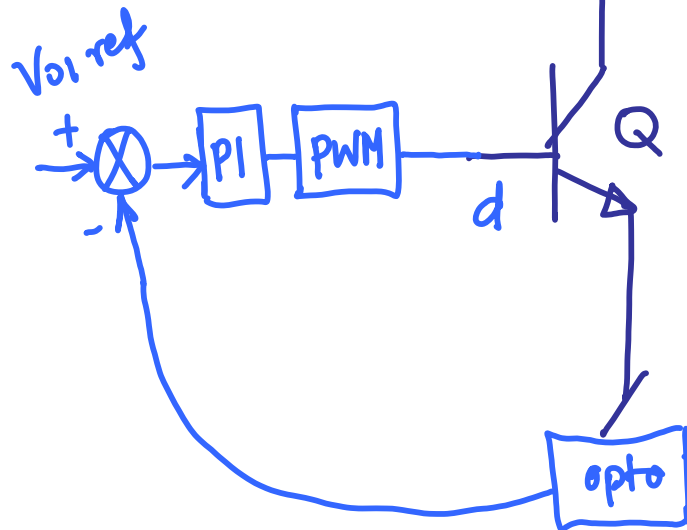

$$V_{02} = V_B - V_{L2}$$
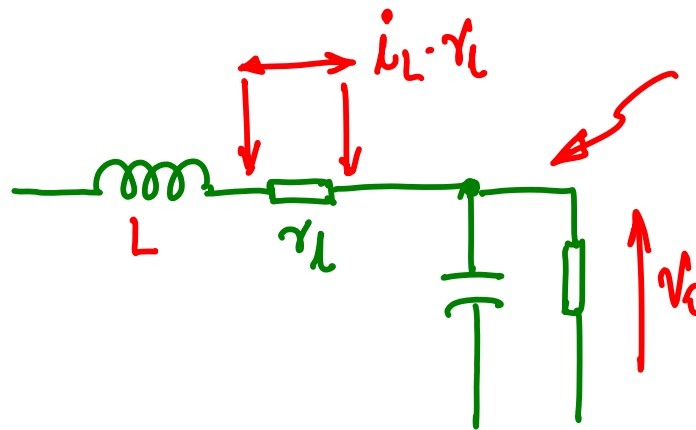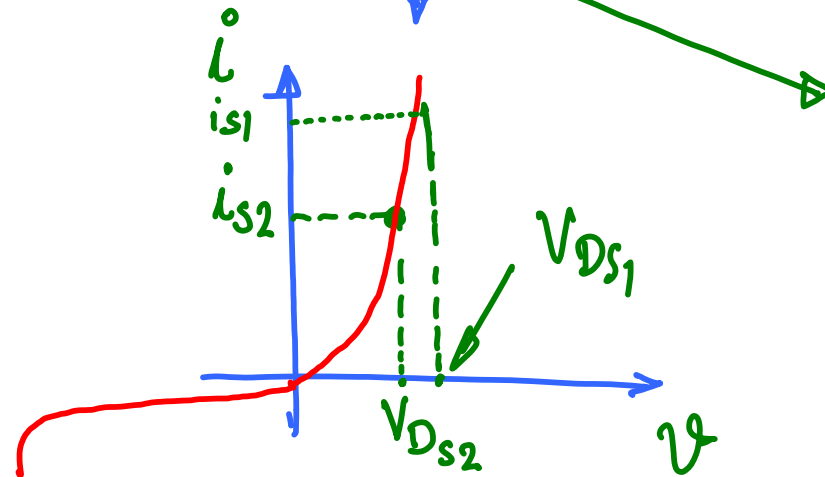
$$= V_{S2} - \textcircled{V_D} - V_{L2}$$




$$V_{01} = V_A - V_{L1}$$



$$= V_{S1} - \textcircled{V_{DS1}} - V_{L1}$$

$$(V_S - \textcircled{V_D}) - V_L - \textcircled{i_L r_L} = V_o$$

# Magnetic Amplifier method

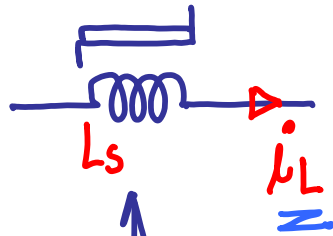

Saturable inductor

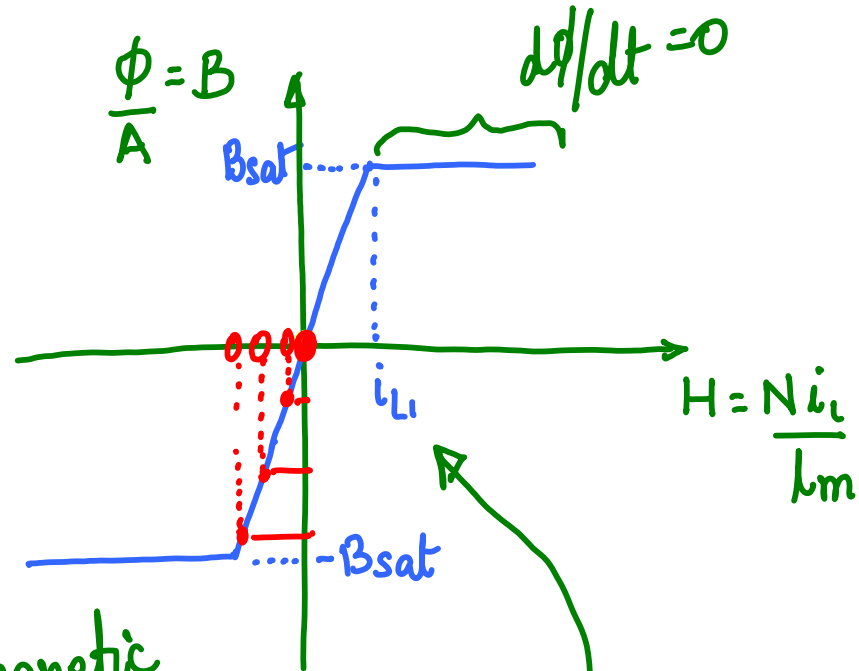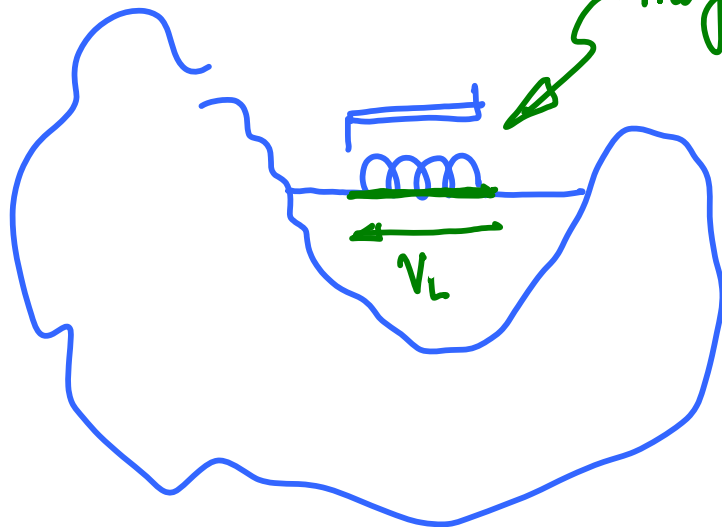

$$\frac{V_L}{L} = \left( \frac{di_L}{dt} \right) = \frac{d\phi}{dt}$$

$$i_L = \frac{1}{L} \int V_L dt$$

$$V_L = N \frac{d\phi}{dt} = 0$$

