

$$C: \quad c \frac{dv_c}{dt} = i_L - \frac{v_c}{R_2}$$

$$\begin{aligned} \frac{di_L}{dt} &= -\left(\frac{R_1}{L}\right)i_L - \left(\frac{1}{L}\right)v_c + \left(\frac{1}{L}\right)v_g \\ \frac{dv_c}{dt} &= \left(\frac{1}{C}\right)i_L - \left(\frac{1}{R_2 C}\right)v_c + 0 \cdot v_g \end{aligned}$$

$$\frac{di_L}{dt} = -\left(\frac{R_1}{L}\right) i_L - \left(\frac{1}{L}\right) v_c + \left(\frac{1}{L}\right) v_g$$

$$\frac{dv_c}{dt} = \left(\frac{1}{C}\right) i_L - \left(\frac{1}{R_2 C}\right) v_c + \underline{0} v_g$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \underbrace{\begin{bmatrix} -\frac{R_1}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_2 C} \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_L \\ v_c \end{bmatrix}}_x + \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}}_B \underbrace{[v_g]}_u$$

STATE EQUATION


$$y = C \cdot x + D \cdot u$$

$$\parallel \quad v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} [v_g]$$

OUTPUT EQUATION




$$\begin{array}{ll} \dot{x} = Ax + Bu & \text{state equation} \\ y = Cx + Du & \text{output equation} \end{array}$$


# BUCK DC-DC CONVERTER

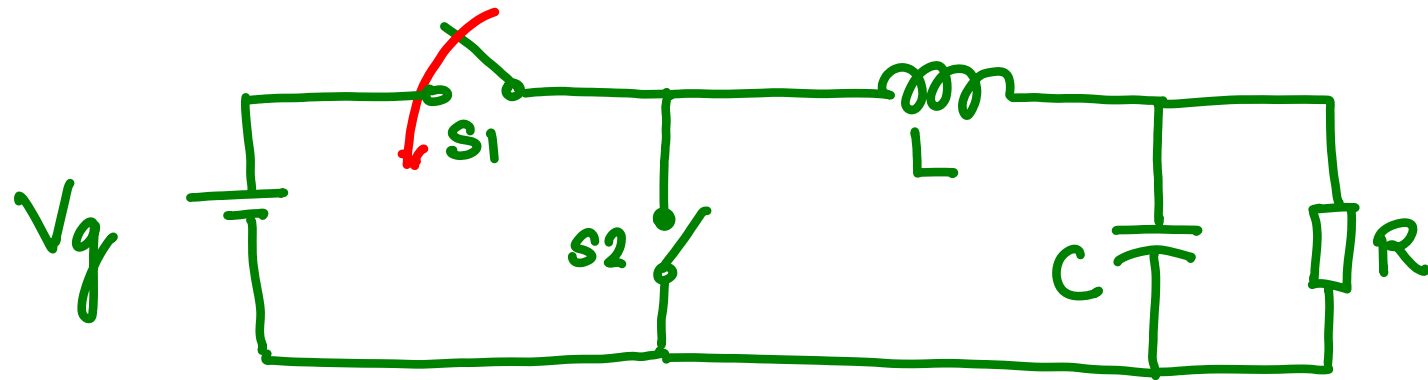

$DT$   
 $S_1$  - ON  
 $S_2$  - OFF

$(1-D)T$   
 $S_1$  - OFF  
 $S_2$  - ON

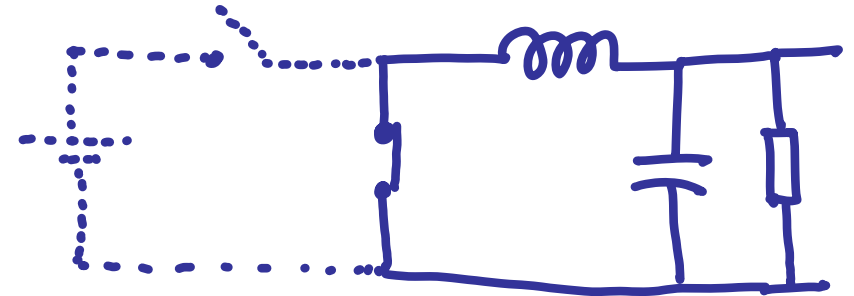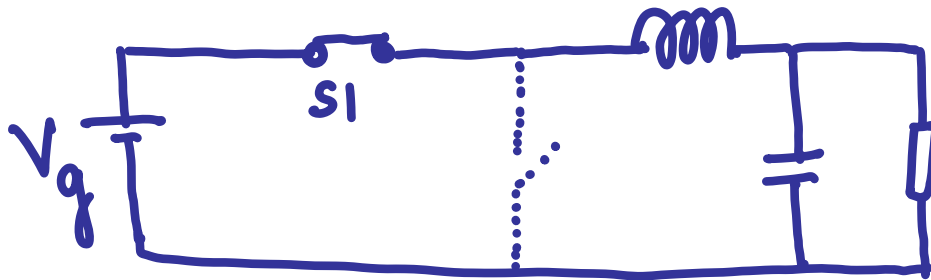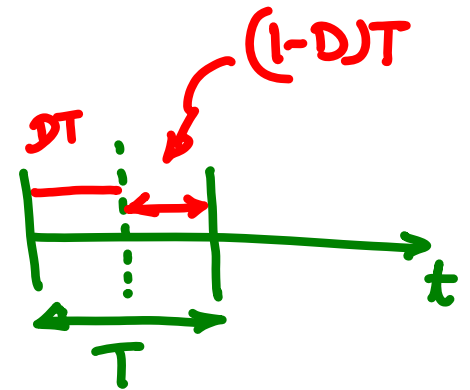

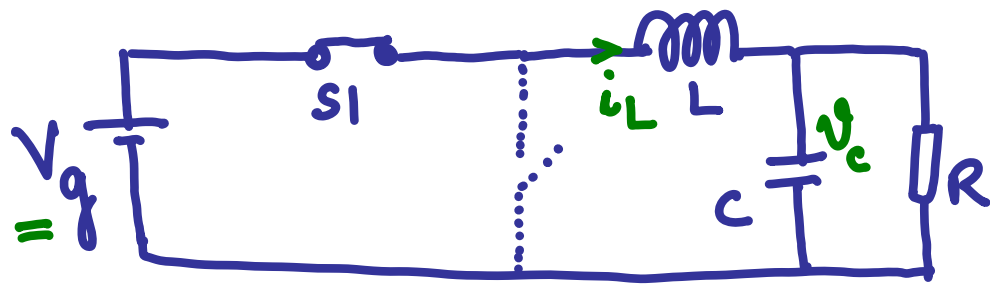


MODE - DT

$$L \frac{di_L}{dt} = V_g - V_c$$

$$C \frac{dV_c}{dt} = i_L - \frac{V_c}{R}$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{V}_c \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ V_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [V_g]$$

$$\dot{x} = A_1 x + B_1 u$$

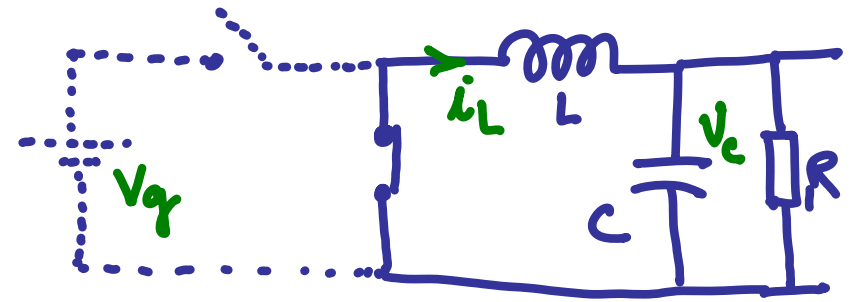

MODE - (1-D)T

$$L \frac{di_L}{dt} = 0 - V_c$$

$$C \frac{dV_c}{dt} = i_L - \frac{V_c}{R}$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{V}_c \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ V_c \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} [V_g]$$

$$\dot{x} = A_2 x + B_2 u$$

$$y = C_1 x + D_1 u$$

$$V_o = [0 \ 1] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$


$$y = C_2 x + D_2 u$$

$$V_o = [0 \ 1] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$\dot{x} = A_1 x + B_1 u$$

$$y = C_1 x + D_1 u$$

Large Signal Model  
during DT

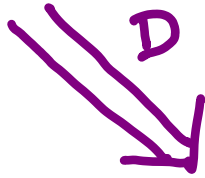


$$\dot{x} = A_2 x + B_2 u$$

$$y = C_2 x + D_2 u$$

Large Signal Model  
during  $(1-D)T$



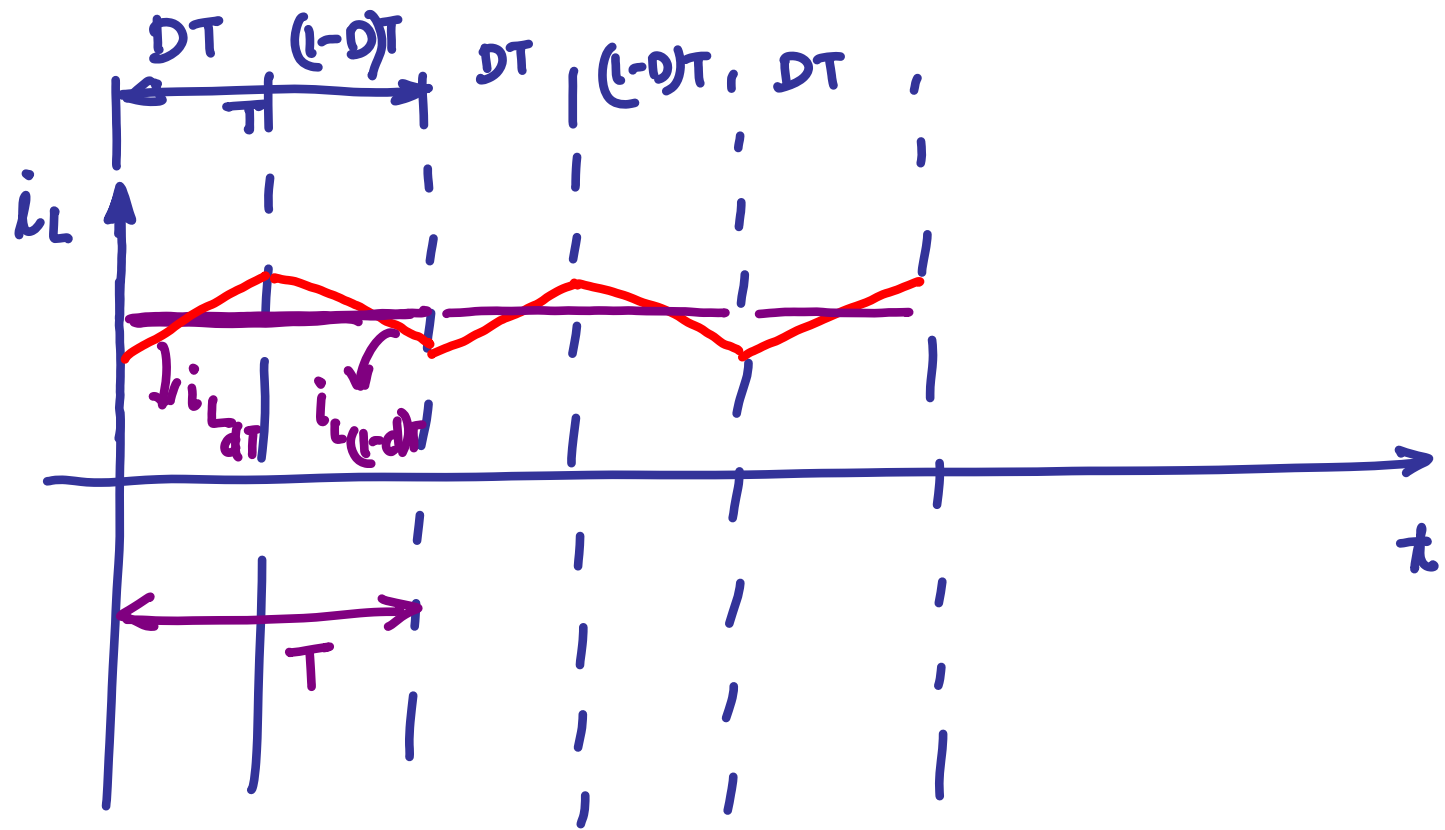
$$x_{avg} = \frac{x_{dT} \cdot D + x_{(1-d)T} (1-D)}{1}$$


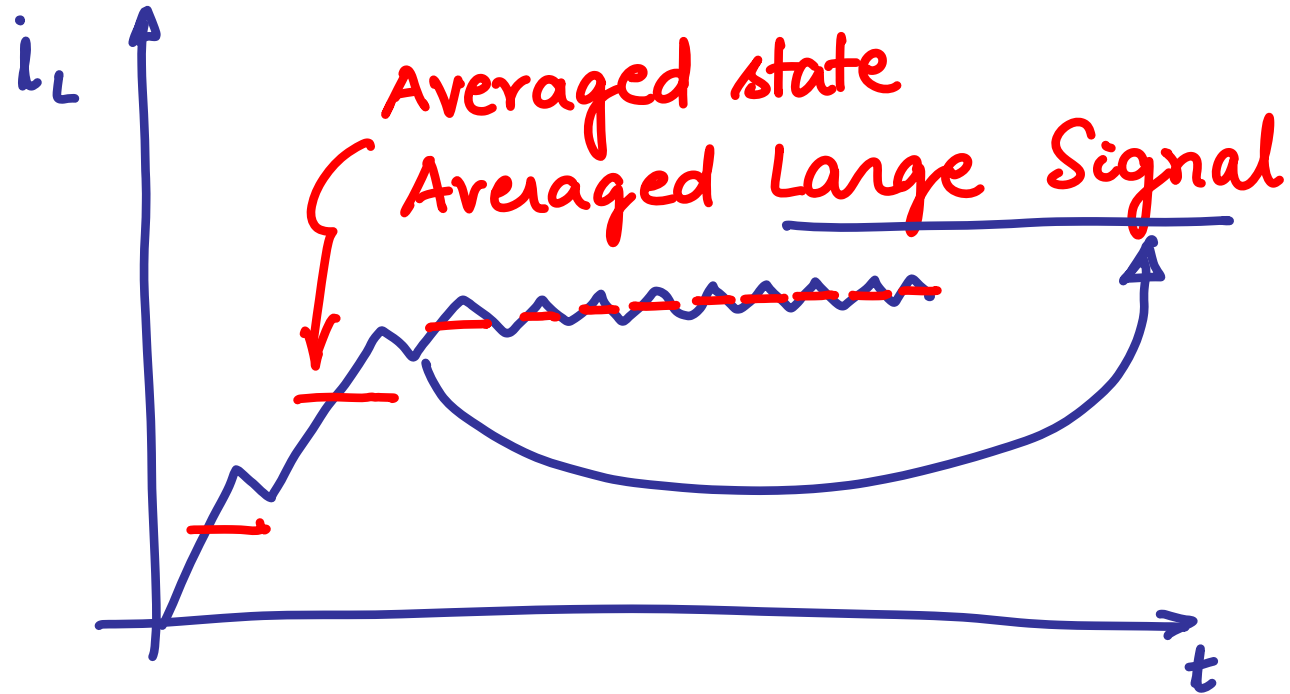
$$\underline{\underline{i_{L_{avg}}} = \frac{i_{L_{dT}} \cdot D + i_{L_{(1-d)T}} \cdot (1-D)}{1}}$$







$$x_{avg} = x_d \cdot d + x_{(1-d)}(1-d)$$

$$\dot{x} = A_1 x + B_1 u$$

&

$$\dot{x} = A_2 x + B_2 u$$

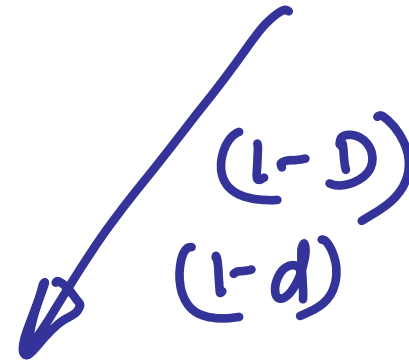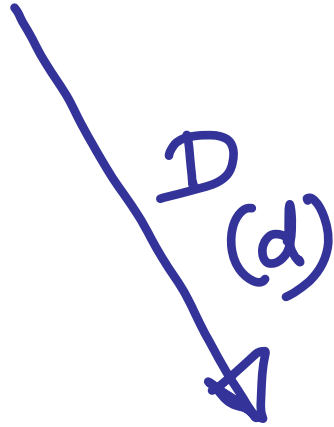

$$\dot{x} = A x + B u$$

Averaged Large Signal Model