

(\mathcal{L}) inductor Design

STEP 1: Obtain the value ' L ' of the inductor

$$v_L = \underline{L} \frac{di_L}{dt}$$

Step 2: $\underline{A_p} = \underline{A_c A_w} = \frac{2 \mathcal{E}}{K_w \cdot K_c \cdot J \cdot B_m}$

\mathcal{E} : energy , Joules

K_w : window factor , 0.6
like flyback transformer
0.3 - 0.4


$K_c \approx 1$

$J = 3 \times 10^6 \text{ A/m}^2 \quad \{(2-5) \text{ A/mm}^2\}$

$B_m = 0.25 \text{ T}$

$A_{c \text{ select}}$





$A_{w \text{ select}}$

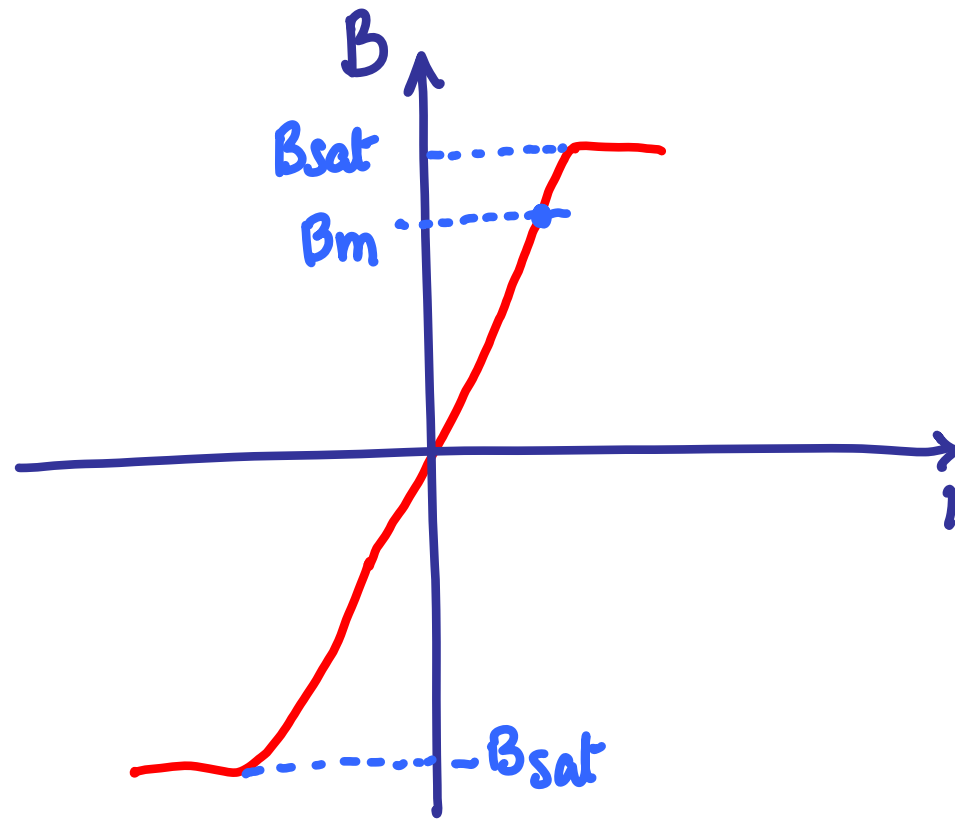

	B_{sat}	B_m
Ferrite -	0.3T	0.25T
CR60 -	1.2 to 1.4T	1.1T
CRN60 -	1.1 - 1.2 T	1T
Powdered Iron -	1.5T	1.3T
Amorphous Glass -	1.6T	1.4T

Step 3: Permeance, Λ

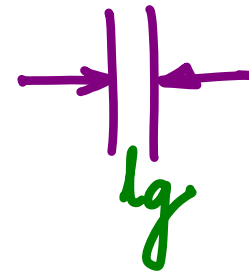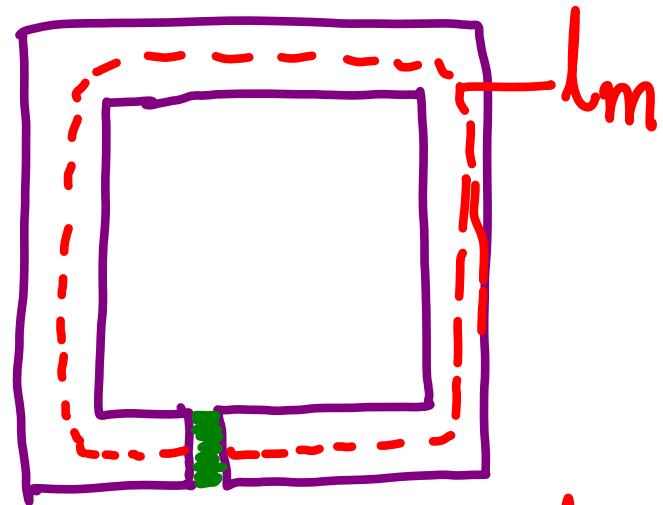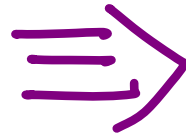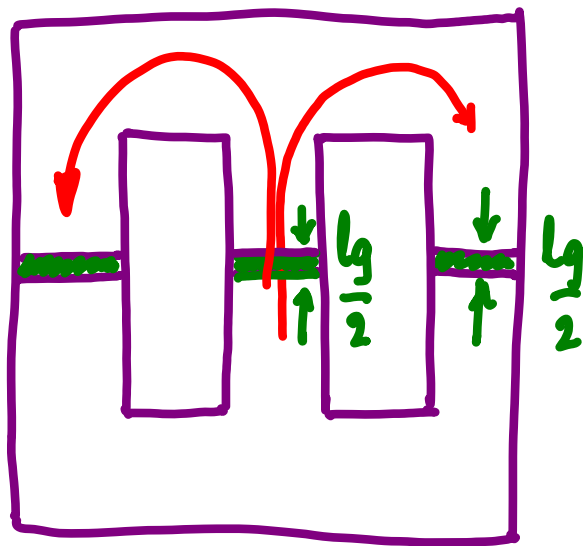$\rightarrow A_L$ factor $\Rightarrow nH/\text{turn}^2$



$l_m + l_g$

$$R = \frac{l_m}{\mu_0 \mu_r A_c} + \frac{l_g}{\mu_0 A_c} = \frac{1}{\mu_0 A_c} \left\{ \frac{l_m}{\mu_r} + l_g \right\}$$

$$\Lambda = \frac{1}{R} = \frac{\mu_0 A_c}{\left\{ \frac{l_m}{\mu_r} + l_g \right\}}$$

$\frac{l_m}{\mu_r} \ll l_g$

$$\Lambda \approx \frac{\mu_0 A_c}{l_g}$$


Step 4: Number of turns

$$\Lambda = \frac{L}{N^2}$$

$$N = \sqrt{\frac{L}{\Lambda}} = \sqrt{\frac{L}{A_L}}$$

Step 5: Gauge of the Wire
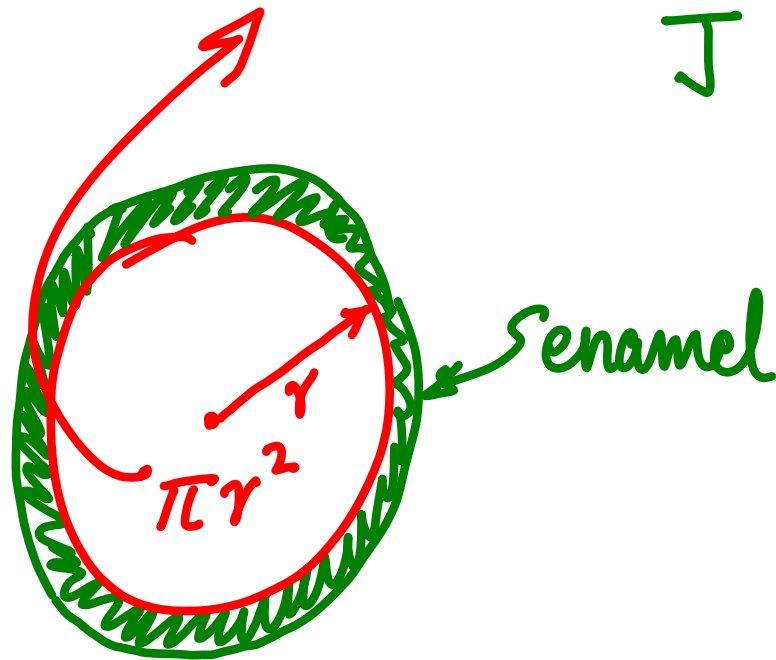
$$A_{\text{wire}} = \frac{I_{\text{rms}}}{J}, \text{ m}^2$$




$A_{\text{wire}_{\text{select}}}$

Step 6: Window area cross check

$$K_w A_w > a_{\text{wire}_{\text{select}}} \cdot N$$

Design of Transformer

μ : permeability & Δ are HIGH

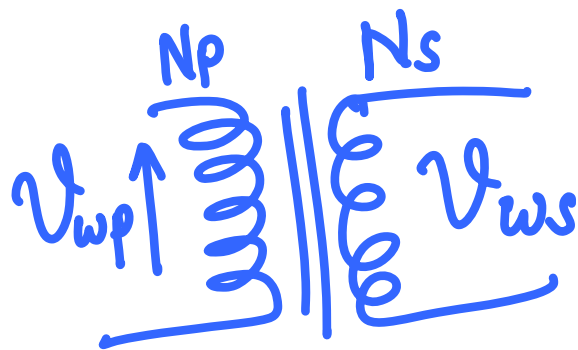


$$A_p = A_c \cdot A_w =$$

$$\underline{V_{wp}} = N_p \frac{d\phi}{dt} = N_p \cdot A_c \cdot \frac{dB}{dt} \begin{matrix} f(V_{rms}) \\ f(P_o) \end{matrix}$$

$$= N_p \underline{A_c} \frac{\Delta B}{\Delta T}$$

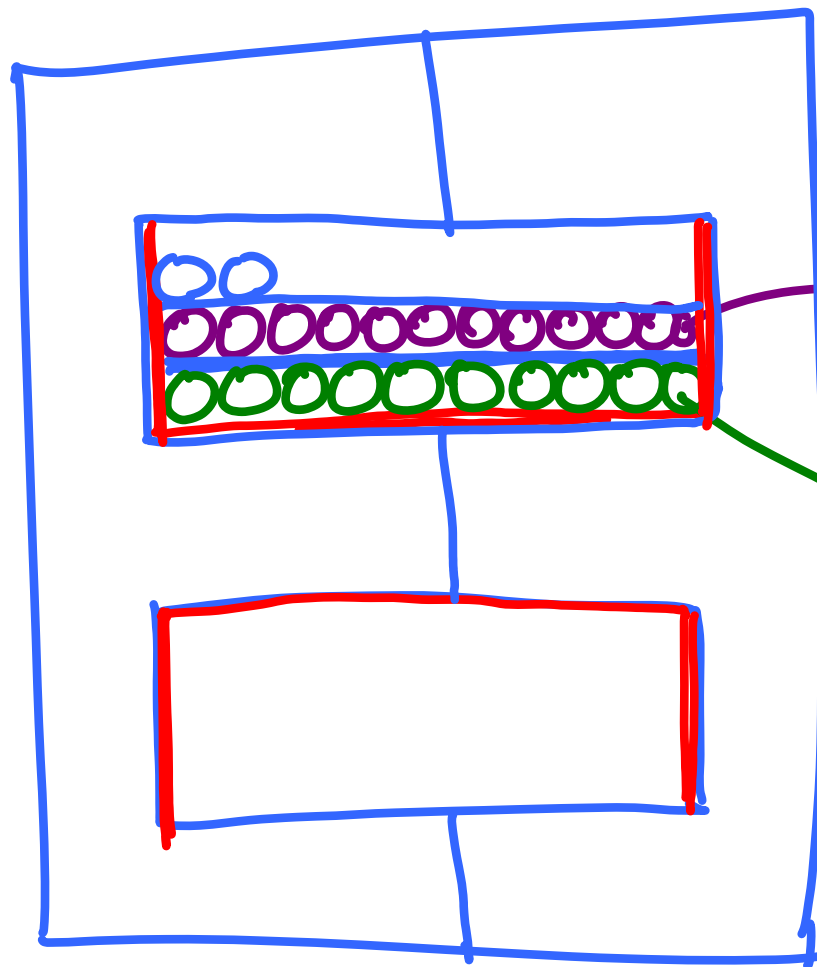
$$K_w \underline{A_w} > \underbrace{A_{wirep} \cdot N_p}_{\substack{I_{rms} \\ J}} + \underbrace{A_{wires} \cdot N_s}_{\substack{I_{rms} \\ J}}$$



N_s number of winding wires

N_p, A_{wirep}

FULL BRIDGE FORWARD CONVERTER.

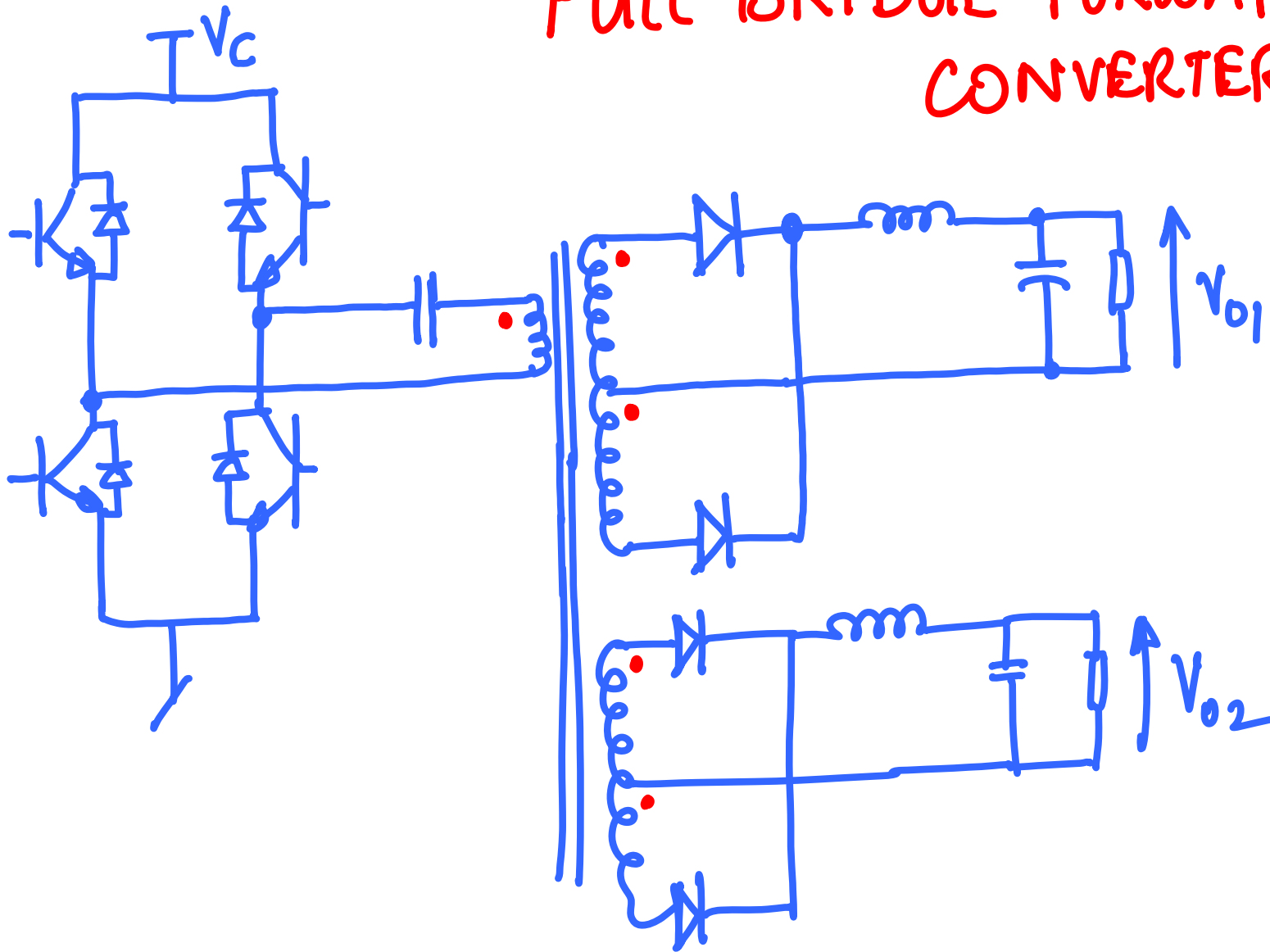

Step 1: Specifications (USER)

$V_c = 325 \text{ V dc}$; # nominal dc link voltage

$V_{cmin} = 200 \text{ V dc}$;

$V_{cmax} = 380 \text{ V dc}$;

$V_o = [15\text{V}, 5\text{V}]$; vector

$I_o = [0.5\text{A}, 1\text{A}]$;

Step 2: Specs (DESIGNER)

$$\Delta i_L = \underline{\underline{10\% \text{ of } I_o}}$$


$$\left(\frac{2L}{R_D T_s} \right) \Rightarrow \text{conduction.}$$

$$f_s = \underline{\underline{20 \text{ kHz}}}$$

$$B_m = 0.2 \text{ T}$$

$$B_{mL} = 0.25 \text{ T}$$

$$\eta = 0.8 \text{ (80\%)}$$

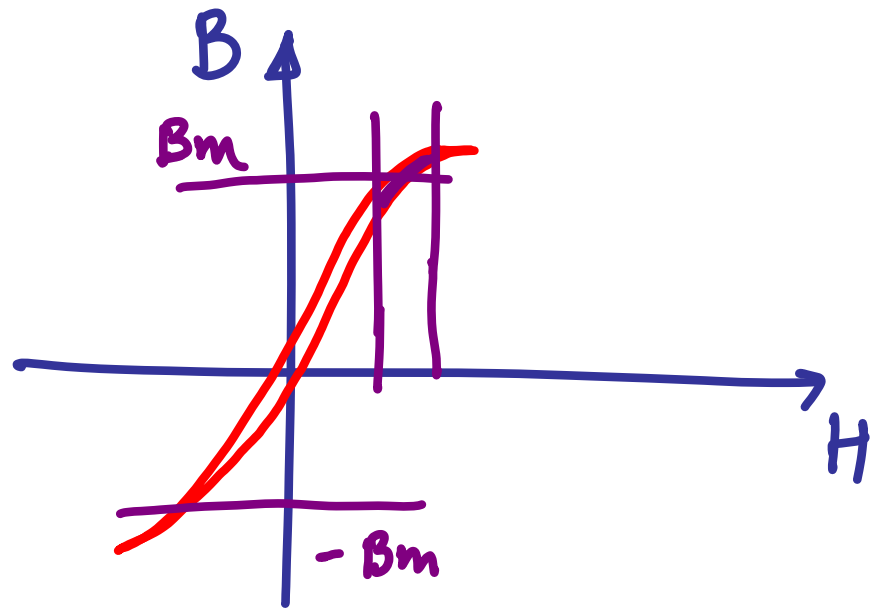

$$P_{\max} = 0.45$$

$$J = 3 \times 10^6 \text{ A/m}^2$$

$$K_w = 0.4$$

$$K_{wL} = 0.6$$

$$V_d = 0.7 \text{ to } 1 \text{ V}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

Step 3: Power calculations

$$P_s = \sum_{\text{all sec}} 1 \cdot 1 (V_o + V_d) \cdot I_o$$

secondary power
just at the Xfm sec.

Step 4: Turns ratio

$$n = \frac{1 \cdot 1 (V_o + V_d)}{2 \cdot D_{\max} (V_{c\min} - 0.1 V_{c\max})}$$

$$D_{\min} = (D_{\max} \cdot V_{c\min}) / V_{c\max}$$

Step. 5: Transformer

$$A_p = f(P_o)$$

$$A_{cselect}, A_{wselect}$$

$$N_p = \frac{V_{cmax}}{4 B_m \cdot A_{cselect} \cdot f_s}$$

$$N_s = n \cdot N_p$$

$$A_{wirep} = \frac{nI_0}{J}$$

$$A_{wires} = \frac{I_0 \sqrt{D_{max}}}{J}$$

$$A_{wirp_{select}}, \quad A_{wires_{select}}$$

$$K_w A_w > \sum a_w \cdot N$$

Step 6 : Inductor

- L
- $A_p = f(\varepsilon)$
- \wedge
- N
- A_{wire}
- $\forall w A_w > A_{wire_select} \cdot N$

Step: 7 Flux walking capacitance

$$C_w = \frac{n I_o \cdot D_{max}}{0.1 V_{cmax} \cdot f_s}$$

↓
Σ of all sec reflected currents.


Step: 8 Filter capacitor at output

$$C = \frac{\Delta i_L}{\Delta V_C \cdot 8 \cdot f_s}$$

ΔV_C

ripple that needs to be allowed

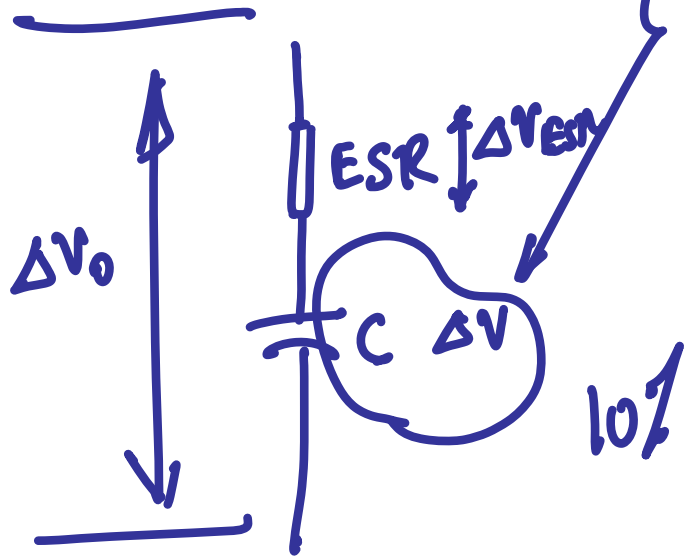
$$ESR < 0.8 \frac{\Delta V_o}{\Delta i_L^p}$$



Step. 9: DIODE

$$\underline{PIV > 2n V_{Cmax}}$$
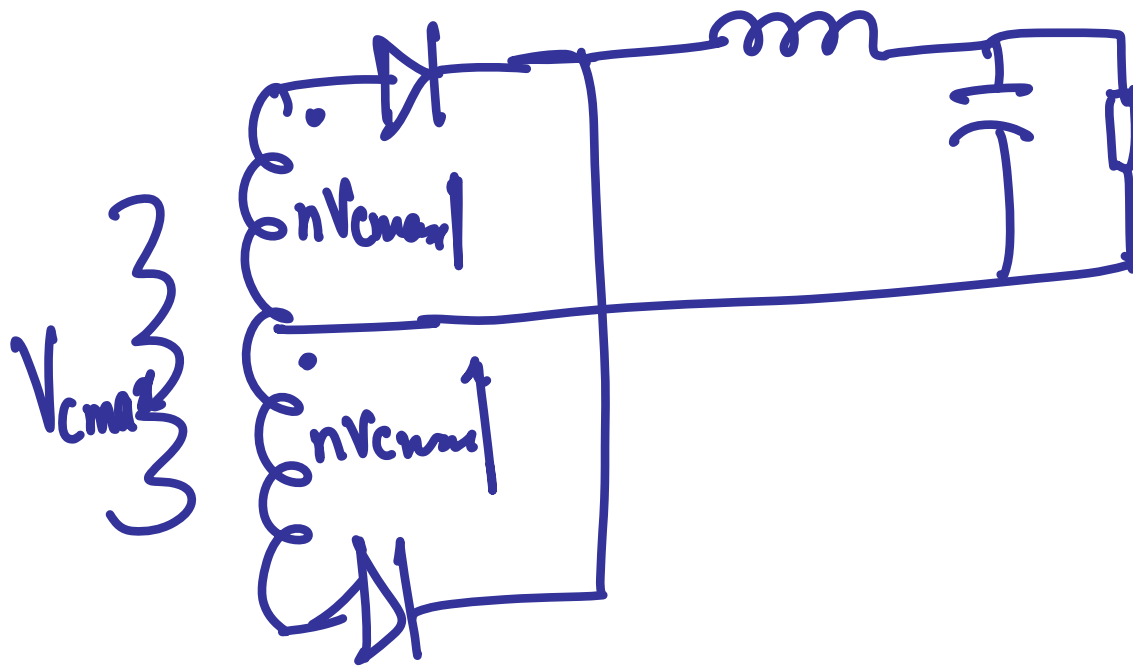
$$\underline{I_{dm} > \left(I_o + \frac{\Delta i_L}{2} \right)}$$



$$\underline{I_{dcr} > I_{dm} \times D_{max}}$$




Step 10: Switches


$$V_{CE0} > V_{Cmax}$$

$$I_{cm} \geq \underbrace{\sum n \left(I_0 + \frac{\sigma_{ii}}{2} \right)} + I_{mag}$$

↓
10% of I_0

FLYBACK CONVERTER

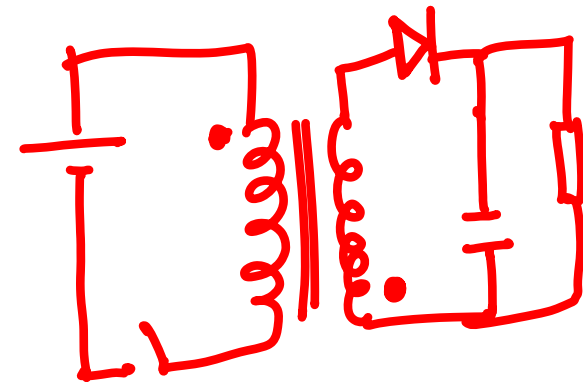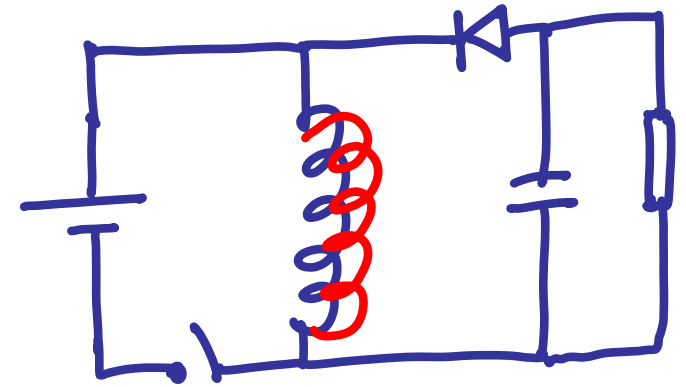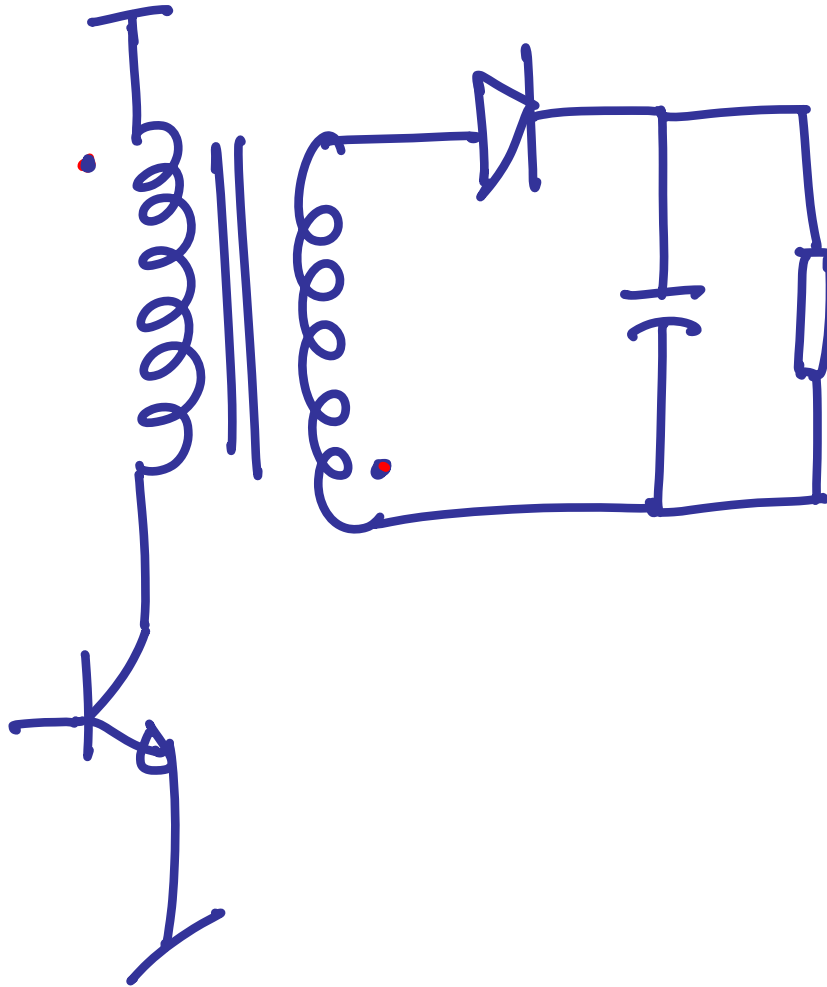

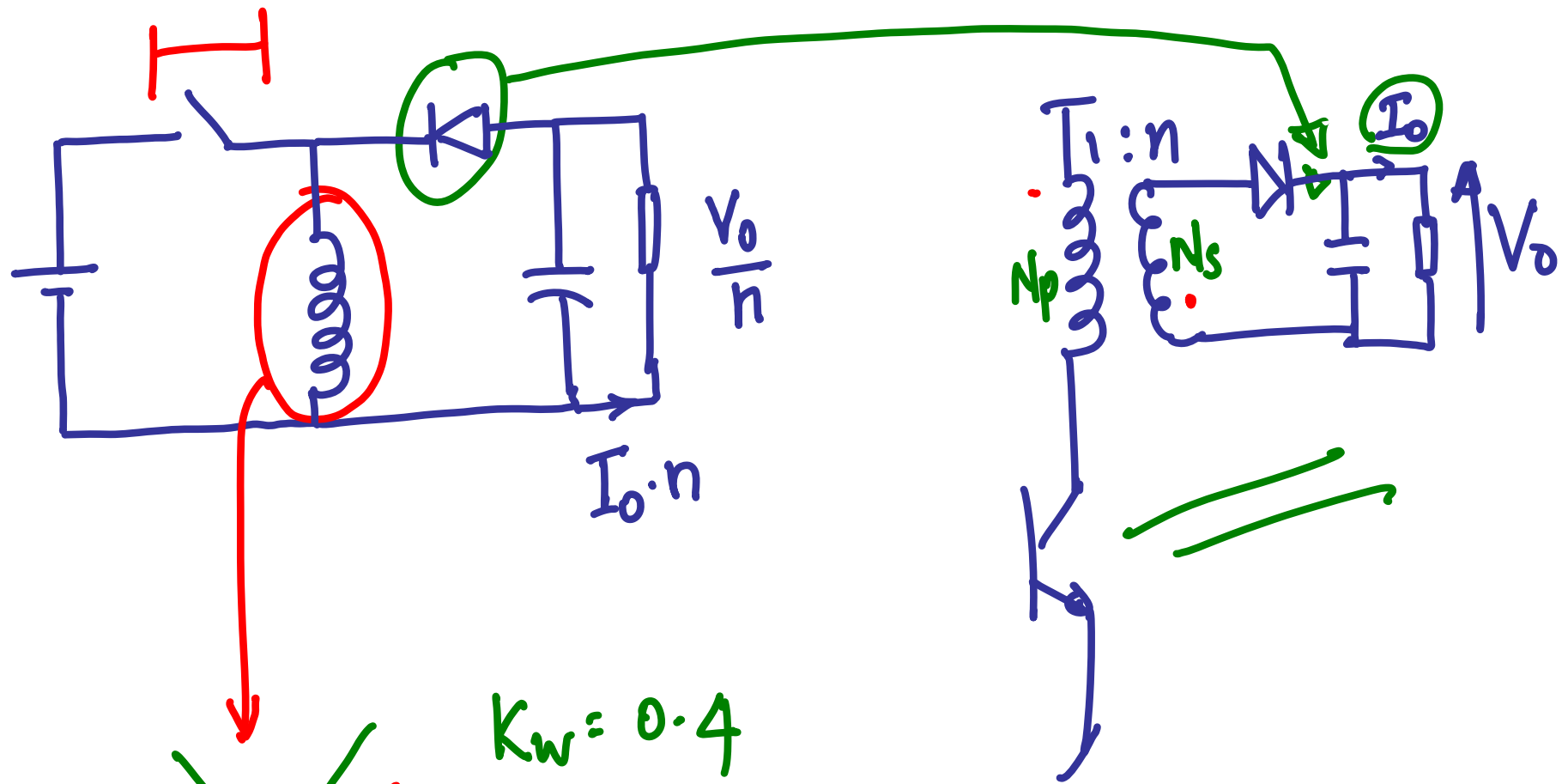

~~$K_w = 0.6$~~

$K_w = 0.4$
 $(= 0.3)$

$$K_w A_w > A_{wirep} \cdot N_p + A_{wires} \cdot N_s$$