

Switched Mode Power Conversion

Switches

Devices for Efficient Power Conversion

Switches

Inductors

Transformers

Capacitors

Switched Mode Power Conversion

Switches



Switch is a Bistable Circuit Element


OFF State

&

ON State

Switched Mode Power Conversion

Switches

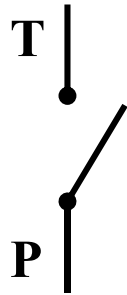


Simple Switch has Two Terminals

**Pole
&
Throw**

Switched Mode Power Conversion

Switches

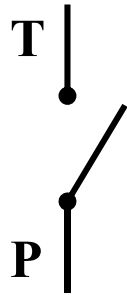

In the OFF State

Pole & Throw are Isolated from Each Other

Switched Mode Power Conversion

Switches




In the ON State

Pole & Throw are Connected to Each Other

Switched Mode Power Conversion

Switches

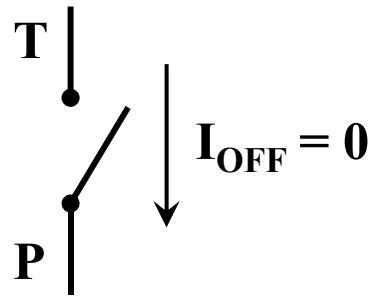


In the OFF State

Current through the Switch is Zero

Switched Mode Power Conversion

Switches

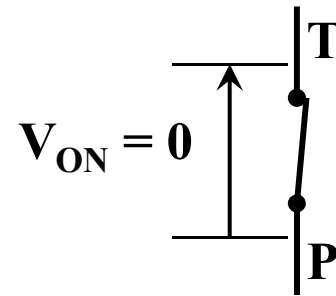


In the ON State

Voltage Across the Switch is Zero

Switched Mode Power Conversion

Switch – Primary Characteristics

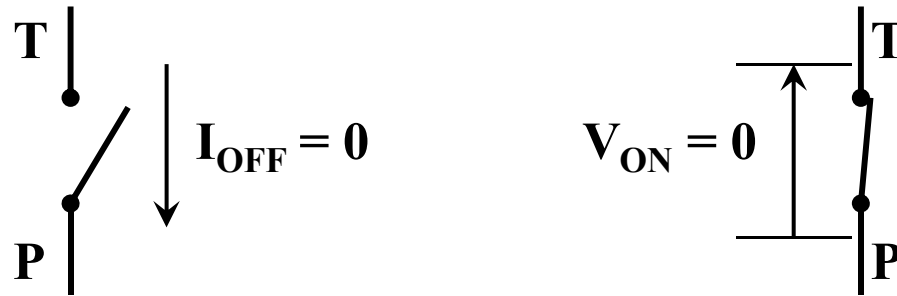


In the OFF State: $I_{\text{OFF}} = 0$

In the ON State: $V_{\text{ON}} = 0$

Switched Mode Power Conversion

Switch

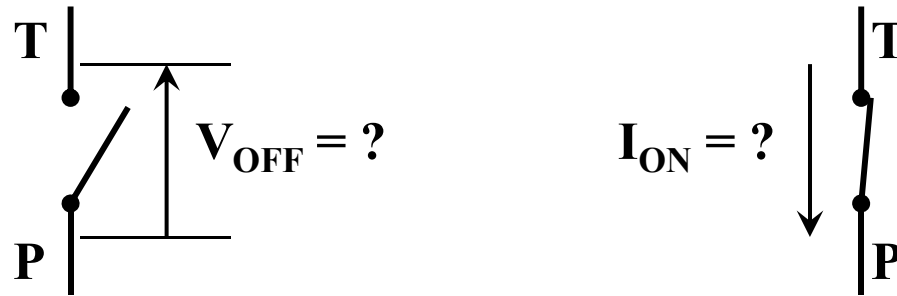


In the OFF State: $V_{\text{OFF}} = ?$

In the ON State: $I_{\text{ON}} = ?$

Switched Mode Power Conversion

Switch – OFF State

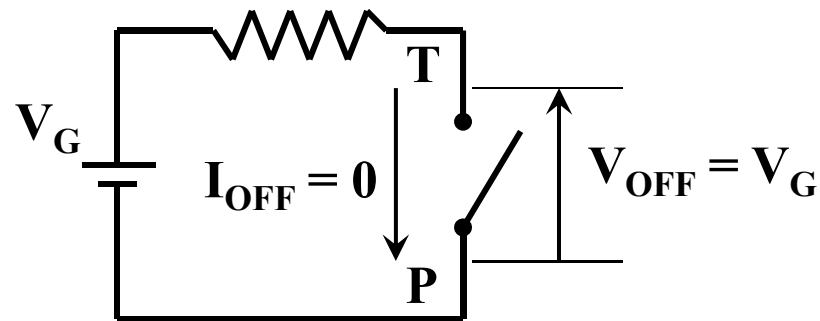


In the OFF State: $I_{OFF} = 0$

In the OFF State: $V_{OFF} = V_G$

Switched Mode Power Conversion

Switch – ON State

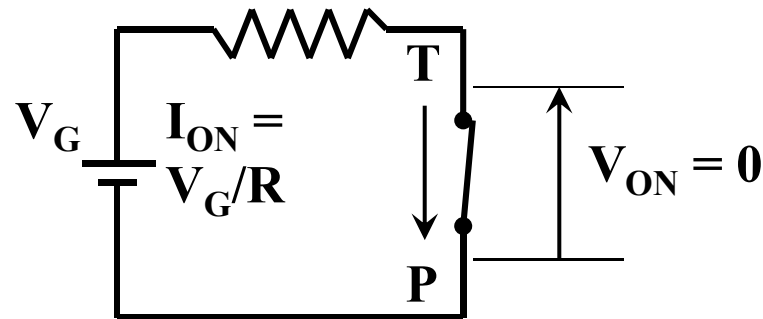


In the ON State: $V_{ON} = 0$

In the ON State: $I_{ON} = V_G/R$

Switched Mode Power Conversion

Switch – Ideal Performance

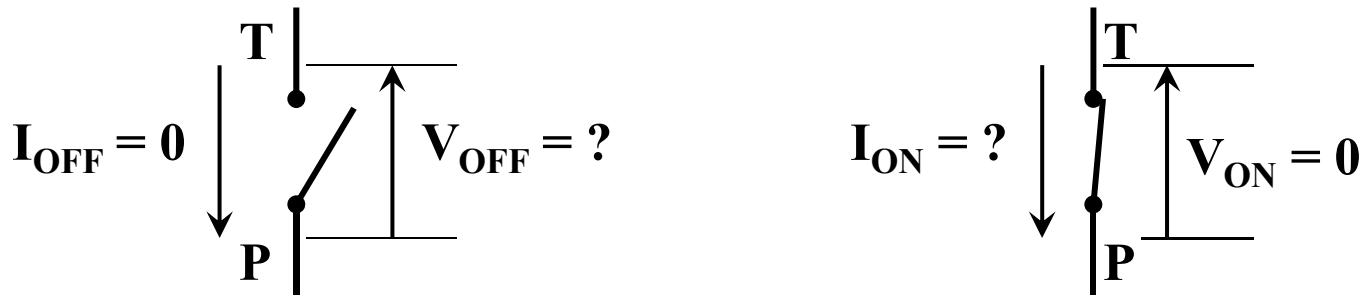

In the OFF State:




$I_{\text{OFF}} = 0$; V_{OFF} by External Circuit

In the ON State:

$V_{\text{ON}} = 0$; I_{ON} by External Circuit



Switched Mode Power Conversion

Ideal Switch – In the VI Plane

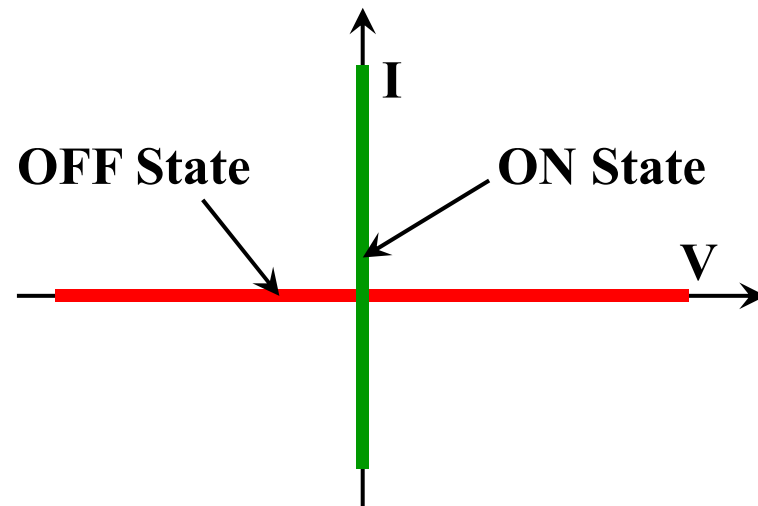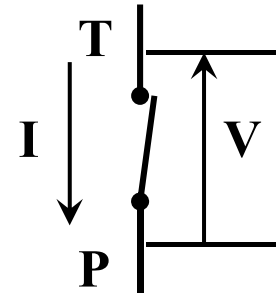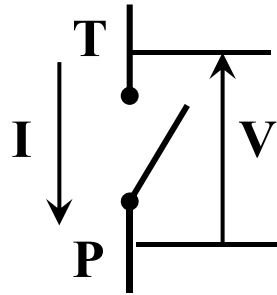

Switched Mode Power Conversion

Ideal Switch – Power Loss

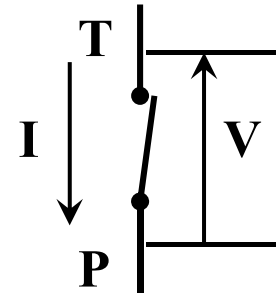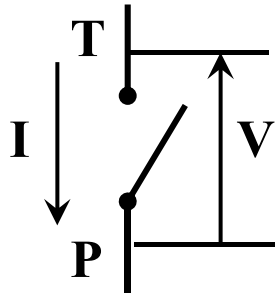



Power Loss in the Ideal Switch

$$\text{Conduction Loss} = V_{\text{ON}} * I_{\text{ON}} = 0$$

$$\text{Blocking Loss} = V_{\text{OFF}} * I_{\text{OFF}} = 0$$

Switched Mode Power Conversion

Ideal Switch – Switching Performance

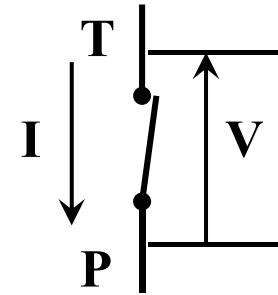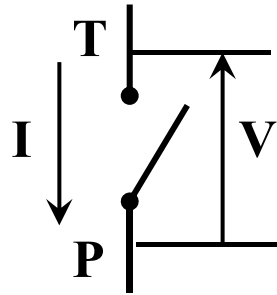

**How Does the Switch Perform
in
Switching?**



Time Taken to Switch!

Energy Needed to Switch!

Dependence on Environment!

Switched Mode Power Conversion

Ideal Switch – Switching Performance

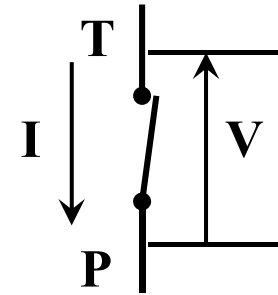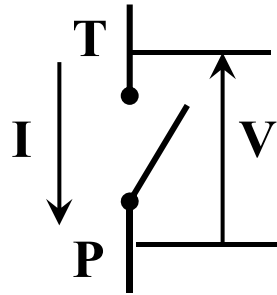



**How Does the Switch Perform
in
Switching?**

Energy Required to Remain On = $E_{ON} = 0$

Energy Required to Remain Off = $E_{OFF} = 0$

Switched Mode Power Conversion

Ideal Switch – Switching Performance

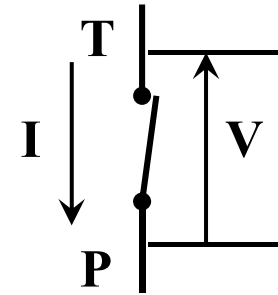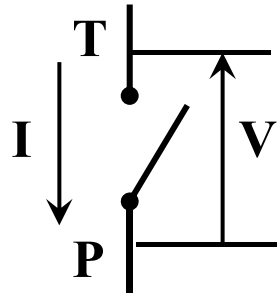



**How Does the Switch Perform
in
Switching?**

Time Taken to Turn On = $T_{\text{OFF/ON}} = 0$

Time Taken to Turn Off = $T_{\text{ON/OFF}} = 0$

Switched Mode Power Conversion

Ideal Switch – Switching Performance

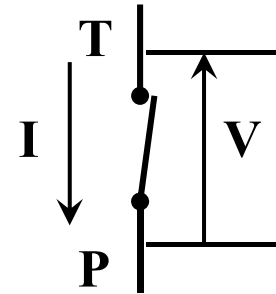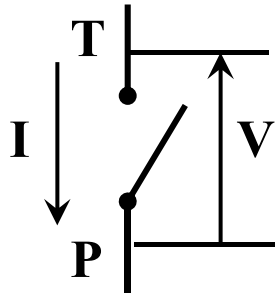



**How Does the Switch Perform
in
Switching?**

Energy Consumed to Turn On = $E_{\text{OFF/ON}} = 0$

Energy Consumed to Turn Off = $E_{\text{ON/OFF}} = 0$

Switched Mode Power Conversion


Ideal Switch – Dependence on Ambient

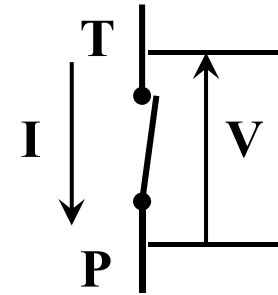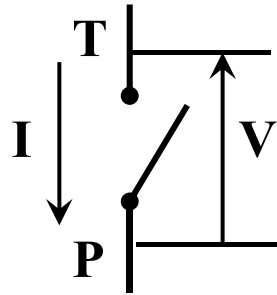

Switch Performance
is
Independent of Ambient Conditions

Switched Mode Power Conversion

Compound Switch

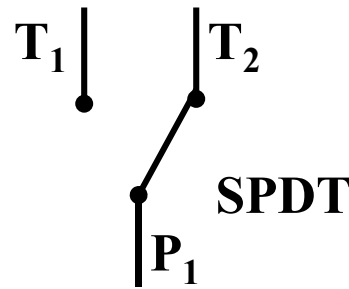


Example: Single Pole Double Throw Switch

Made-up of Two Single Pole Single Throw Switches

Multiple Pole Multiple Throw Switches are Common

Switched Mode Power Conversion

Real Switch

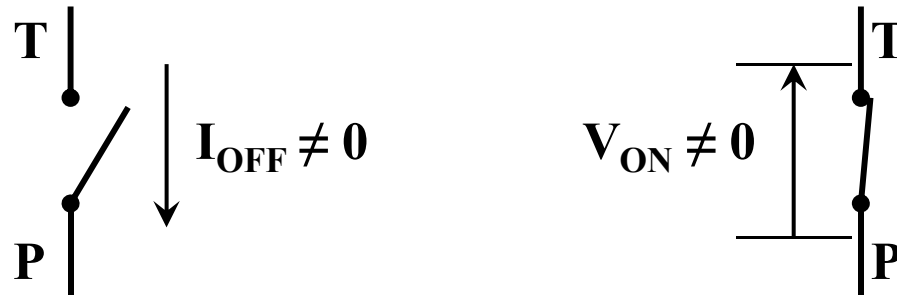

In the OFF State: $I_{OFF} \neq 0$

In the ON State: $V_{ON} \neq 0$

Switched Mode Power Conversion

Real Switch – Power Loss






Power Loss in the Real Switch

$$\text{Conduction Loss} = V_{\text{ON}} * I_{\text{ON}} \neq 0$$

$$\text{Blocking Loss} = V_{\text{OFF}} * I_{\text{OFF}} \neq 0$$


Switched Mode Power Conversion

Real Switch – In the VI Plane

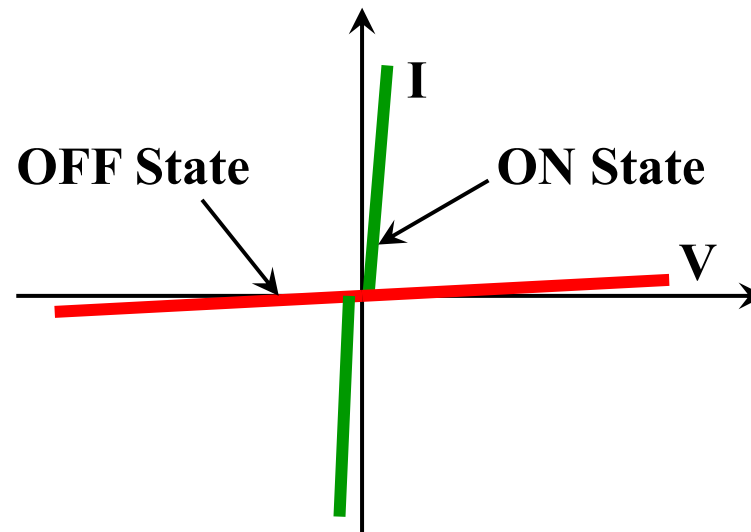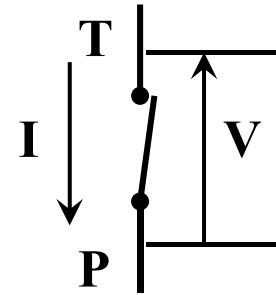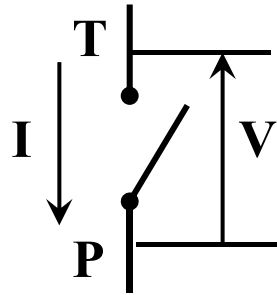

Switched Mode Power Conversion

A Sample Real Switch – Diode

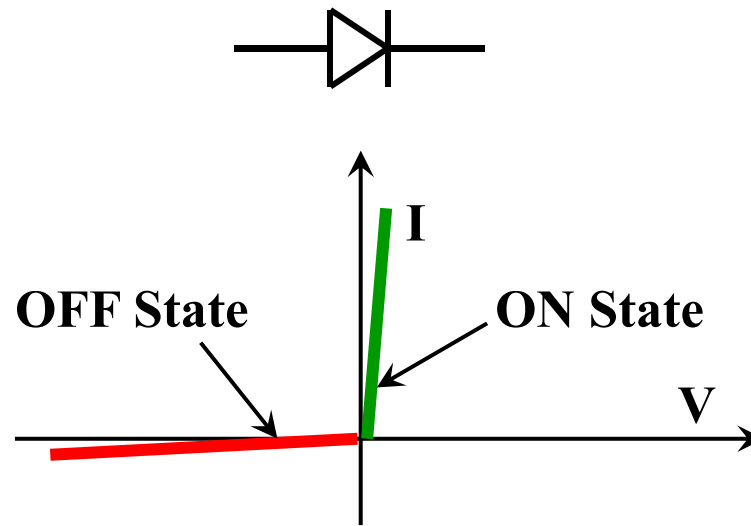


Diode

ON Switch for $I > 0$

OFF Switch for $V < 0$

Switched Mode Power Conversion

A Sample Real Switch – Diode

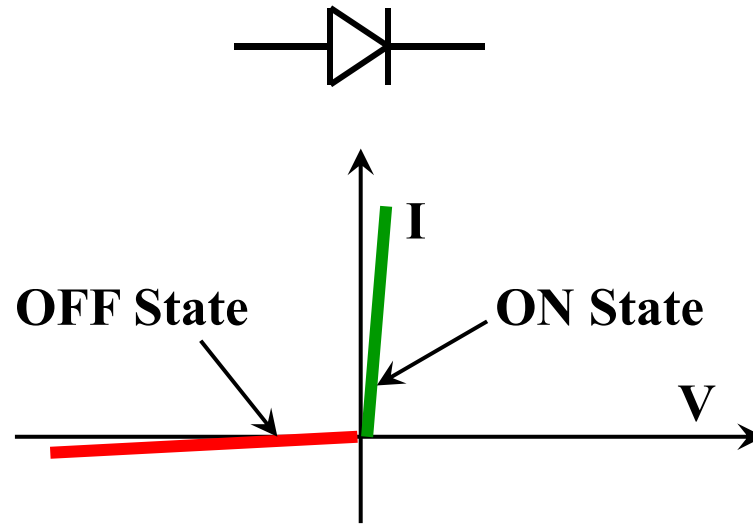


Single Quadrant Switch

Uncontrolled Switch

Switched Mode Power Conversion


Diode – Typical Datasheet

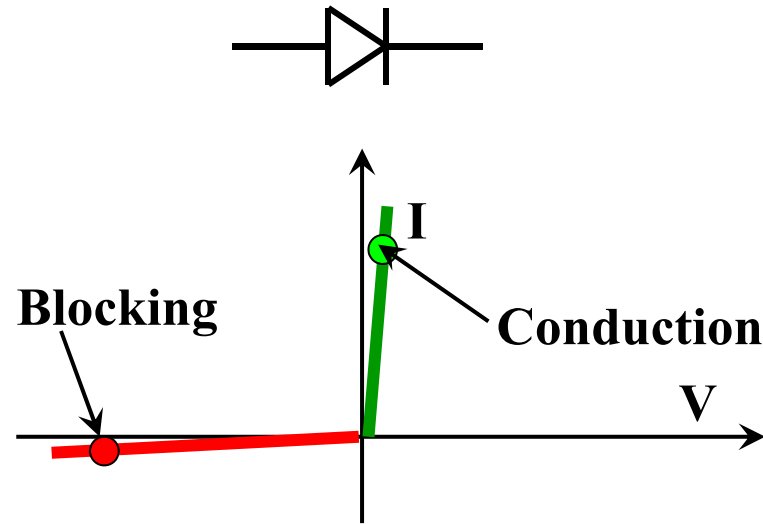

20ETS Diodes

Switched Mode Power Conversion

Diode – Percentage Loss

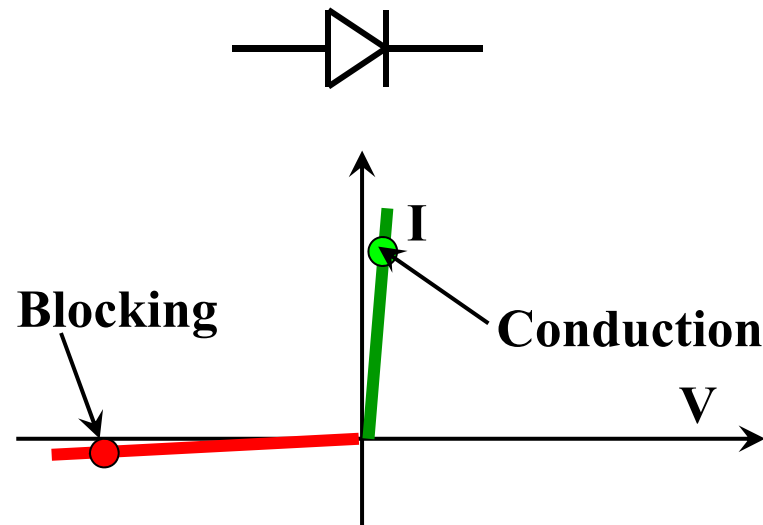

Conduction Loss : $(1.1\text{V}/20\text{A})$ 22 W @ 25 °C


Blocking Loss : $(0.1\text{mA}/800\text{V})$ 0.8 W @ 25 °C

Blocking Loss is Invariably Negligible

True for All Switching Devices

Switched Mode Power Conversion

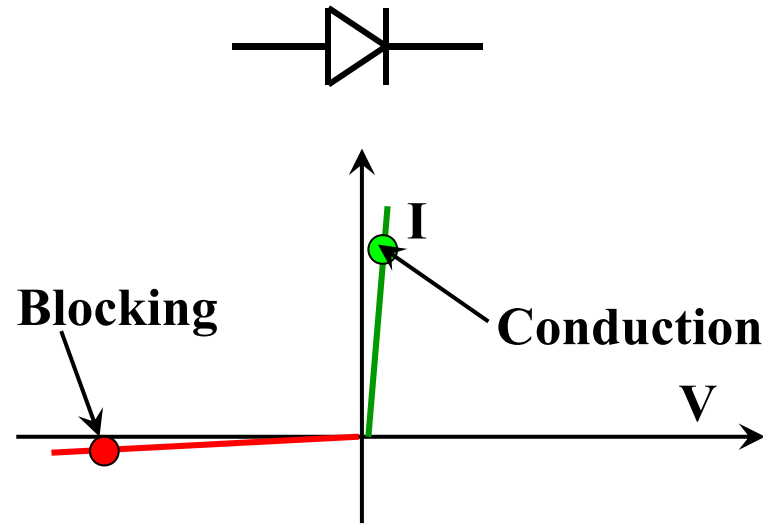Diode – Temperature Co-efficient of V_{ON}



Conduction Drop



1.0V/10A @ 25°C ; 0.9V/10A @ 150°C

20ETS Diodes

Caution is Required in Parallel Operation

Switched Mode Power Conversion



Diode – A Simple Application

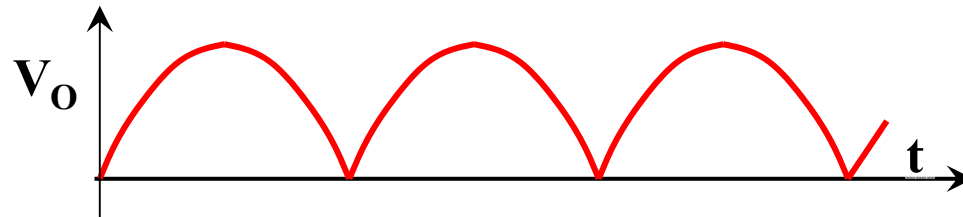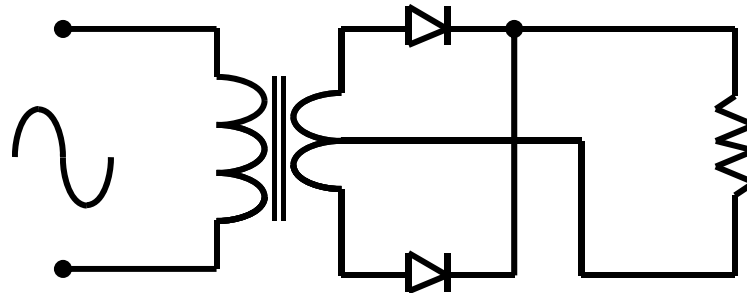

AC/DC Rectifier

Switched Mode Power Conversion

Another Real Switch – SCR

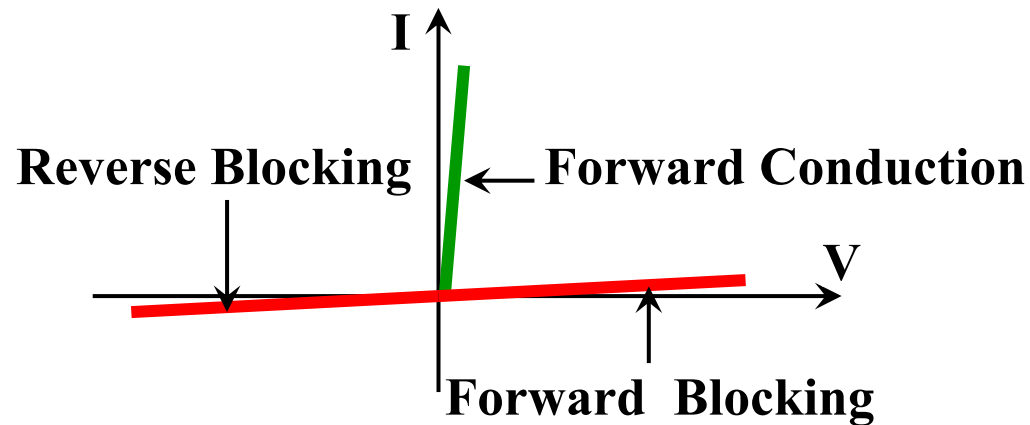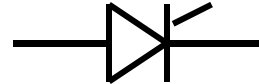



SCR

ON Switch for $I > 0$

OFF Switch for $V < 0$; $V > 0$

Switched Mode Power Conversion

Another Real Switch – SCR

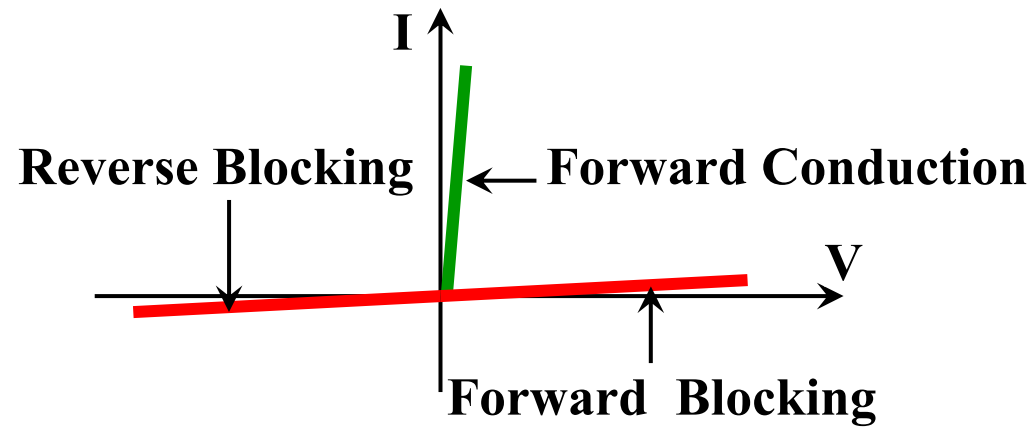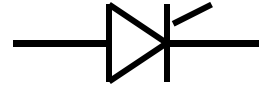


SCR

Two Quadrant Switch

Semicontrolled Switch

Switched Mode Power Conversion


SCR – Data Sheet

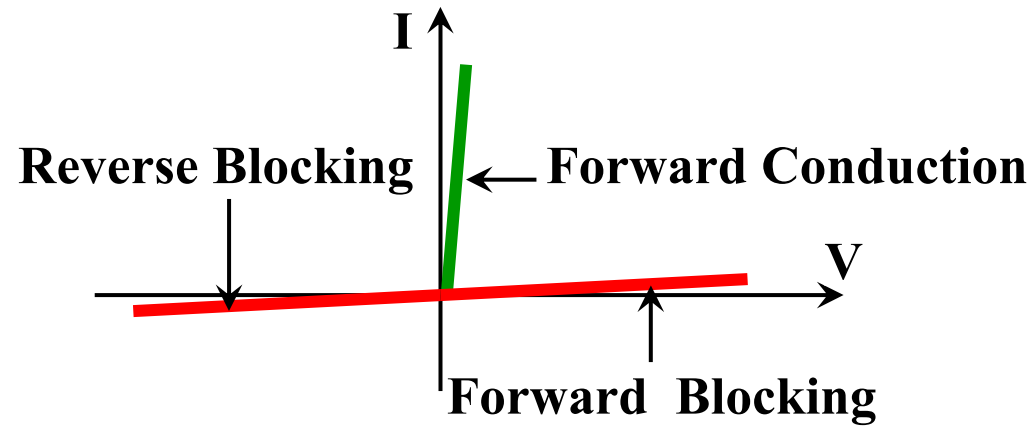

SCR

Switched Mode Power Conversion

SCR – Data Sheet

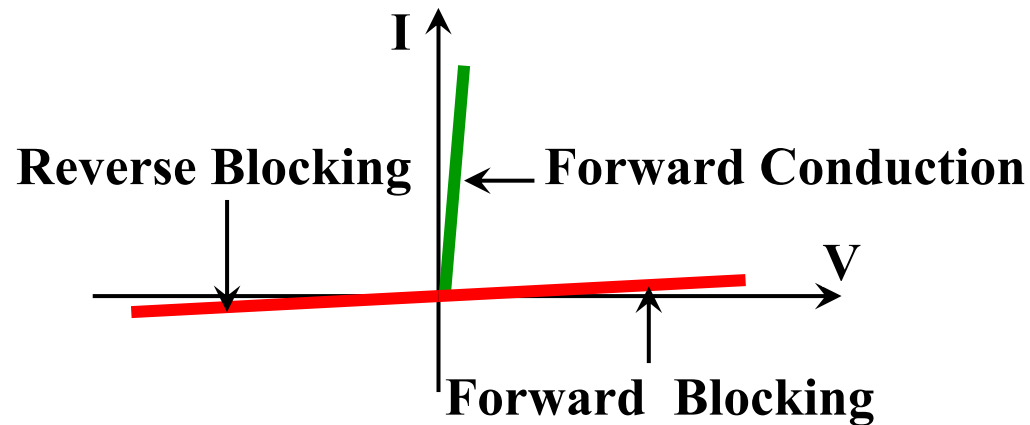

Conduction Loss : $(1.7\text{V}/32\text{A})$ 54 W @ 25 °C



Blocking Loss : $(2 \text{ mA}/400\text{V})$ 0.8 W @ 25 °C

Blocking Losses or Invariably Negligible

True for All Switching Devices

Switched Mode Power Conversion

SCR – A Simple Application

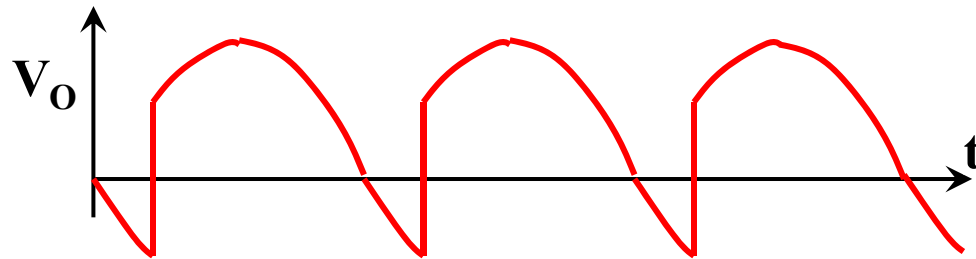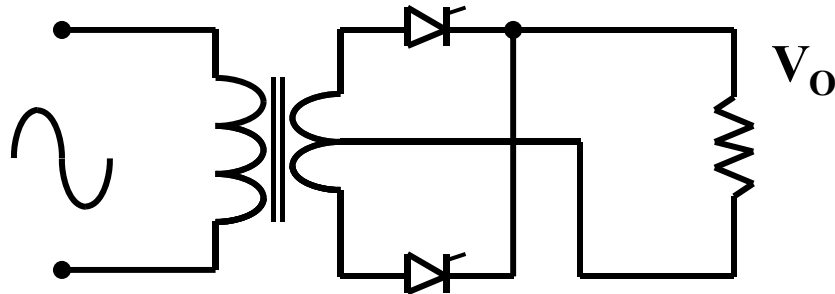

Controlled AC/DC Rectifier

Switched Mode Power Conversion

Diode & SCR – Short Circuit Protection




20ETS Diodes

SCR

For Satisfactory Protection
Fuse $I^2t < \text{Device } I^2t$

Switched Mode Power Conversion

Power Device – Thermal Protection

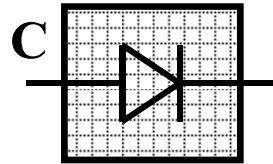

20ETS Diodes

SCR

Device is Mounted on a Case C

$$R_{TH}(JC) * P = \Theta_J - \Theta_C$$

$R_{TH}(JC)$: Thermal Resistance


P : Power Dissipation in Device

Θ_J : Junction Temperature

Θ_C : Case Temperature

Switched Mode Power Conversion

Thermal Protection – An Example

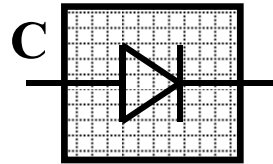

20ETS Diodes

Device is Mounted on a Case C

$$R_{TH}(JC) * P = \Theta_J - \Theta_C$$

$$R_{TH}(JC) : 1.3 \text{ }^{\circ}\text{C/W}$$



$$P : 22 \text{ W}$$

$$\Theta_J : 125 \text{ }^{\circ}\text{C}$$

$$\Theta_C : ? = 96.4 \text{ }^{\circ}\text{C}$$

Switched Mode Power Conversion

Diode – Dynamic Performance

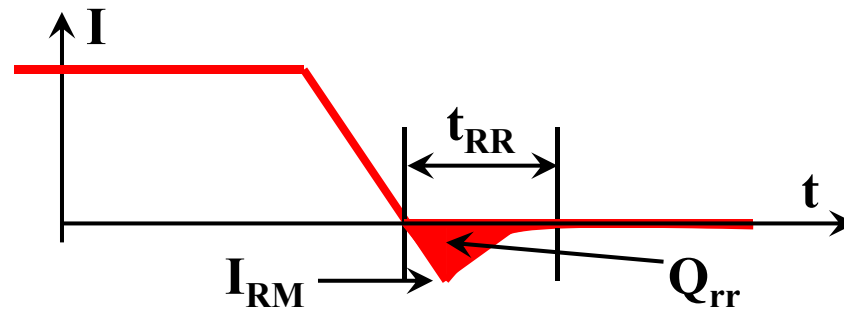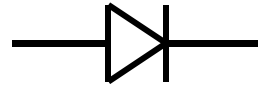


RHRG

$$I_{RM} = t_A * dI_F/dt = 5 \text{ A}$$

Switched Mode Power Conversion

A Fully Controlled Switch – BJT

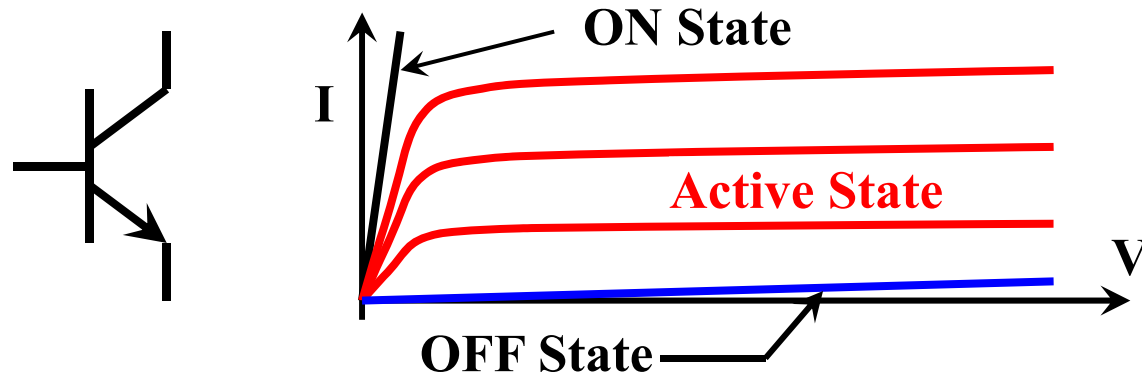


BJT

ON Switch for $I > 0$

OFF Switch for $V > 0$

Switched Mode Power Conversion

A Fully Controlled Switch – BJT

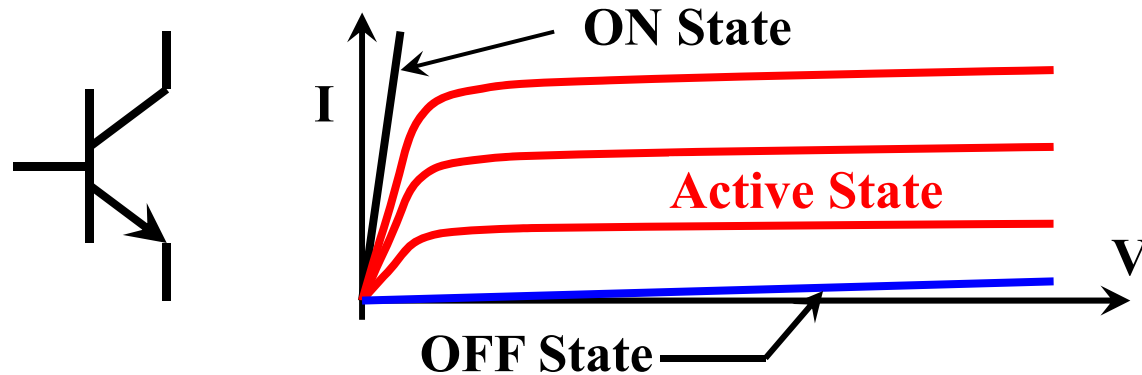

BJT


Single Quadrant Switch

Fully Controlled Switch

Current Controlled Switch

Switched Mode Power Conversion

BJT – Data Sheet

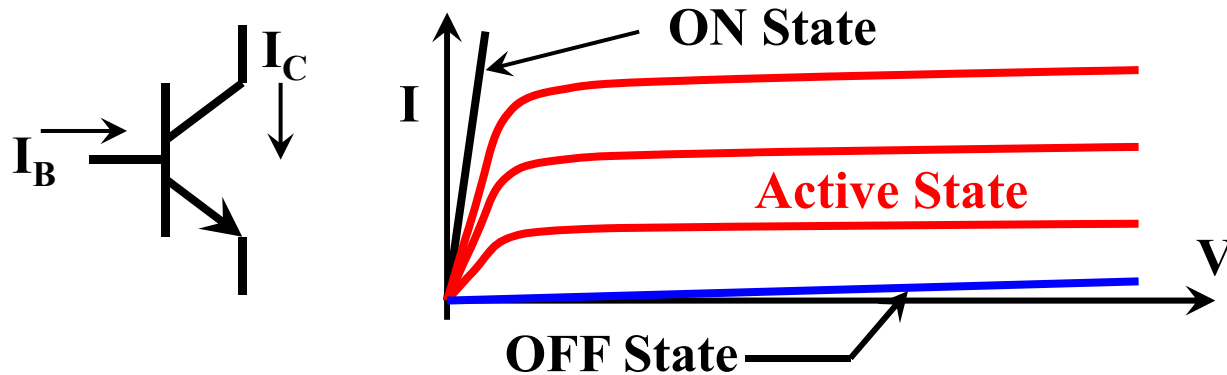

BJT


$V_{CE}(\text{sat}) : 1.5 \text{ V @ } I_C = 10 \text{ A}, I_B = 2 \text{ A}$

$R_{TH}(\text{JC}) : 1^\circ\text{C/W}$

$I_{CEX} : 2 \text{ mA}$

Switched Mode Power Conversion

A Fully Controlled Switch – MOSFET

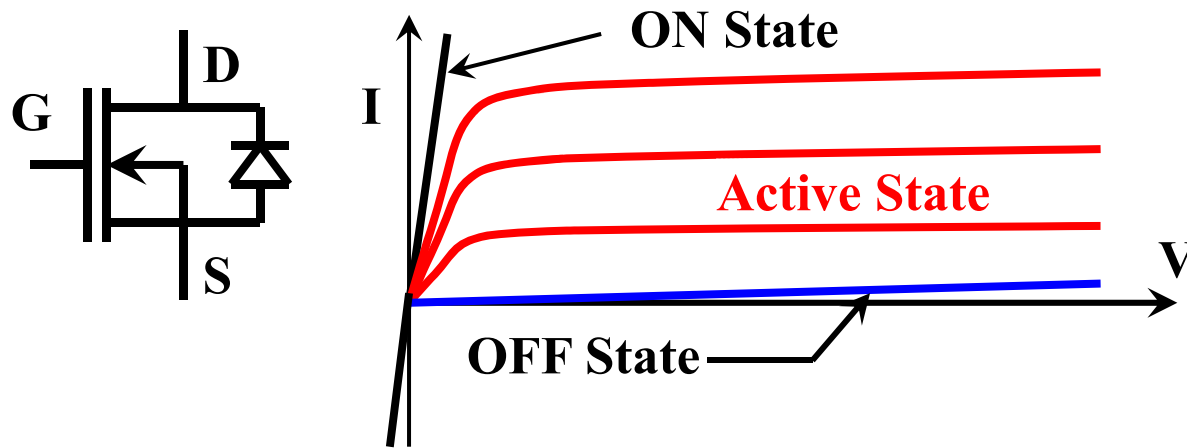


MOSFET

ON Switch for $I > 0$ & $I < 0$

OFF Switch for $V > 0$

Switched Mode Power Conversion

A Fully Controlled Switch – MOSFET

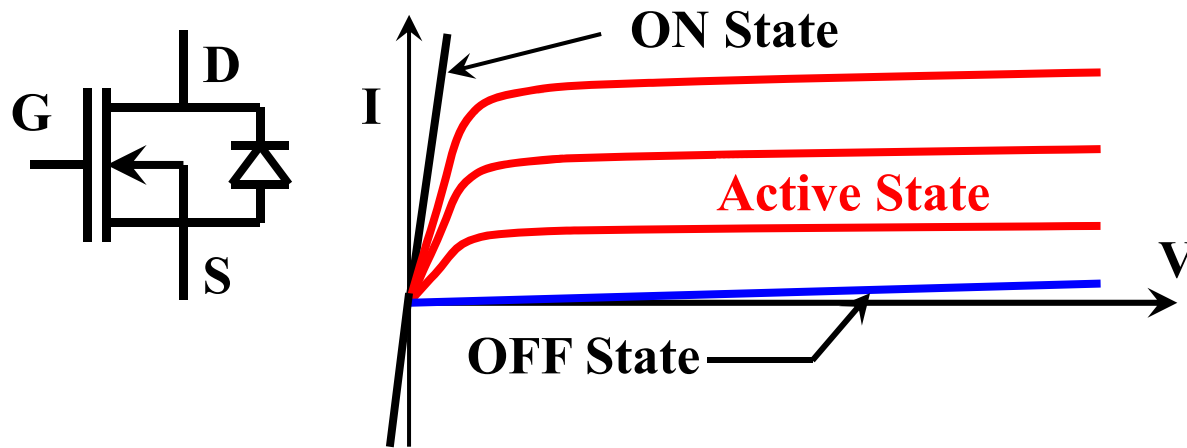

MOSFET


Two Quadrant Switch

Fully Controlled Switch

Voltage Controlled Switch

Switched Mode Power Conversion

MOSFET – Data Sheet

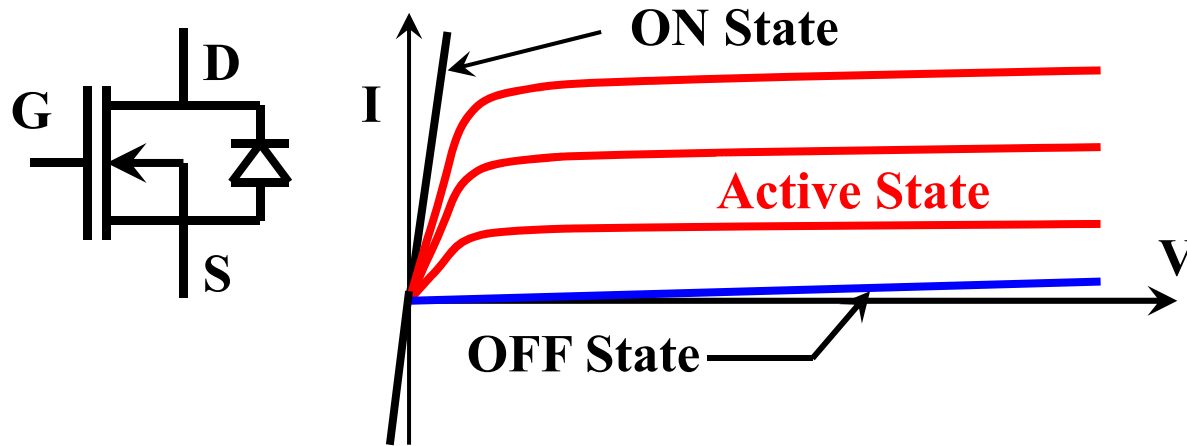

MOSFET


$R_{DS(on)} : 0.05 \, \Omega @ I_D = 16 \, A, V_{GS} = 10 \, V$

$R_{TH(JC)} : 1.6^\circ C/W$

$I_{CEX} : 250 \, \mu A$

Switched Mode Power Conversion

A Fully Controlled Switch – IGBT

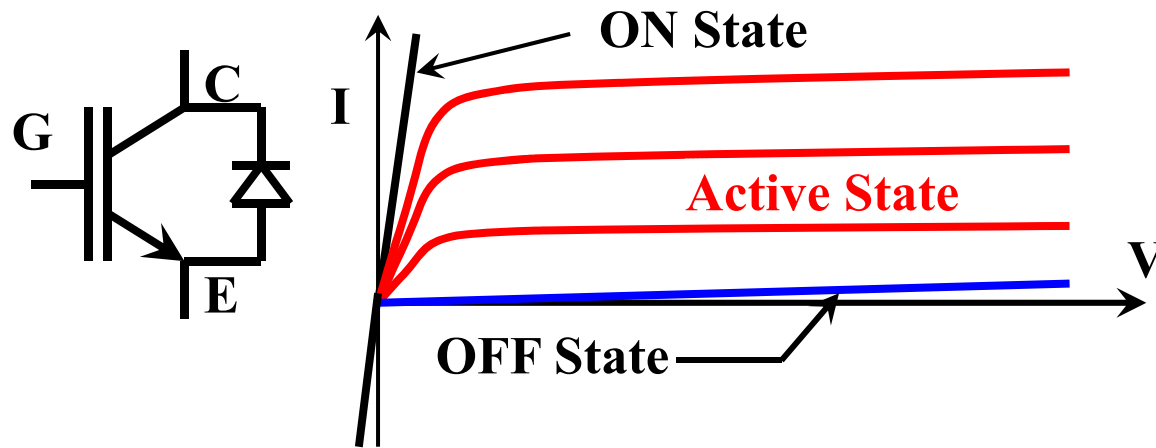


IGBT

ON Switch for $I > 0$ & $I < 0$

OFF Switch for $V > 0$

Switched Mode Power Conversion

A Fully Controlled Switch – IGBT

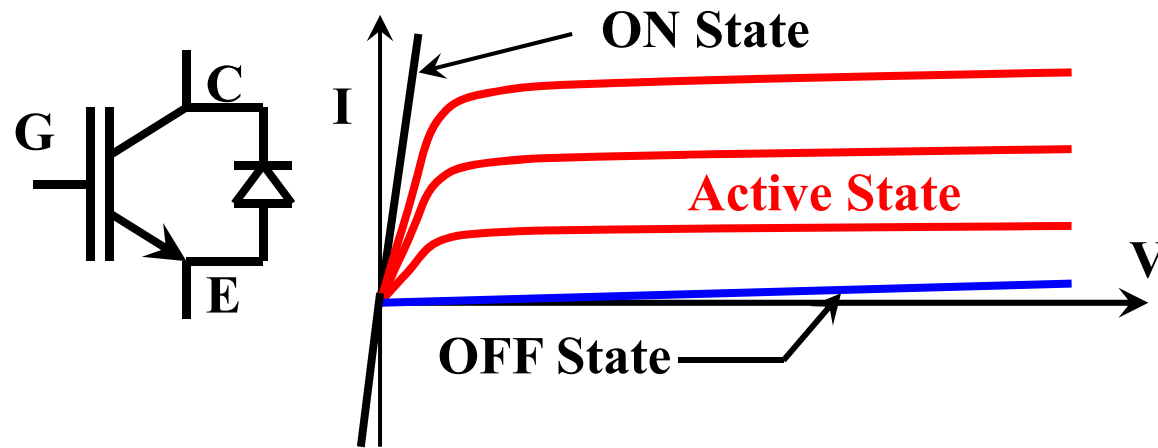

IGBT


Two Quadrant Switch

Fully Controlled Switch

Voltage Controlled Switch

Switched Mode Power Conversion

IGBT – Data Sheet

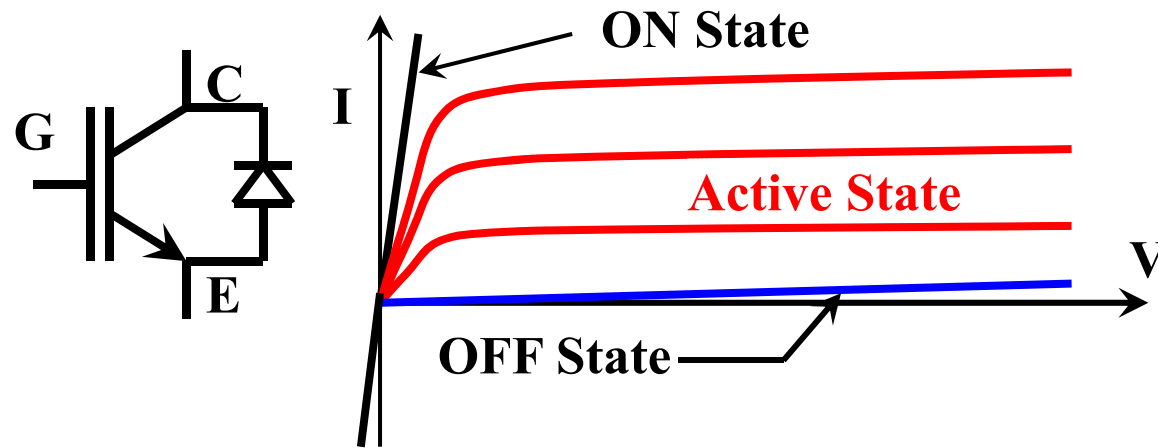

IGBT


$V_{CE}(\text{sat}) : 3.5 \text{ V @ } I_C = 30 \text{ A, } V_{GE} = 15 \text{ V}$

$R_{TH}(JC) : 0.6^\circ\text{C/W}$

$I_{CEX} : 4 \text{ mA}$

Switched Mode Power Conversion

Compound Switches

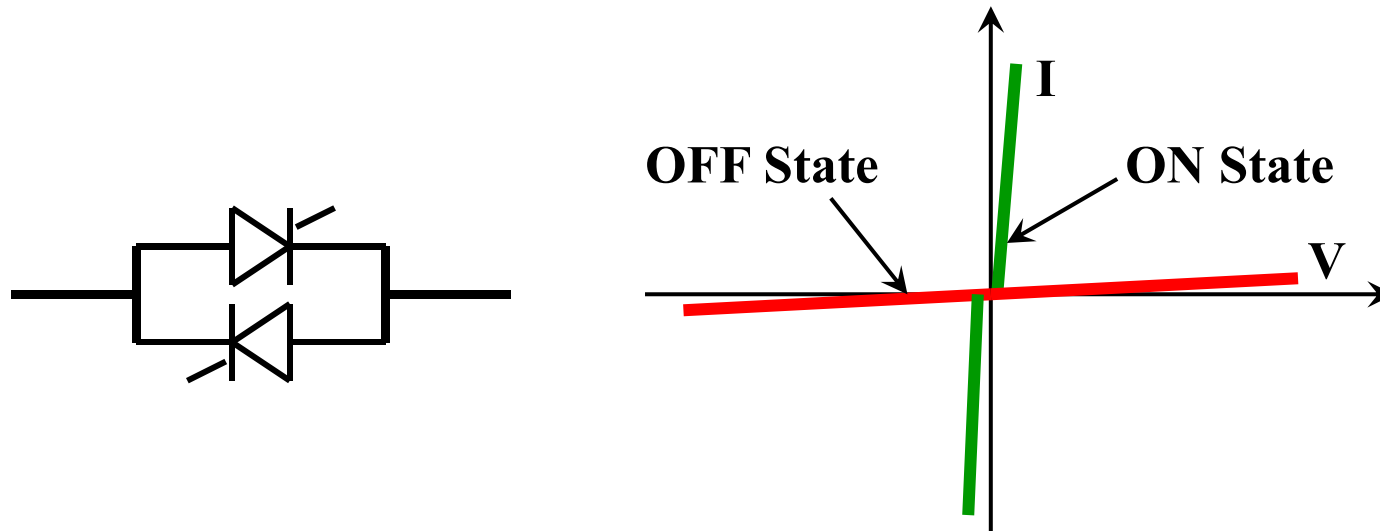

Anti-parallel SCRs


Four Quadrant Switch

Semicontrolled Switch

Pulse Triggered Switch

Switched Mode Power Conversion

Compound Switches

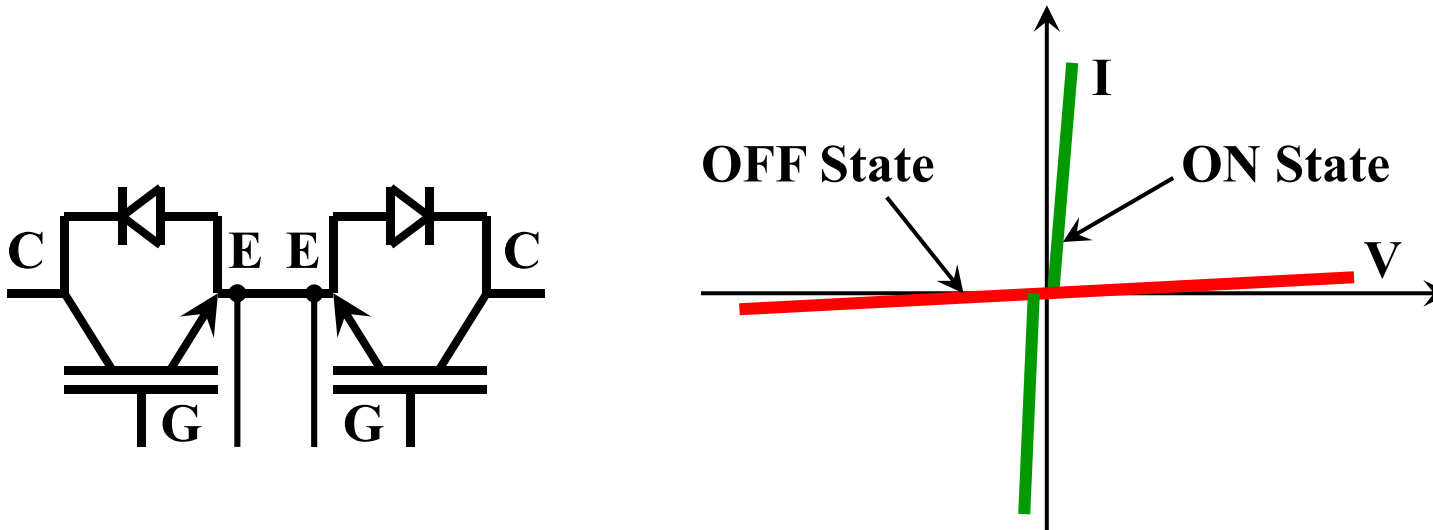

Anti-parallel MOSFET/IGBTs


Four Quadrant Switch

Fully Controlled Switch

Voltage Controlled Switch

Switched Mode Power Conversion

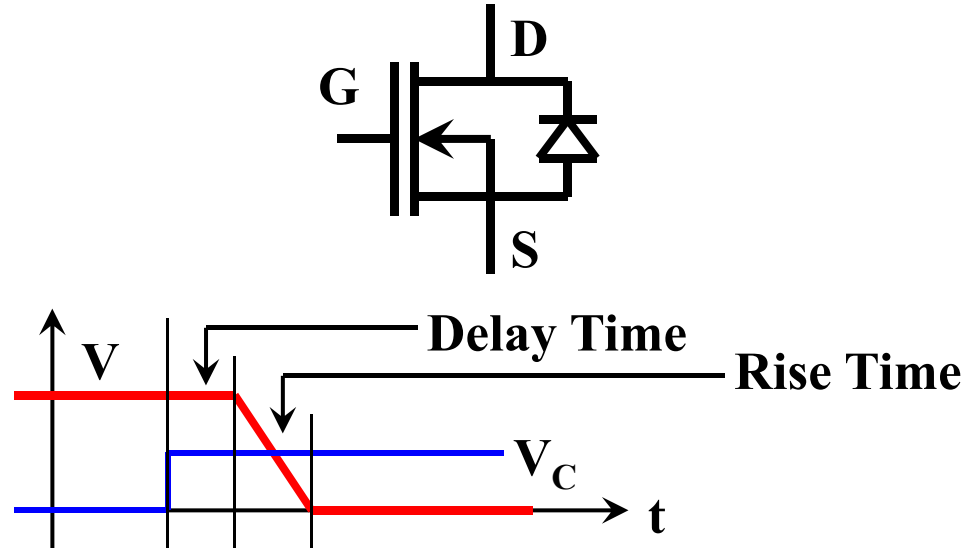Switching Characteristics – Controlled Switch



MOSFET – Turn-On


Turn-on delay time (t_d)

Rise time (t_r)

In time t_r , Switch voltage drops linearly to zero

Switched Mode Power Conversion

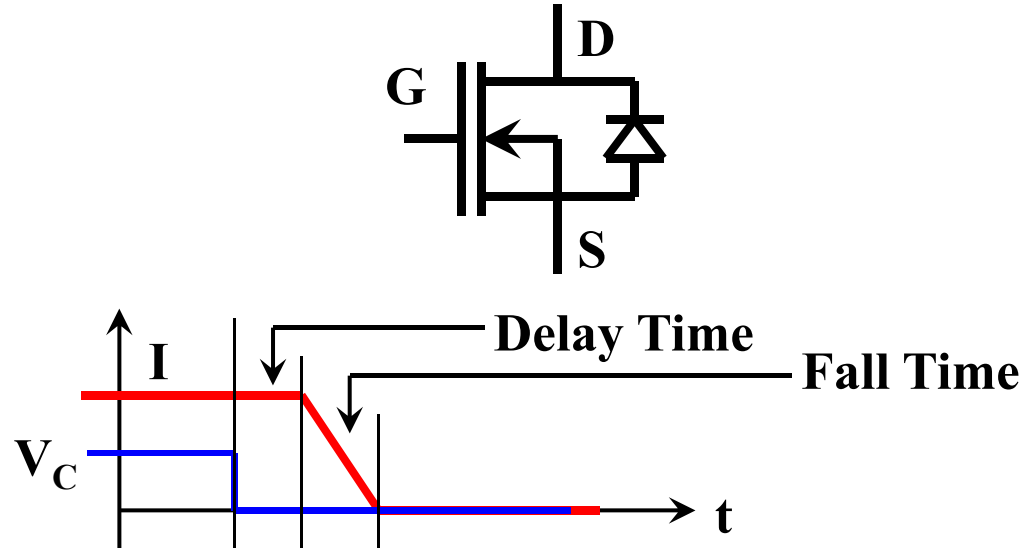Switching Characteristics – Controlled Switch



MOSFET – Turn-Off



Turn-off delay time (t_d)

Fall time (t_f)

In time t_f , Switch current drops linearly to zero

Switched Mode Power Conversion

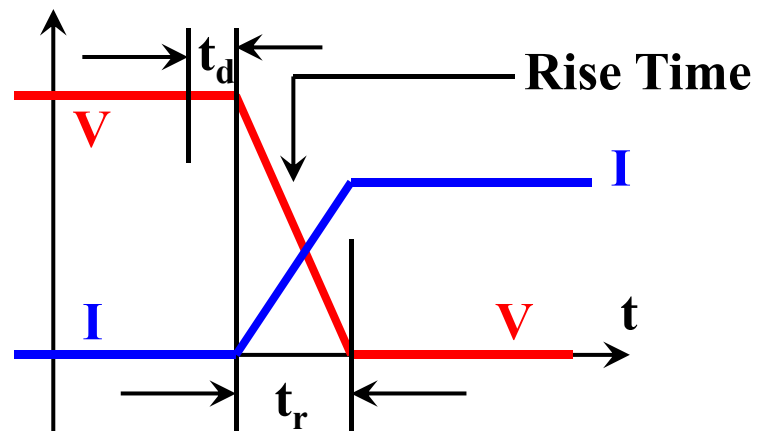
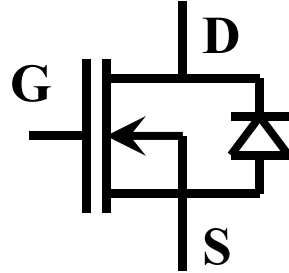
Switching Characteristics – Controlled Switch



MOSFET – Turn-On – Resistive Load

Switched Mode Power Conversion


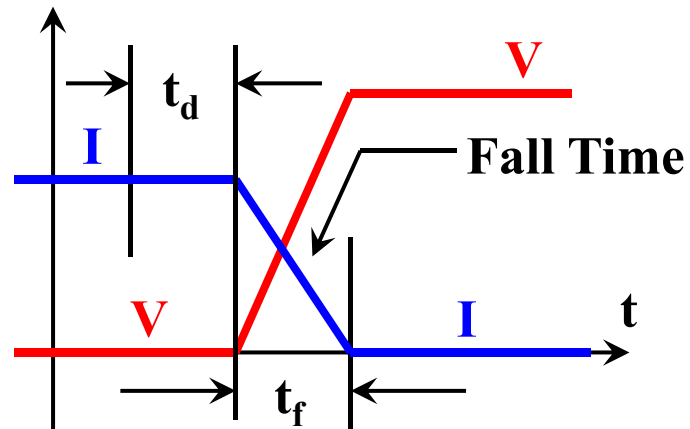
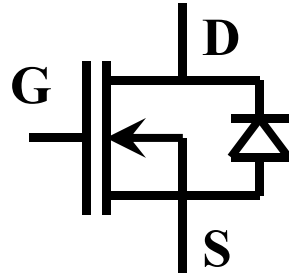
Switching Characteristics – Controlled Switch



MOSFET – Turn-Off – Resistive Load

Switched Mode Power Conversion



Switching Characteristics – Data Sheet

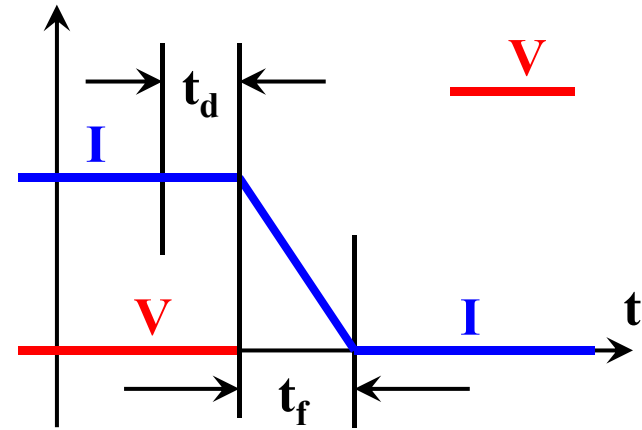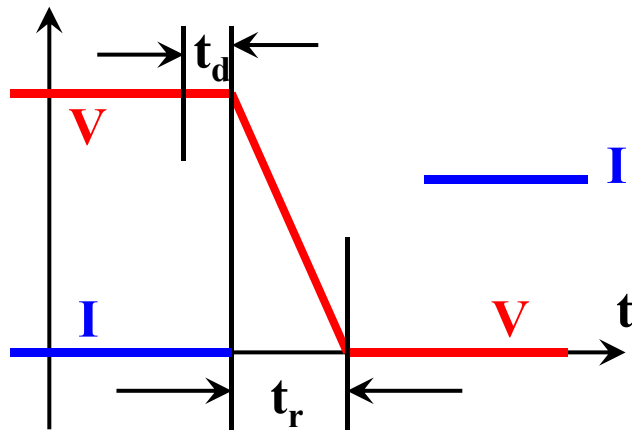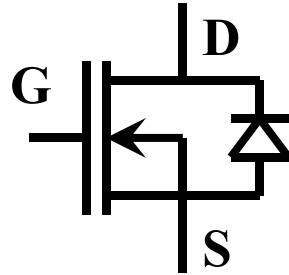

MOSFET

Switched Mode Power Conversion



Switching Characteristics

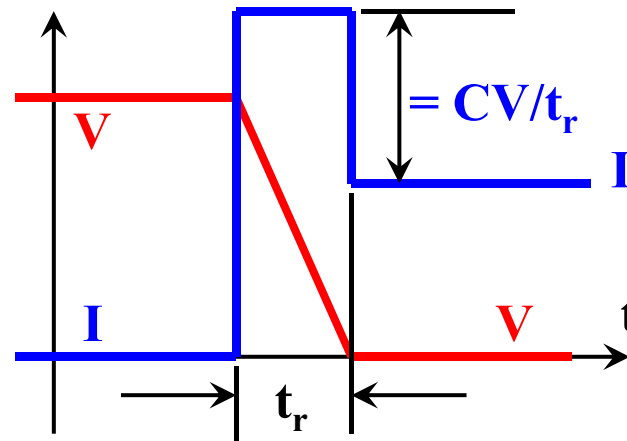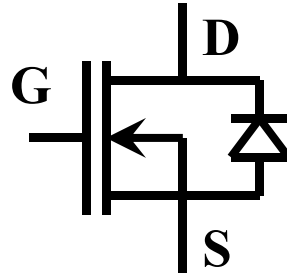

Turn-On of Capacitive Load
Over-current in Turn-On

Switched Mode Power Conversion

Switching Characteristics

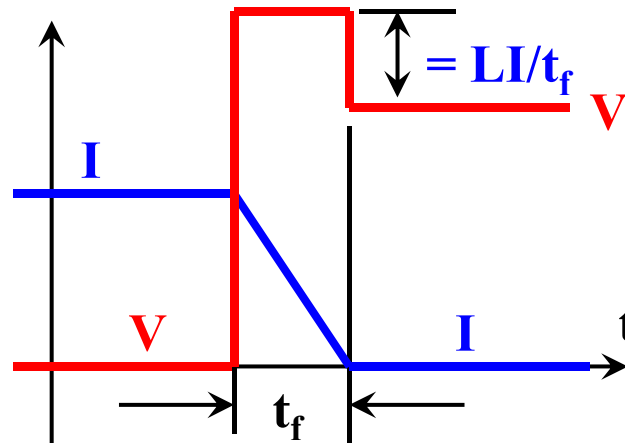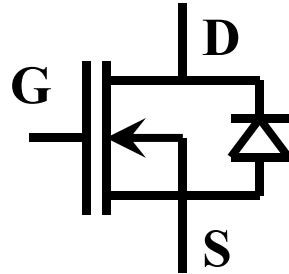


Turn-Off of Inductive Load

Over-voltage in Turn-Off

Switched Mode Power Conversion

Switching Stress

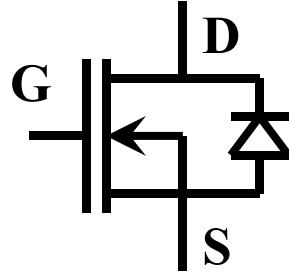

Preferred Load

Inductive Turn-On & Capacitive Turn-Off


Switching-Aid Circuits

(Snubber Circuits)

Exploit this Feature

Switched Mode Power Conversion

Switching Aid Circuit

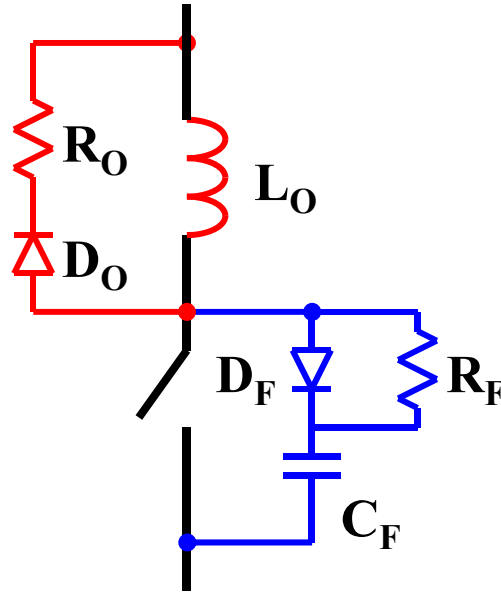


Strategy for Reducing Switching Stress

L_O , R_O , D_O , form Turn-On Aid Circuit

L_F , R_F , D_F , form Turn-Off Aid Circuit


Switched Mode Power Conversion

Switching V-I Characteristic

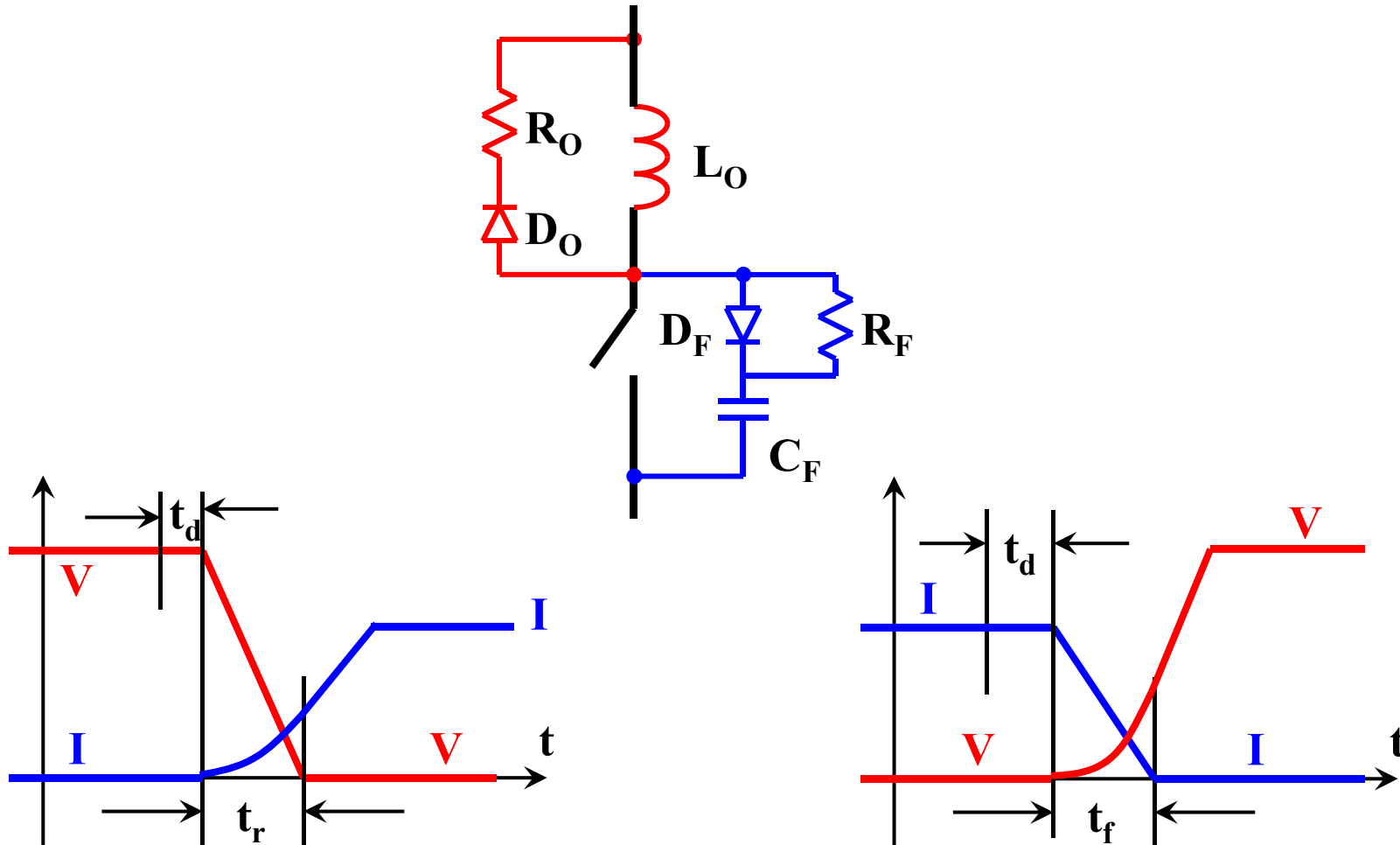


Switched Mode Power Conversion

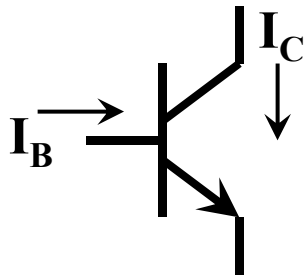
Other Fully Controlled Switches – Data Sheet



BJT

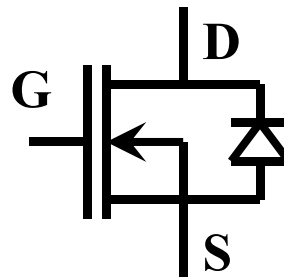


MOSFET

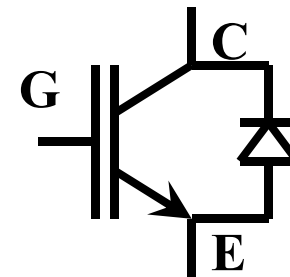

IGBT

Switched Mode Power Conversion

Switching Aid Circuit – Sample Design

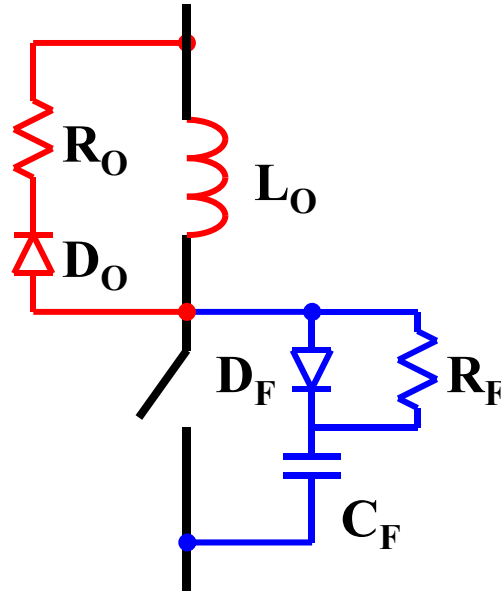

Switching Voltage & Current


400 V, 15 A

Switching Time

400 ns

Switched Mode Power Conversion

Switching Aid Circuit – Sample Design

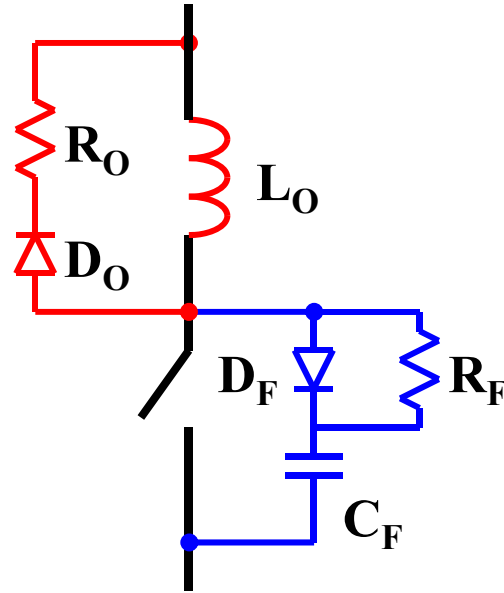



Apparent Switching Loss

$$400 * 15 * 0.4 \mu\text{J}$$

2.4 mJ per switching

Switched Mode Power Conversion

Turn-On Snubber Design

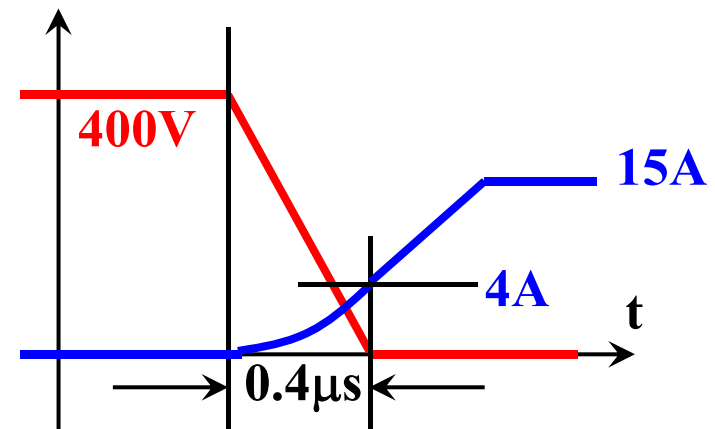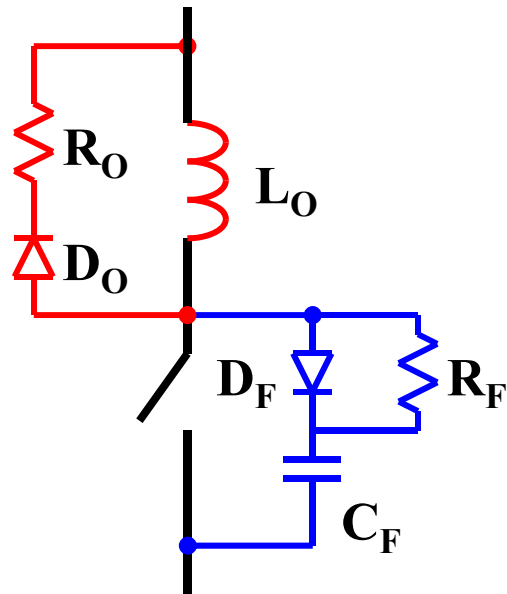

Switched Mode Power Conversion



Turn-On Snubber Design

$$L_O = (0.5 \cdot 400 \cdot 0.4 \mu\text{s}) / 4 = 20 \mu\text{H}$$

$$\text{Switching loss} = (400 \cdot 4 \cdot 0.4 \mu\text{s}) / 12$$

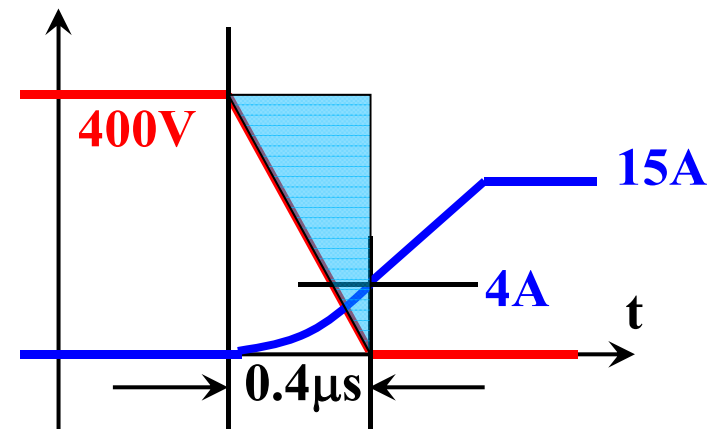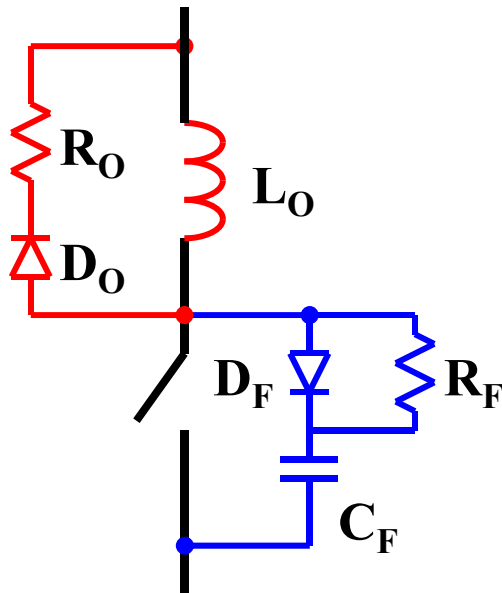
0.053 mJ per switching

Select L_O/R_O to be much less than T_{ON}



Switched Mode Power Conversion

Switching Aid Circuit – Sample Design

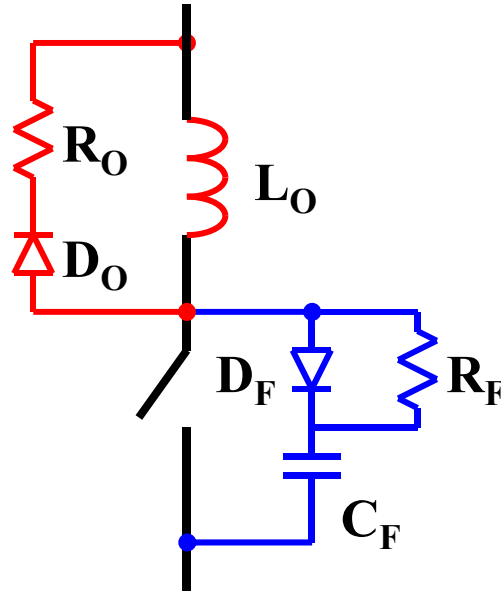

Switching Voltage & Current


400 V, 15 A

Switching Time

800 ns

Switched Mode Power Conversion

Switching Aid Circuit – Sample Design

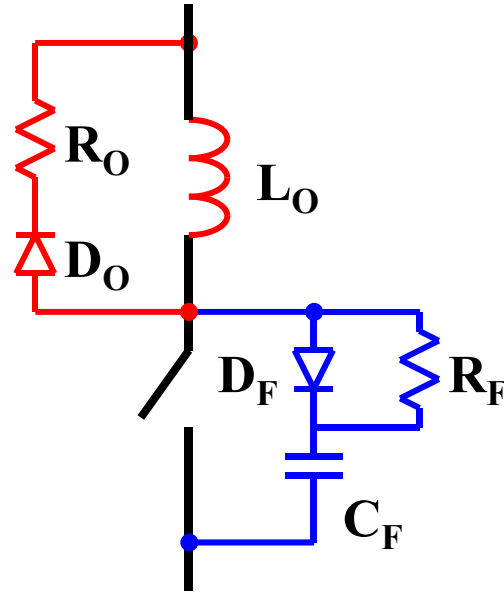



Apparent Switching Loss

$$400 * 15 * 0.8 \mu\text{J}$$

4.8 mJ per switching

Switched Mode Power Conversion

Turn-Off Snubber Design

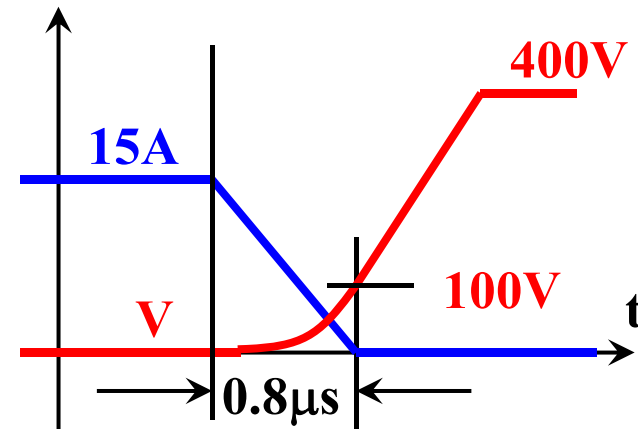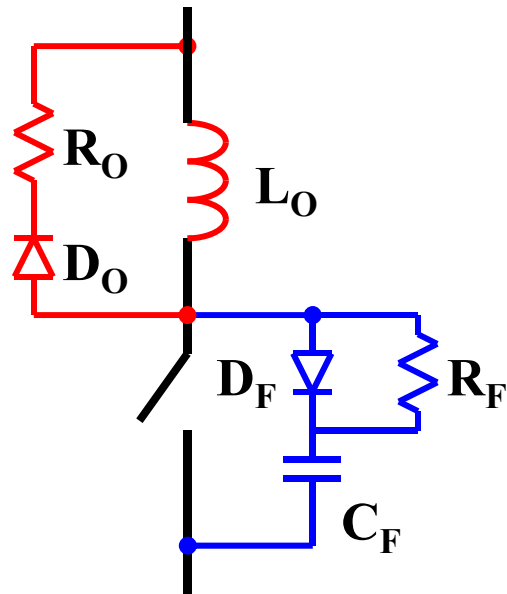

Switched Mode Power Conversion



Turn-Off Snubber Design

$$C_O = (0.5 \cdot 15 \cdot 0.8 \mu s) / 100 = 0.06 \mu F$$

$$\text{Switching loss} = (15 \cdot 100 \cdot 0.8 \mu s) / 12$$

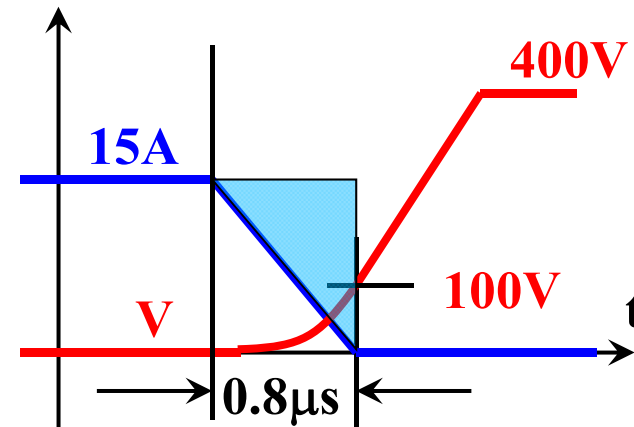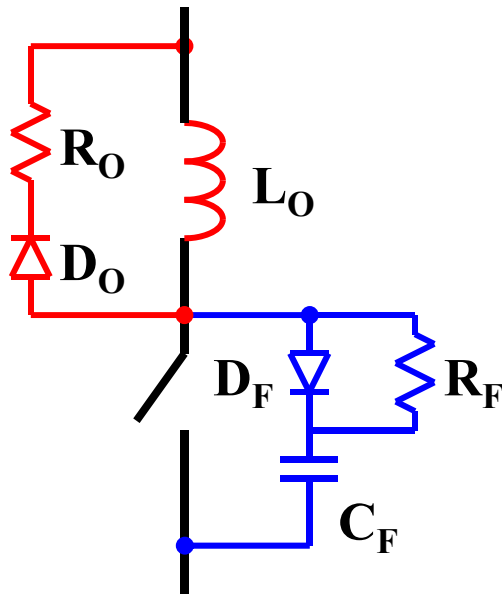0.01 mJ per switching

Select $C_F R_F$ to be much less than T_{OFF}



Switched Mode Power Conversion

Switches – Summary

Ideal Switch

Lossless Operation

Instantaneous Operation

Four Quadrant Operation

Switched Mode Power Conversion

Switches – Summary

Ideal Switch

Lossless, Instantaneous, Four Quadrant

Real Switches

Uncontrolled Switch – Diode

Semiconrolled Switch – SCR

Controlled Switch – BJT, MOSFET, IGBT

Single & Multiquadrant Switches

Losses & Thermal Design

Switched Mode Power Conversion

Switches – Summary

Ideal Switch

Lossless, Instantaneous

Real Switches

Diode, SCR, BJT, MOSFET, IGBT

Single & Multiquadrant Switches

Losses & Thermal Design

Protection

Fuse Protection – Diodes & SCRs

Through Driver – BJT, MOSFET, IGBT

Switched Mode Power Conversion

Switches – Summary

Ideal Switch

Lossless, Instantaneous

Real Switches

Diode, SCR, BJT, MOSFET, IGBT

Single & Multiquadrant Switches

Losses & Thermal Design

Protection

Fuse Protection – Diodes & SCRs

Through Driver – BJT, MOSFET, IGBT

Switching Transients

Switching Aid Circuit