


Week 4: Course Material

Test Generation

Lecture 17

Test

Generation


- D Introduction
 - D Random Test Generation
 - D Theoretical Foundations
 - D Deterministic Combinational ATPG
 - D Untestable Fault Identification
 - D Simulation-based ATPG
 - D ATPG for Delay and Bridge Faults
 - D Other Topics in Test Generation
 - D Concluding Remarks
- 

Introduction

- ▷ Test generation is the bread-and-butter in VLSI Testing
 - Efficient and powerful ATPG can alleviate high costs of DFT
 - Goal: generation of a small set of effective vectors at a low computational cost
- ▷ ATPG is a very challenging task
 - Exponential complexity
 - Circuit sizes continue to increase (Moore's Law)
 - Aggravate the complexity problem further
 - Higher clock frequencies
 - Need to test for both structural and delay defects

Conceptual View of ATPG

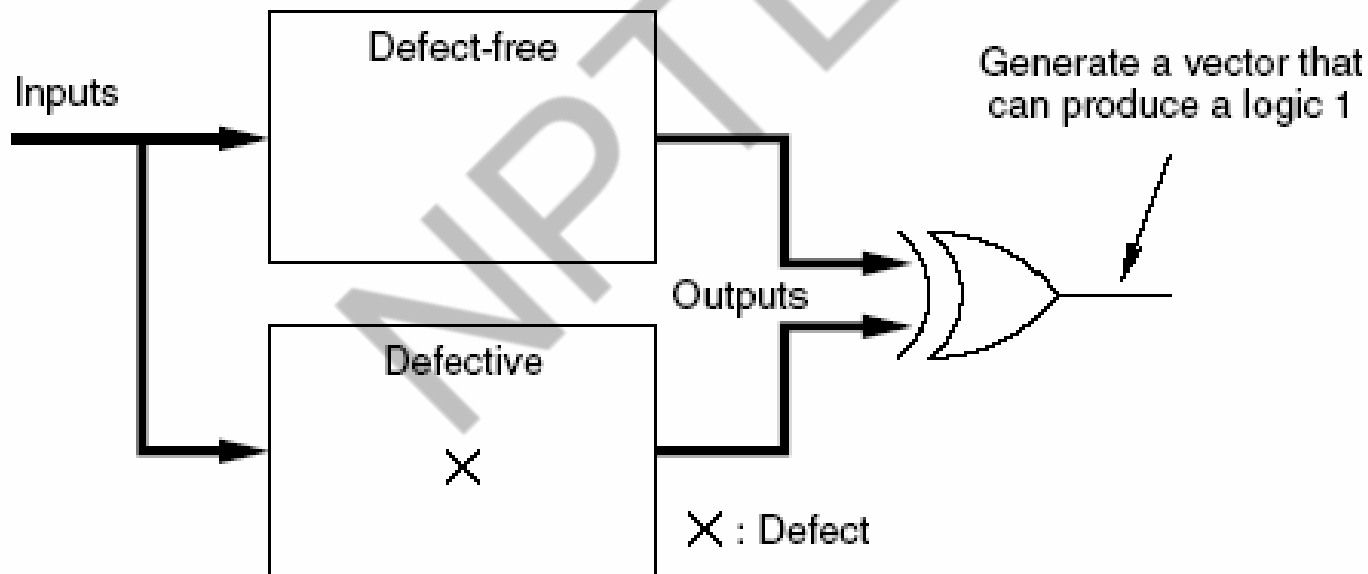- ▷ Generate an input vector that can distinguish the defect-free circuit from the hypothetically defective one




Fault Models

- ▯ Instead of targeting specific defects, fault models are used to capture the logical effect of the underlying defect
- ▯ Fault models considered in this chapter:
 - Stuck-at fault
 - Bridging fault
 - Transition fault
 - Path-delay fault

Simple illustration of ATPG

 - ▷ Consider the fault d/1 in the defective circuit
- ▷ Need to distinguish the output of the defective circuit from the defect-free circuit
- ▷ Need: set d=0 in the defect-free circuit
- ▷ Need: propagate effect of fault to output
- ▷ Vector: abc=001 (output = 0/1)



A Typical ATPG System

- ▷ Given a circuit and a fault model
 - Repeat
 - Generate a test for each undetected fault
 - Drop all other faults detected by the test using a fault simulator
 - Until all faults have been considered
- ▷ Note 1: a fault may be untestable, in which no test would be generated
- ▷ Note 2: an ATPG may abort on a fault if the resources needed exceed a preset limit

Random Test Generation

- ▷ Simplest form of test generation
 - N tests are randomly generated
- ▷ Level of confidence on random test set T
 - The probability that T can detect all stuck-at faults in the given circuit
 - Quality of a random test set highly depends on the underlying circuit
 - Some circuits have many **random-resistant** faults

Weighted Random Test Generation

- ▮ Bias input probabilities to target random resistant faults
- ▮ Consider an 8-input AND gate
 - Without biasing input probabilities, the prob of generating a logic 1 at the gate output = $(0.5)^8 = 0.004$
 - If we bias the inputs to 0.75, then the prob of generating a logic 1 at the gate output = $(0.75)^8 = 0.100$
- ▮ Obtaining an optimal set of input probabilities a difficult task
- ▮ Goal: increase the signal probabilities of hard-to-test regions

Probability of Fault Detection

- ▷ Given a circuit with n inputs
- ▷ Let T_f be the set of vectors that can detect fault f
- ▷ Then $d_f = \frac{|T_f|}{2^n}$ is the prob that f can be detected by a random vector
- ▷ Let $e_f = 1 - d_f$ be the prob that a random vector cannot detect f


Prob of Fault Detection (Cont.)

- ▷ Then, $e_f^N = (1 - d_f)^N$ is the prob that N random vectors do not detect f
- ▷ Thus, the prob that at least one out of N random vectors can detect f is

$$1 - (1 - d_f)^N$$

Minimum Detection Probability

 - ▯ The min detection prob of any detectable fault actually does **not** depend on n , the num of PIs
- ▯ Instead, it depends on the largest primary-output cone that it is in
- ▯ This is because any detectable fault must be excited and sensitized to a primary output



Lemma

1

- In a combinational circuit with multiple outputs, let n_{max} be the number of primary inputs that can lead to a primary output. Then, the detection probability for the most difficult detectable fault, d_{min} , is: $d_{min} \geq (0.5)^{n_{max}}$

Exhaustive Test Generation

D Exhaustive Testing

- Apply 2^n patterns to an n -input combinational *circuit under test* (CUT)
- Guarantees all detectable faults in the combinational circuits are detected
- Test time maybe be prohibitively long if the number of inputs is large
- Feasible only for small circuits

D Pseudo-exhaustive Testing

- Partition circuit into respective cones
- Apply exhaustive testing only to each cone
- Still guarantees to detect every detectable fault based on Lemma 1

Week 4: Course Material


Test Generation (Contd.)

Lecture 18

NPTEL

Theoretical Foundations: Boolean *Difference*

 - ▮ The function for the circuit is $f = xy + \bar{y}z$
- ▮ Let the target fault be $y/0$, then the function for the faulty circuit is $f' = f(y=0)$
- ▮ Goal of test generation: *find a vector that makes $f \text{ XOR } f' = 1$*



Boolean Difference

Continued

- ▷ $f \text{ XOR } f' = 1$ iff f and f' result in opposing logic values
- ▷ Thus, any vector that can set $f \text{ XOR } f' = 1$ is able to produce opposing values at the outputs of the fault-free and faulty circuits respectively
- ▷ Definition: $\frac{df}{dy} = f(y = 1) \oplus f(y = 0)$.


Boolean Difference

Example

▷ To excite the fault $y/0, y=1$

▷ Thus,
 
$$\begin{aligned}y \cdot f(y=1) \oplus f(y=0) &= y \cdot (x \oplus z) \\&= y \cdot (x\bar{z} + \bar{x}z) \\&= xy\bar{z} + \bar{x}yz\end{aligned}$$



$xyz = 110$ or 011 can detect the fault

Another Example

Let target fault be $w/0$

$$w \cdot \frac{df}{dw} = 1$$

$$\Rightarrow w \cdot (f(w=1) \oplus f(w=0)) = 1$$

$$\Rightarrow w \cdot (1 \oplus xy) = 1$$

$$\Rightarrow w \cdot (\overline{xy}) = 1$$

$$\Rightarrow w \cdot (\overline{x} + \overline{y}) = 1$$

$$\Rightarrow w\overline{x} + w\overline{y} = 1$$

But: $w = \overline{y} \cdot z$


$$w \cdot \overline{x} + w \cdot \overline{y} = 1$$

$$\Rightarrow \overline{y} \cdot z \cdot \overline{x} + \overline{y} \cdot z \cdot \overline{y} = 1$$

$$\Rightarrow \overline{x} \cdot \overline{y} \cdot z + \overline{y} \cdot z = 1$$

$$\Rightarrow \overline{y} \cdot z = 1$$

*xyz=001, 101
can detect w/0*

 

A Third Example

D Fault: $z/0$

$$z \cdot \frac{df}{dz} = 1$$


$$\Rightarrow z \cdot (f(z=1) \oplus f(z=0)) = 1$$

$$\Rightarrow z \cdot (xy \oplus xy) = 1$$

$$\Rightarrow z \cdot 0 = 1$$

$$\Rightarrow \text{UNSATISFIABLE}$$

This fault is untestable!

 

Wrap Up on Boolean Difference

- ▷ Given a circuit with output f and fault α/v ,
- ▷ The set of vectors that can detect this fault includes all vectors that satisfy

$$(\alpha = \bar{v}) \cdot \frac{df}{d\alpha} = 1$$

Deterministic ATPG

- ▷ In general, we don't need an entire set of vectors that can detect the target fault
- ▷ Instead, we just want to compute one vector quickly
- ▷ Rather than using Boolean Difference that can obtain all vectors
 - Simply use a branch-and-bound search to find one vector quickly
- ▷ Deterministic ATPG has two main goals
 - Excite the target fault
 - Propagate the corresponding fault effect to an output

5-valued Algebra for Comb. Circuits

- ▷ Instead of using two circuits (fault-free and the faulty)
 - We will solve the ATPG problem on one single circuit
- ▷ To do so, every signal value must be able to capture fault-free and faulty values simultaneously
- ▷ 5-Value Algebra: 0, 1, X, D, D-bar
 - D: 1/0
 - D-bar: 0/1

Boolean Operators on 5-Valued Algebra


AND	0	1	D	\bar{D}	X
0	0	0	0	0	0
1	0	1	D	\bar{D}	X
D	0	D	D	0	X
\bar{D}	0	\bar{D}	0	\bar{D}	X
X	0	X	X	X	X

OR	0	1	D	\bar{D}	X
0	0	1	D	\bar{D}	X
1	1	1	1	1	1
D	D	1	D	1	X
\bar{D}	\bar{D}	1	1	\bar{D}	X
X	X	1	X	X	X

NOT	
0	1
1	0
D	\bar{D}
\bar{D}	D
X	X

Decision Tree for Branch-and-Bound Search

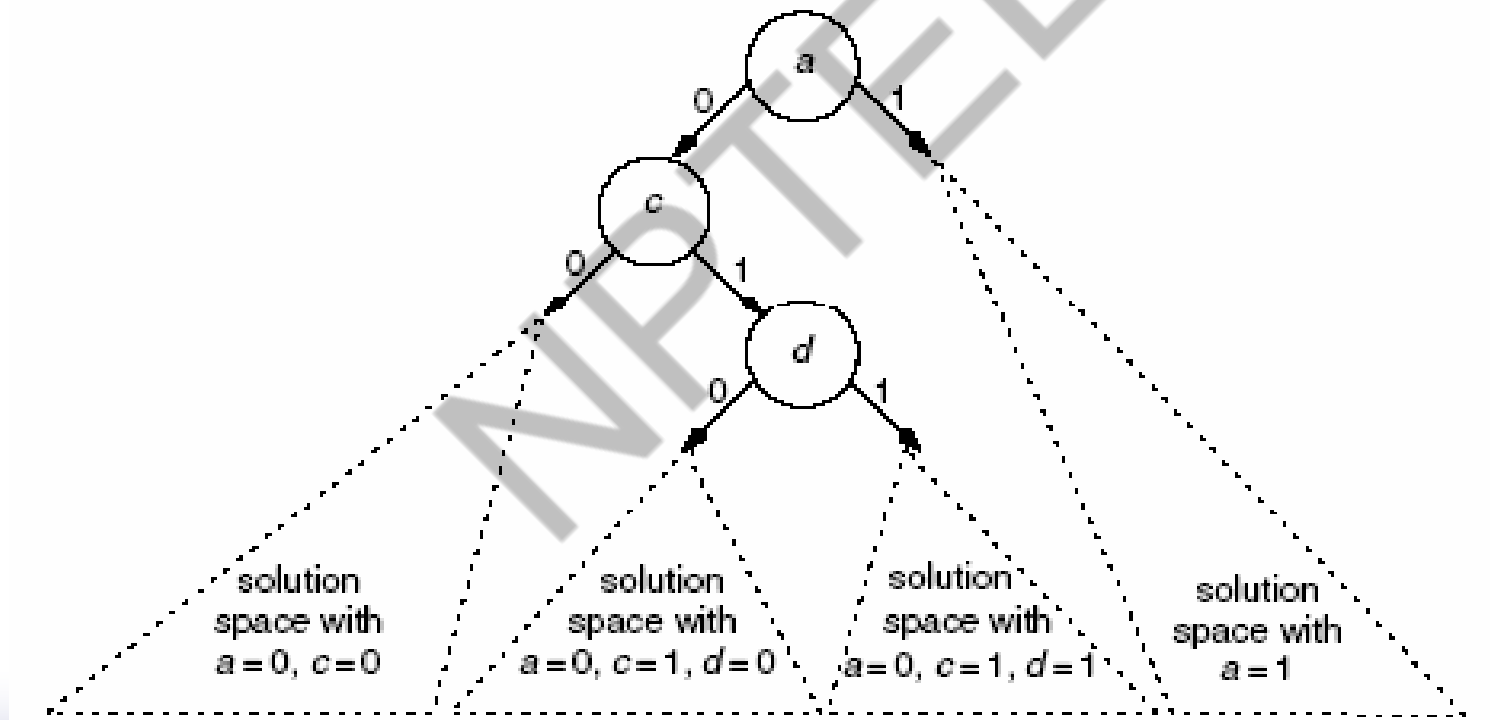
- ▮ The ATPG systematically and implicitly searches the entire search space



Backtrackin

g

 - ▯ The ATPG searches one branch at a time
- ▯ Whenever a conflict (e.g., all D's disappeared) arises, must backtrack on previous decisions



If $d=1$ also causes a conflict, backtrack to $c=0$

Basic ATPG for Fanout-Free Circuits

Algorithm 2 Basic Fanout Free ATPG ($C, g/v$)


- 1: initialize circuit by setting all values to X ;
 - 2: JustifyFanoutFree(C, g, \bar{v}); /* excite the fault by justifying line g to \bar{v} */
 - 3: PropagateFanoutFree(C, g); /* propagate fault-effect from g to a PO */
-

The Justify Routine

Algorithm 3 JustifyFanoutFree(C, g, v)

```
1:  $g = v$ ;  
2: if gate type of  $g ==$  primary input then  
3:   return;  
4: else if gate type of  $g ==$  AND gate then  
5:   if  $v == 1$  then  
6:     for all inputs  $h$  of  $g$  do  
7:       JustifyFanoutFree( $C, h, 1$ );  
8:     end for  
9:   else  $\{v == 0\}$   
10:     $h =$  pick one input of  $g$  whose value  $== X$ ;  
11:    JustifyFanoutFree( $C, h, 0$ );  
12:   end if  
13: else if gate type of  $g ==$  OR gate then  
14:   ...  
15: end if
```

Example

 

The recursive calls to JustifyFanoutFree():

- call #1: JustifyFanoutFree(C , g , 1)
- call #2: JustifyFanoutFree(C , a , 1)
- call #3: JustifyFanoutFree(C , f , 1)
- call #5: JustifyFanoutFree(C , c , 0)

The Propagate Routine

Algorithm 4 PropagateFanoutFree(C, g)


```
1: if  $g$  has exactly one fanout then
2:    $h =$  fanout gate of  $g$ ;
3:   if none of the inputs of  $h$  has the value of  $X$  then
4:     backtrack;
5:   end if
6: else { $g$  has more than one fanout}
7:    $h =$  pick one fanout gate of  $g$  that is unjustified;
8: end if
9: if gate type of  $h ==$  AND gate then
10:  for all inputs,  $j$ , of  $h$ , such that  $j \neq g$  do
11:    if the value on  $j == X$  then
12:      JustifyFanoutFree( $C, j, 1$ );
13:    end if
14:  end for
15: else if gate type of  $h ==$  OR gate then
16:  for all inputs,  $j$ , of  $h$ , such that  $j \neq g$  do
17:    if the value on  $j == X$  then
18:      JustifyFanoutFree( $C, j, 0$ );
19:    end if
20:  end for
21: else if gate type of  $h == \dots$  gate then
22:   ...
23: end if
24: PropagateFanoutFree( $C, h$ );
```

Week 4: Course Material

Test Generation Lecture 19

NPTEL


Example Continued

 

call #1: `PropagateFanoutFree(C, g)`
call #2: `JustifyFanoutFree(C, h, 0)`
call #3: `JustifyFanoutFree(C, b, 0)`
call #4: `PropagateFanoutFree(C, z)`

D

Algorithm


- ▷ Can handle arbitrary combinational circuits, with internal fanout structures
 - ▷ Main idea: always maintain a non-empty D-frontier and try to propagate at least a fault effect to a primary output
 - ▷ Initially, all circuit nodes are X, except for the fault site, where a fault effect (D or D-bar) is placed.
- 

D-Frontier and J-Frontier

- ▷ D-Frontier: All gates whose outputs are X but has at least one D or D-bar at the input of the gates
 - Initially, the D-frontier consists of only 1 gate (output of the fault-site)
- ▷ J-Frontier: All gates whose outputs are specified by are not justified by the input assignments


D-Frontier Example

- ▯ The D-frontier contains 2 gates

 


J-Frontier Example

- ▯ The J-Frontier contains 2 gates

 

Idea Behind D Algorithm

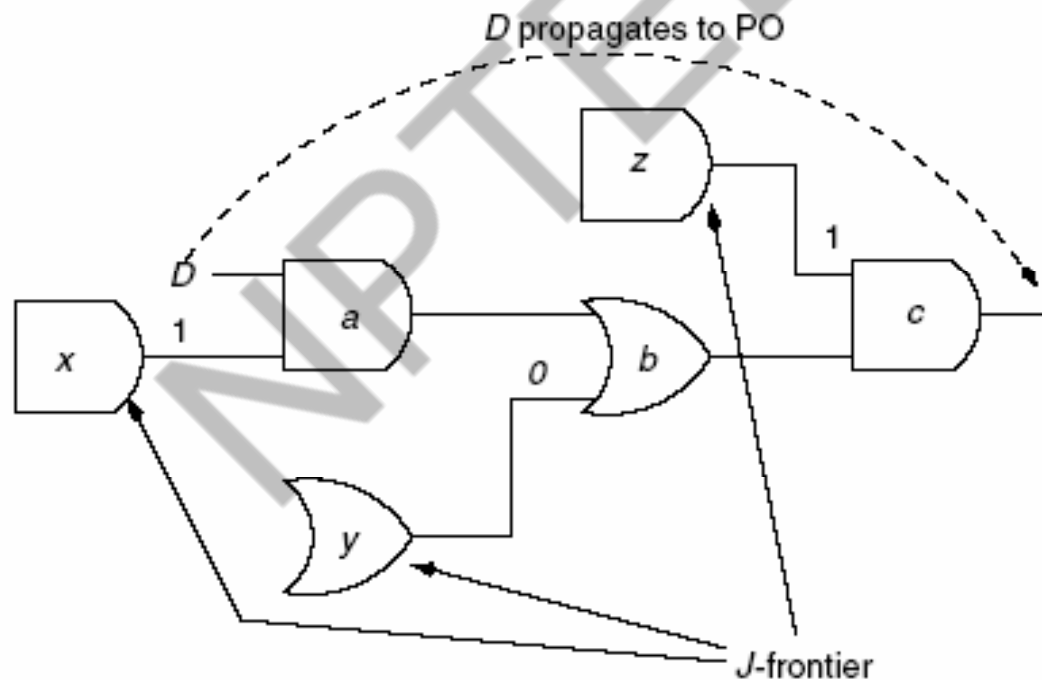- To advance the fault-effects in the D-frontier, add nodes to the J-frontier to justify



D

Algorithm

Algorithm 5 *D*-Algorithm(C, f)

```
1: initialize all gates to don't-cares;  
2: set a fault-effect ( $D$  or  $\overline{D}$ ) on line with fault  $f$  and insert it to the  $D$ -frontier;  
3:  $J$ -frontier  $= \phi$ ;  
4: result  $= D$ -Alg-Recursion( $C$ );  
5: if result == success then  
6:   print out values at the primary inputs;  
7: else  
8:   print fault  $f$  is untestable;  
9: end if
```

Algorithm 6 D-Alg-Recursion(C)

```
1: if there is a conflict in any assignment or  $D$ -frontier is  $\emptyset$  then
2:   return failure;
3: end if
4: /* first propagate the fault-effect to a PO */
5: if no fault-effect has reached a PO then
6:   while not all gates in  $D$ -frontier has been tried do
7:      $g$  = a gate in  $D$ -frontier that has not been tried;
8:     set all unassigned inputs of  $g$  to non-controlling value and add them to the  $J$ -frontier;
9:      $result = D\text{-Alg-Recursion}(C)$ ;
10:    if  $result == success$  then
11:      return (success);
12:    end if
13:  end while
14:  return (failure);
15: end if {fault-effect has reached at least one PO}
16: if  $J$ -frontier is  $\emptyset$  then
17:   return (success);
18: end if
19:  $g$  = a gate in  $J$ -frontier;
20: while  $g$  has not been justified do
21:    $j$  = an unassigned input of  $g$ ;
22:   set  $j = 1$  and insert  $j = 1$  to  $J$ -frontier;
23:    $result = D\text{-Alg-Recursion}(C)$ ;
24:   if  $result == success$  then
25:     return (success);
26:   else try the other assignment
27:     set  $j = 0$ ;
28:   end if
29: end while
30: return(failure);
```

D Algorithm Example

Target f stuck-at-0

Initialize all gates to X

Places D on line f

Propagate fault effect to z

Places $a=1$ in J-frontier, followed by
 $h=0$

Fault effect has reached primary output


Try to justify entries in J-frontier

a is already justified as it is primary input


For $f=D$, $d=0$, making $c=0$

For $h=0$, either $e=0$ or $b=0$ is sufficient

Test found.

 


D Algorithm Example

 

- ▷ Target fault: *g/1*
- ▷ Initially, D-Frontier: {*h*}, J-Frontier={*g=D-bar*}
- ▷ To advance D-frontier, add *f=1* and *c=1* to J-frontier

D Algorithm Example (Cont.)

 


- Now justify every value in J-Frontier via branch-and-bound search
 - Must not make D-frontier empty or conflict with other J-frontier values
 - Otherwise backtrack
- Result: *g/1* is unstable

PODE M

- ▷ Also a branch-and-bound search
- ▷ Decisions only on PIs
 - No J-Frontier needed
 - No internal conflicts
- ▷ D-frontier may still become empty
 - Backtrack whenever D-frontier becomes empty
 - Backtrack also when no X-path exists from any $D/D\text{-bar}$ to a PO
- ▷ Decisions selected based on a backtrack from the current objective

X- Path

 - The D in the circuit has no path of X's to any PO
 - i.e., the D is blocked by every path to any PO



Getting the Objective

Algorithm 9 getObjectiv(C)

```
1: if fault is not excited then
2:   return ( $g, \bar{v}$ );
3: end if
4:  $d$  = a gate in  $D$ -frontier;
5:  $g$  = an input of  $d$  whose value is  $x$ ;
6:  $v$  = non-controlling value of  $d$ ;
7: return ( $g, v$ );
```

Backtrace to Select a Decision

Algorithm 10 backtrace(C)

```
1:  $i = g$ ;  
2:  $\text{num\_inversion} = 0$ ;  
3: while  $i \neq$  primary input do  
4:    $i =$  an input of  $i$  whose value is  $x$ ;  
5:   if  $i$  is an inverted gate type then  
6:      $\text{num\_inversion}++$ ;  
7:   end if  
8: end while  
9: if  $\text{num\_inversion} == \text{odd}$  then  
10:   $v = \bar{v}$ ;  
11: end if  
12: return( $i, v$ );
```


Week 4: Course Material

Test Generation Lecture 20

NPTEL

PODEM


Example

 

- D 1st Objective: *f*=1 in order to excite the target fault
- D Backtrace from the object: *c*=0
- D Simulate(*c*=0): D-Frontier = {*g*}, some gates have been assigned {*c*=*d*=*e*=*h*=0, *f*=D}
- D 2nd Objective: advance D-frontier, *a*=1
- D Backtrace from the object: *a*=1
- D Simulate(*a*=0): Fault detected at *z*

Another PODEM

Example

 

Target fault: b/0

- ▷ 1st Objective: excite fault: $b=1$
- ▷ Backtrace from objective: $a=0$
- ▷ Simulate($a=0$): $b=D$, $c=0$, $d=0$: empty D-frontier.
Must backtrack
- ▷ Change decision to $a=1$
- ▷ Simulate($a=1$): $b=0$, $c=1$, $d=1$, D-frontier still empty
- ▷ Backtrack, no more decisions. Fault untestable.

FAN


- ▷ Extend PODEM for an improved ATPG
- ▷ Concept of headlines to reduce the number decisions
- ▷ Multiple Objectives to reduce later conflicts

Headline


S

- Output signals of fanout-free cones
- Any value on headlines can always be justified by the PIs

 ***We only need to
backtrace to the
headlines to
reduce the
number of
decisions***



Multiple Objectives

 


- ▮ Objectives: $\{k=0, m=1\}$
- ▮ Backtrace from $k=0$ may favor $b=0$, but $\text{simulate}(b=0)$ would violate the second objective $m=1$!
- ▮ Makes backtrace more intelligent to avoid future conflicts

Static Logic Implications

- ▮ Can help ATPG make better decisions
- ▮ Avoid conflicts
- ▮ Reduce the number of backtracks
- ▮ Idea: what is the effect of asserting a logic value to a gate on other gates in the circuit?

Direct Implications

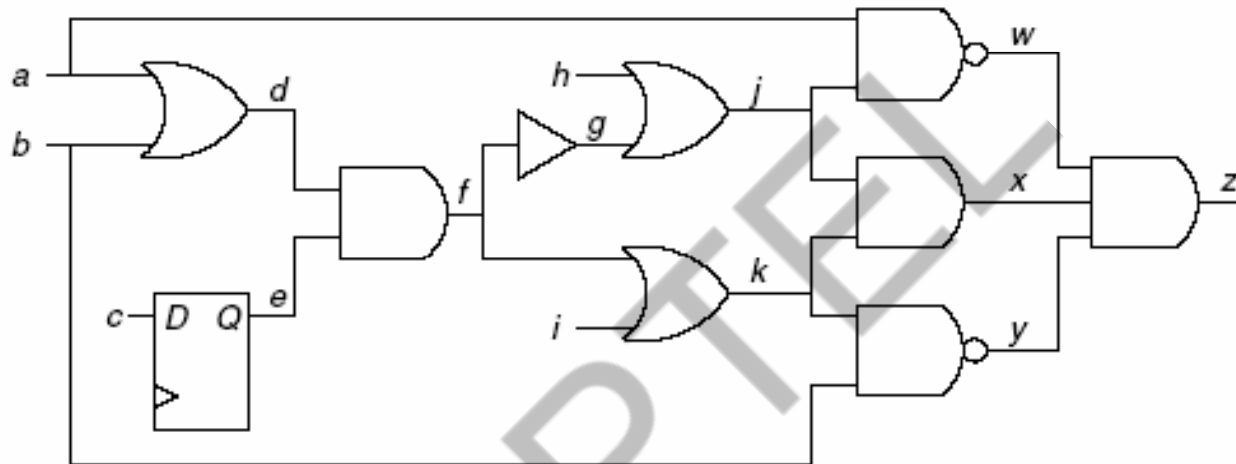


□ Direct implications for $f=1$:

- $\{d=1, e=1, g=1, j=1, k=1\}$

□ Direct implications for $j=0$:


- $\{h=0, g=0, f=0, w=1, w=0, z=0\}$

Indirect Implications

 

- ▷ Direct implications for $f=1$:
 - $\{d=1, e=1, g=1, j=1, k=1\}$
- ▷ Indirect Implications for $f=1$ obtained by simulating the direct implications of $f=1$:
 - $\{x=1\}$
- ▷ This is repeated for every node in the circuit


Extended Backward Implications

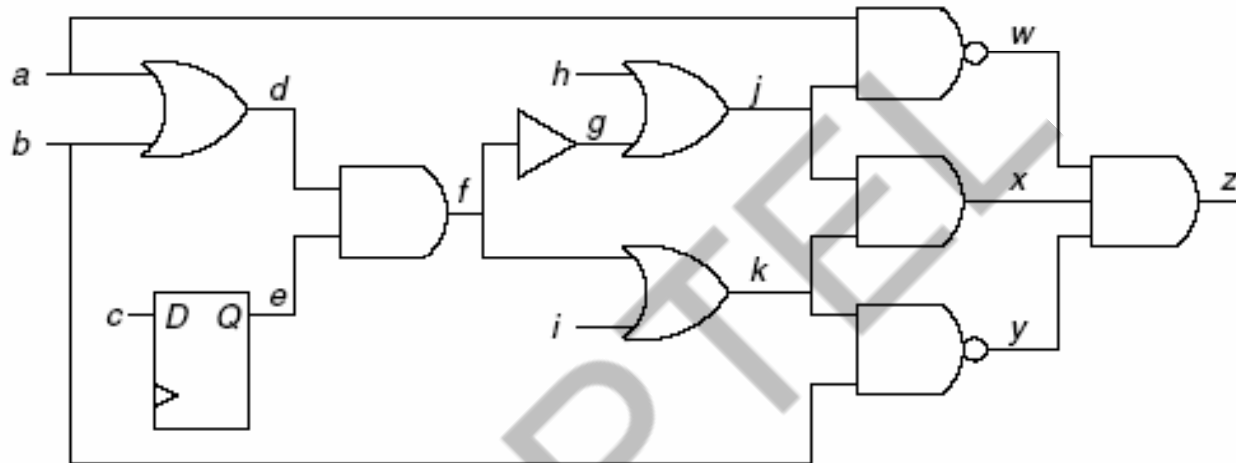

- ▷ Direct and indirect implications for $f=1$:
 - $\{d=1, e=1, g=1, j=1, k=1, x=1\}$
- ▷ Ext. Back. Implications obtained by enumerating cases for unjustified gates
 - Unjustified gates: $\{d=1\}$

Extended Backward


Implications

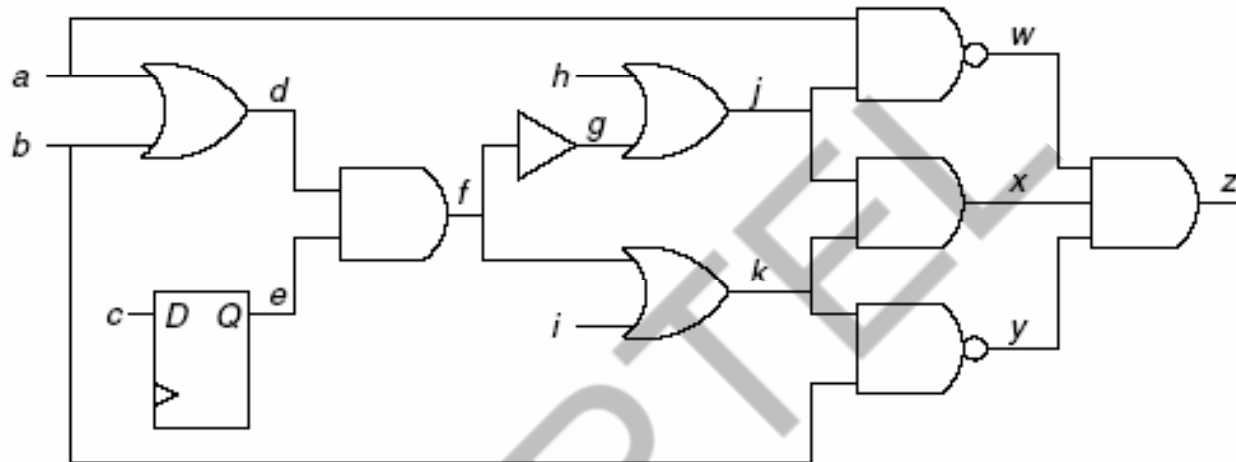

- D In order to justify $d=1$, need either $a=1$ or $b=1$
 - $\text{Simulate}(a=1, \text{impl}(f=1)) = S_a$
 - $\text{Simulate}(b=1, \text{impl}(f=1)) = S_b$
- D Intersection of S_a and S_b is the the set of ext. back. Implications for $f=1$
 - $f=1$ implies $\{z=0\}$
- D This is repeated for every unjustified gate, as well as for every node in the circuit

Dynamic Logic Implications

 
- ▷ Similar to Static Logic Implications, but has some signals already assigned values
- ▷ Suppose $c=1$ has already been assigned
 - Then to obtain $z=0$, b must be 0
 - This is the intersection of having either $d=0$ or $e=0$ in the presence of $c=1$



Another Dynamic Implications

 
Example

- Suppose $b=D$
- In order to propagate the fault-effect to z , $f = 1$ is a necessary condition [Akers 76, Fujiwara 83]
- To take this further, the intersection of all the necessary assignments for all fault-effects in the D-frontier can be taken [Hamzaoglu99]



Evaluation Frontiers

 - If two faults have the same E-frontier with at least one fault-effect, then the values on the unassigned PIs can be the same [Giraldi 90]




Fast Untestable Fault Identification

- ▷ Untestable faults are:
 - Those that could not be excited, or
 - Those that could not be propagated, or
 - Those that could not be **simultaneously** excited or propagated
- ▷ ATPG can spend a lot of time trying to generate a test for an untestable fault
 - Fast identification of untestable faults can allow the ATPG to skip those faults

FIRE [Iyer 1996]

- D Based on conflict analysis
- D S_0 = set of faults that are untestable when signal $s=0$
 - These faults must require $s=1$ to be detectable
- D S_1 = set of faults that are untestable when signal $s=1$
 - These faults must require $s=0$ to be detectable
- D Intersection of S_0 and S_1 are definitely untestable
 - They require $s=1$ and $s=0$ simultaneously to be detectable!


FIRE Example

 

- D $\text{Impl}[b=1] = \{b=1, b1=1, b2=1, d=1, x=0, z=0\}$
- D Faults unexcitable when $b=1$: $\{b/1, b1/1, b2/1, d/1, x/0, z/0\}$
- D Faults unobservable when $b=1$: $\{a/0, a/1, e1/0, e1/1, y/0, y/1, e2/0, e2/1\}$
- D Faults undetectable when $b=1$: $\{a/0, a/1, b/1, b1/1, b2/1, d/1, e1/0, e1/1, e2/0, e2/1, x/0, y/0, y/1, z/0\}$

FIRE Example


(Cont.)

 

- ▷ $\text{Impl}[b=0] = \{b=0, b1=0, b2=0, e=0, e1=0, e2=0, y=1\}$
- ▷ Faults unexcitable when $b=0$: $\{b/0, b1/0, b2/0, e/0, e1/0, e2/0, y/1\}$
- ▷ Faults unobservable when $b=0$: $\{c/0, c/1\}$
- ▷ Faults undetectable when $b=0$: $\{b/0, b1/0, b2/0, c/0, c/1, e1/0, e2/0, y/1\}$

FIRE Example

(Cont.)

 

- ▷ Now that the two sets of faults undetectable when $b=0$ and $b=1$ have been computed
- ▷ The intersection of the two sets are those faults the require $b=1$ AND $b=0$ for detection, thus untestable:
 - $\{b_2/0, c/0, c/1, e/0, e_1/0, e_2/0, y/1\}$

Week 4: Course Material


Test Generation Lecture 21

NPTEL

Generalization of FIRE

- ▷ Conflict on a single line: $b=0$ AND $b=1$
- ▷ Conflict on any illegal combination
 - Suppose FFs $x=1$, $y=0$, $z=1$ is illegal, then any fault that require $x=1$, $y=0$, and $z=1$ for detection will be untestable
 - This can be generalized to any illegal value combination in the circuit


Multi-Line Conflict

 

- D Consider the AND gate
- D $\{a=0, c=1\}$ is illegal (but this is captured by single-line conflicts)
- D Likewise $\{b=0, c=1\}$
- D But, $\{a=1, b=1, c=0\}$ is a multi-line conflict not captured by single-line conflict
 - S_0 —Set of faults not detectable when signal $a = 0$.
 - S_1 —Set of faults not detectable when signal $b = 0$.
 - S_2 —Set of faults not detectable when signal $c = 1$.


Intersection of S_0 , S_1 , S_2 will be untestable faults due to this multi-line conflict

Multi-Line Conflicts (Cont.)

 

- ▮ Can extend the previous concept further
- ▮ Consider multi-line conflict $\{h=1, g=1, z=0\}$
- ▮ We can extend these values as far as possible: $\{f=1, c=1, d=0, e=0, z=0\}$ is a multi-line conflict as well

Summary on Untestable Fault Identification

- ▷ First compute static logic implications
 - ▷ Compute untestable faults based on single-line conflicts
 - ▷ Compute untestable faults based on multi-line conflicts
 - ▷ Remove all identified untestable faults from the fault list
- 

Simulation-Based ATPG


- Random and weighted-random TPG are the simplest forms of simulation-based ATPG
- Challenge: how to guide the search to generate effective vectors to obtain high fault coverage, low computation costs, and small test sets?

Genetic Algorithms for Sim-based *ATPG*

▷ A GA made up of

- A population of individuals (chromosomes)
 - Each individual is a candidate solution
- Each individual has an associated fitness
 - Fitness measures the quality of the individual
- Genetic operators to evolve from one generation to the next
 - Selection, crossover, mutation

Illustration of GA process

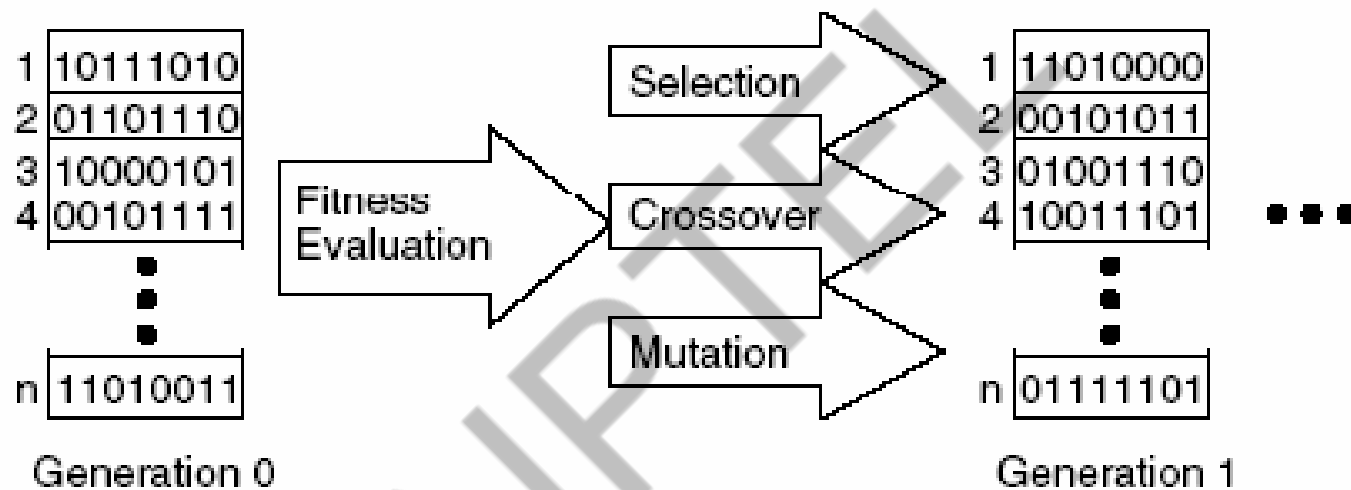


Pseudo Code for

Algorithm 13 Simple_GA_ATPG

```
1: test set  $T = \emptyset$ ;  
2: while there is improvement do  
3:   initialize a random GA currentPopulation;  
4:   compute fitness of currentPopulation;  
5:   for  $i = 1$  to maxGenerations do  
6:     add the best individual to test set  $T$ ;  
7:     nextPopulation =  $\emptyset$ ;  
8:     for  $j = 1$  to populationSize/2 do  
9:       select  $parent_1$  and  $parent_2$  from currentPopulation;  
10:      crossover( $parent_1, parent_2, child_1, child_2$ );  
11:      mutate( $child_1$ );  
12:      mutate( $child_2$ );  
13:      place  $child_1$  and  $child_2$  to nextPopulation;  
14:    end for  
15:    compute fitness of nextPopulation;  
16:    currentPopulation = nextPopulation;  
17:  end for  
18: end while
```

The Selection Operator

▷ Roulette Wheel Selection

 

▷ Tournament Selection

The Crossover Operator

D One-point crossover

Parent #1	110011001100	110011001100
Parent #2	101010101010	101010101010
Child #1	110011001100	101010101010
Child #2	101010101010	110011001100

D Two-point crossover

Parent #1	11001100	11001100	11001100
Parent #2	10101010	10101010	10101010
Child #1	11001100	10101010	11001100
Child #2	10101010	11001100	10101010

Uniform Crossover

- The crossover is performed whenever a mask bit is set

Mask	010011100100010011110101
Parent #1	110011001100110011001100
Parent #2	101010101010101010101010
Child #1	100010101000100010101000
Child #2	111011001110111011001110

The Mutation Operator

- ▷ Random flip of a bit position
- ▷ Need to keep mutation rate small, so that the search will not seem randomized

GA Population Size

- ▷ Should be a function of the individual size
- ▷ Larger individuals require larger populations to allow for reasonable diversity
- ▷ Individual size depends on the number of PIs in the circuit
 - In sequential circuits, an individual may be a sequence of vectors
- ▷ Generation Gap: some individuals may be carried over from one generation to the next

Number of GA Generations

D Related to the population size

- Larger populations usually demand more generations
- Generation gap also will affect the number of generations needed to reach a satisfactory solution

The Fitness Function

- ▯ Measures the quality of the individual
- ▯ Essential for a GA to converge on a solution
- ▯ Example fitness functions:
 - Number of faults detected by the individual
 - Number of faults excited by the individual
 - Number of flip-flops set to a specified value (in seq ckts)
 - A weighted sum of various factors