

# Week 3: Course Material

## Logic and Fault Simulation

### Lecture 11




# *Logic and Fault Simulation*

- D **Introduction**
- D Simulation models
- D Logic simulation
- D Fault simulation
- D Concluding remarks
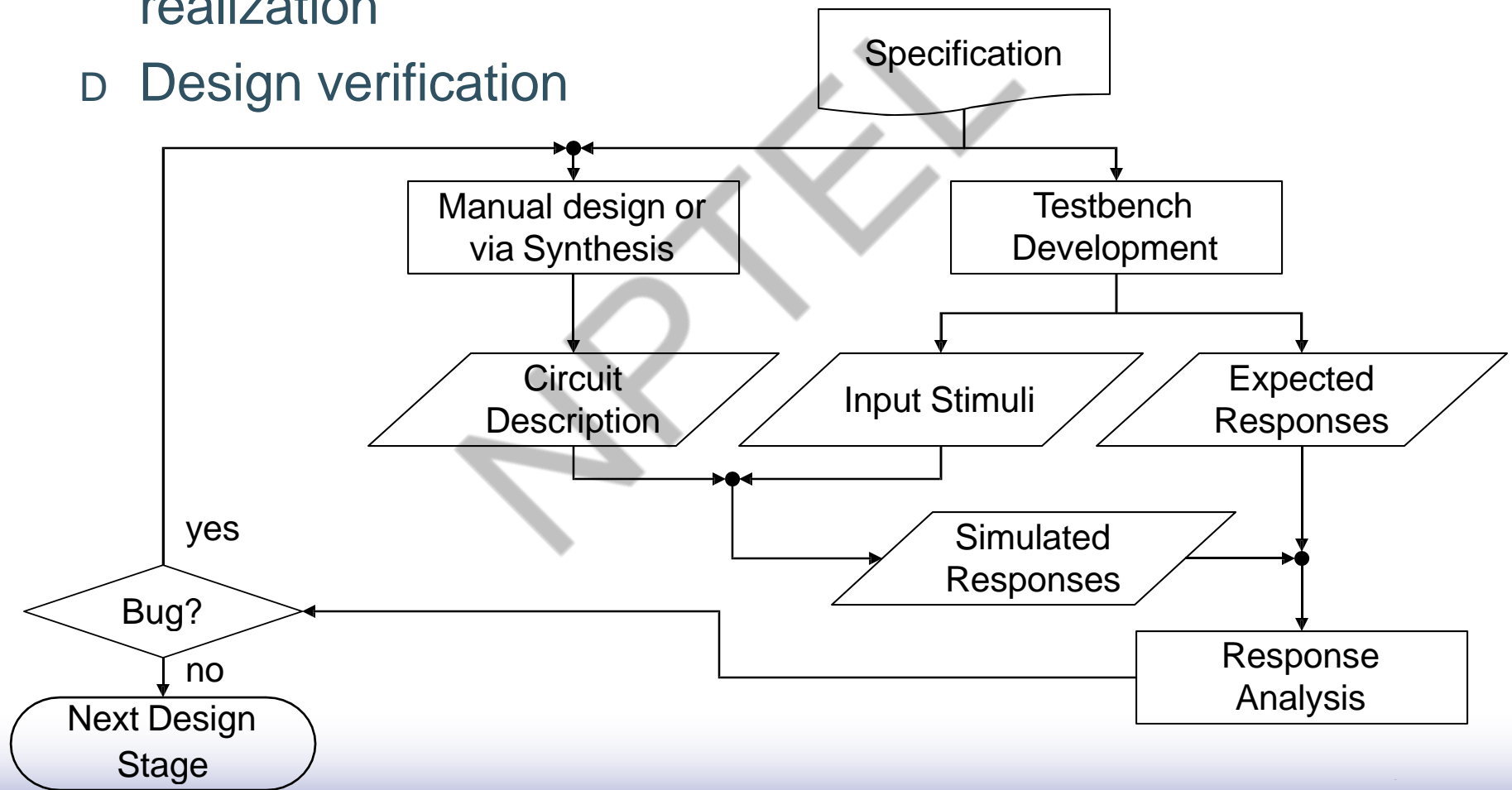
# Logic Simulation

- ▷ Predict the behavior of a design prior to its physical realization
- ▷ Design verification



# *Fault Simulation*


- ▯ Predicts the behavior of faulty circuits
  - As a consequence of inevitable fabrication process imperfections
- ▯ An important tool for test and diagnosis
  - Estimate fault coverage
  - Fault simulator
  - Test compaction
  - Fault diagnosis

# *Logic and Fault Simulation*

- D Introduction
- D **Simulation models**
- D Logic simulation
- D Fault simulation
- D Concluding remarks

## Gate-Level Network

D The interconnections of logic gates

 

# Sequential Circuits


- ▯ The outputs depend on both the current and past input values

$x_i$ : primary input (PI)



$z_i$ : primary output (PO)

$y_i$ : pseudo primary input (PPI)

$Y_i$ : pseudo primary output (PPO)

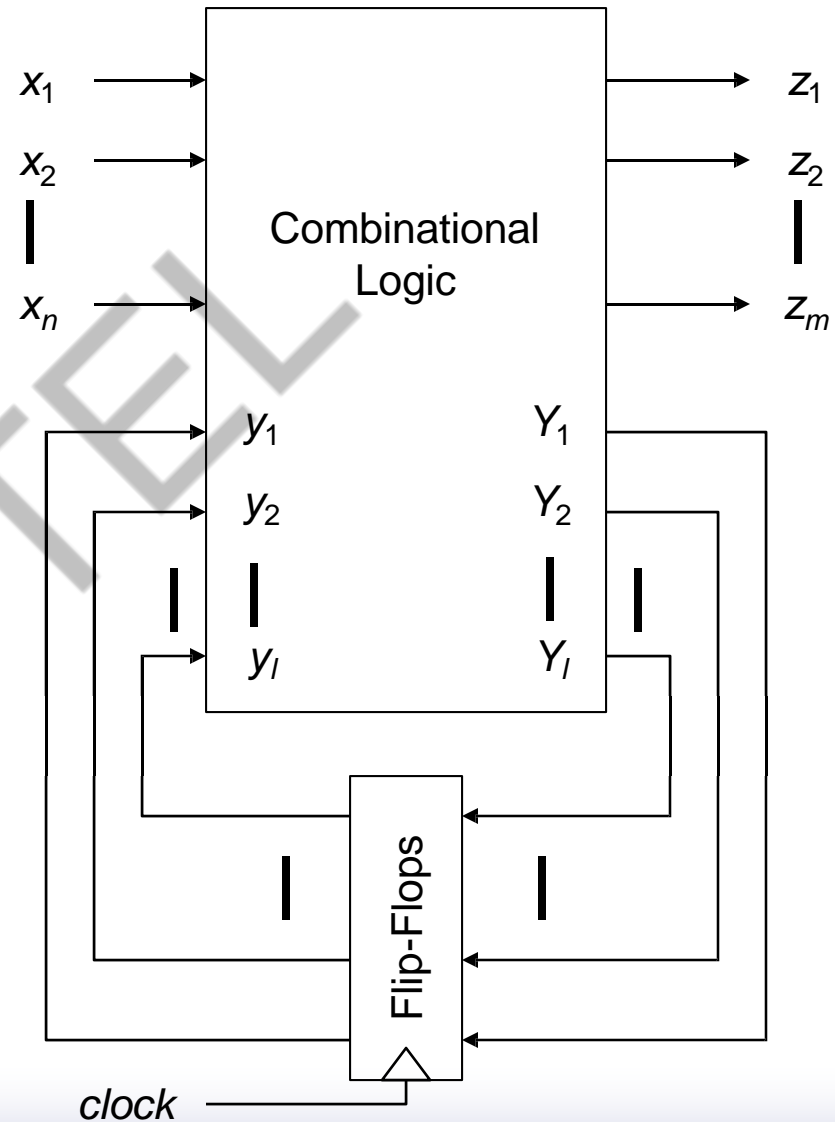

# *A Positive Edge-Triggered D-FF*

  



## *Logic Symbols*

D The most commonly used are 0, 1,  $u$  and  $Z$

D 1 and 0

- *true* and *false* of the two-value Boolean algebra

D  $u$

- Unknown logic state (maybe 1 or 0)

D  $Z$

- High-impedance state
- Not connected to  $V_{dd}$  or ground

# *Ternary Logic*

▷ Three logic symbols: 0, 1, and  $u$


AND	0	1	$u$
0	0	0	0
1	0	1	$u$
$u$	0	$u$	$u$

OR	0	1	$u$
0	0	1	$u$
1	1	1	1
$u$	$u$	1	$u$

NOT	0	1	$u$
	1	0	$u$

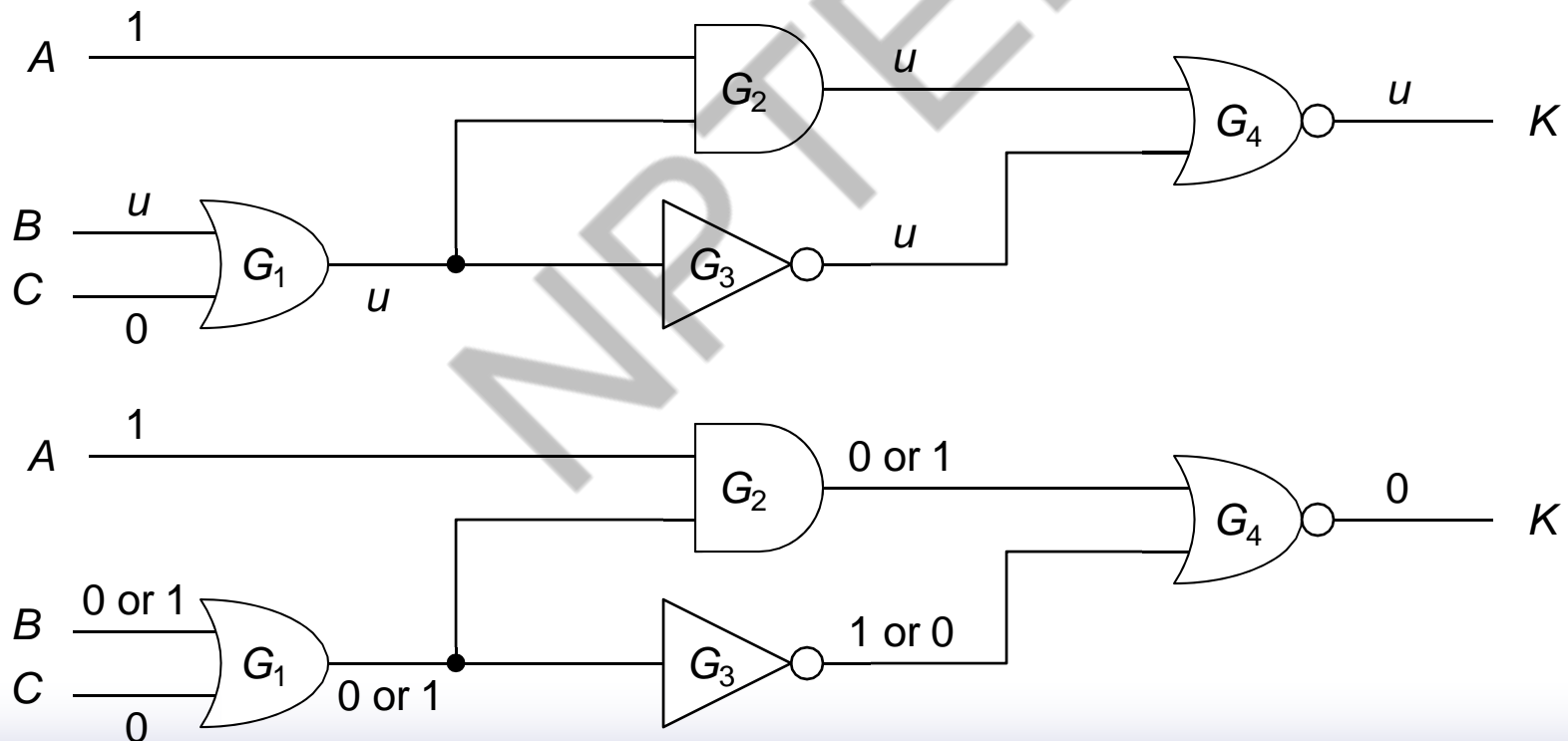
## *Information Loss of Ternary Logic*

- Simulation based on ternary logic is pessimistic
- A signal may be reported as unknown when its value can be uniquely determined as 0 or 1


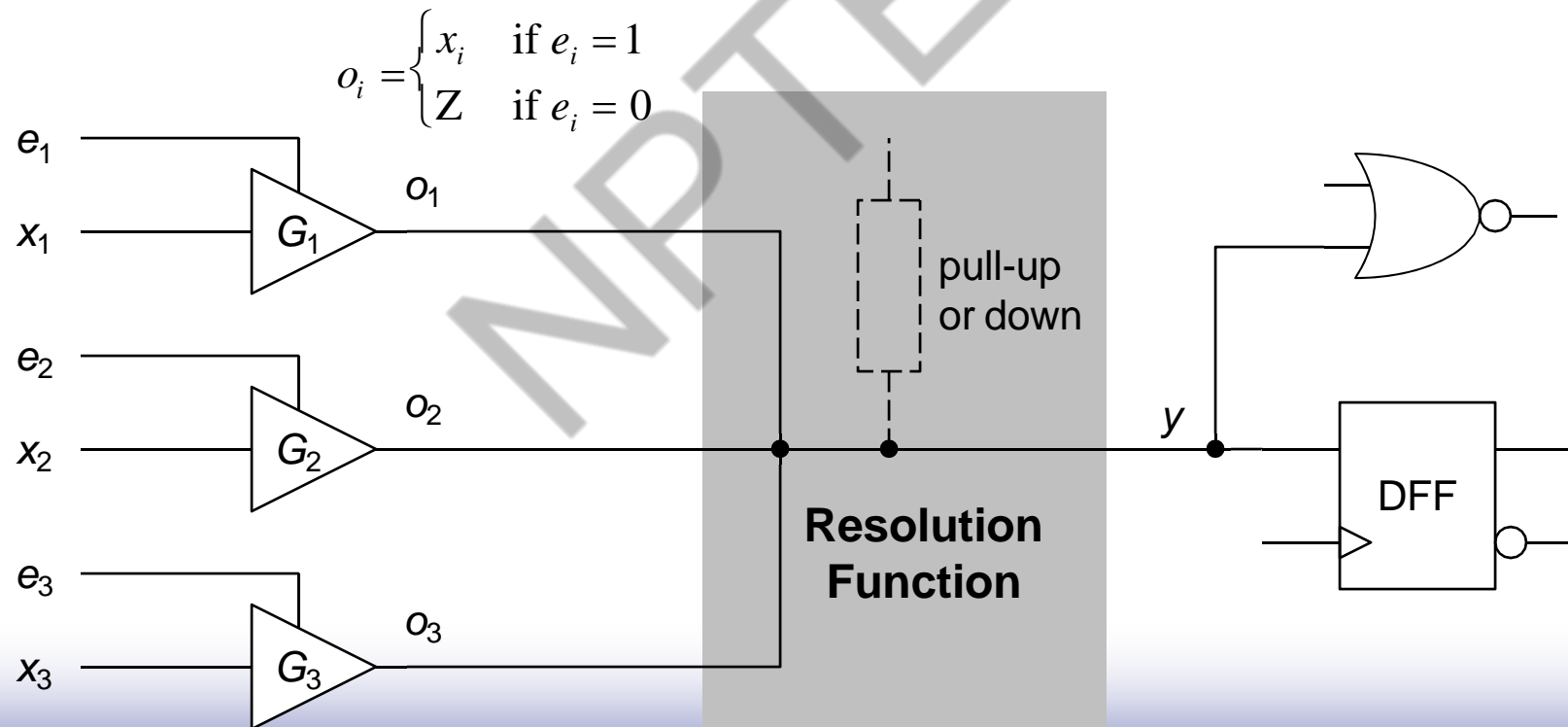
## High-Impedance State Z

- Tri-state gates permit several gates to time-share a common wire, called bus
- A signal is in high-impedance state if it is connected to neither  $V_{dd}$  nor ground



## *Resolving Bus Conflict*

- ▯ Bus conflict occurs if at least two drivers drive the bus to opposite binary values
- ▯ To simulate tri-state bus behavior, one may insert a resolution function for each bus wire
  - May report only the occurrence of bus conflict
  - May utilize multi-valued logic to represent intermediate logic states (including logic signal values and strengths)

# *Logic Element Evaluation Methods*

## ▮ Choice of evaluation technique depends on

- Considered logic symbols
- Types and models of logic elements

## ▮ Commonly used approaches

- Truth table based
- Input scanning
- Input counting
- Parallel gate evaluation

## *Truth Table Based Gate Evaluation*

- ▷ The most straightforward and easy to implement
  - For binary logic,  $2^n$  entries for  $n$ -input logic element
  - May use the input value as table index
  - Table size increases exponentially with the number of inputs
- ▷ Could be inefficient for multi-valued logic
  - A  $k$ -symbol logic system requires a table of  $2^{mn}$  entries for an  $n$ -input logic element
    - $m = \lceil \log_2 k \rceil$
    - Table indexed by  $mn$ -bit words

## Input Scanning


- ▯ The gate output can be determined by the types of inputs
- If any of the inputs is the controlling value, the gate output is  $c \oplus i$
  - Otherwise, if any of the inputs is  $u$ , the gate output is  $u$
  - Otherwise, the gate output is  $c' \oplus i$

Table 3.2: The  $c$  (controlling) and  $i$  (inversion) values of basic gates

	$c$	$i$
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1



## *Input Scanning - cont'd*

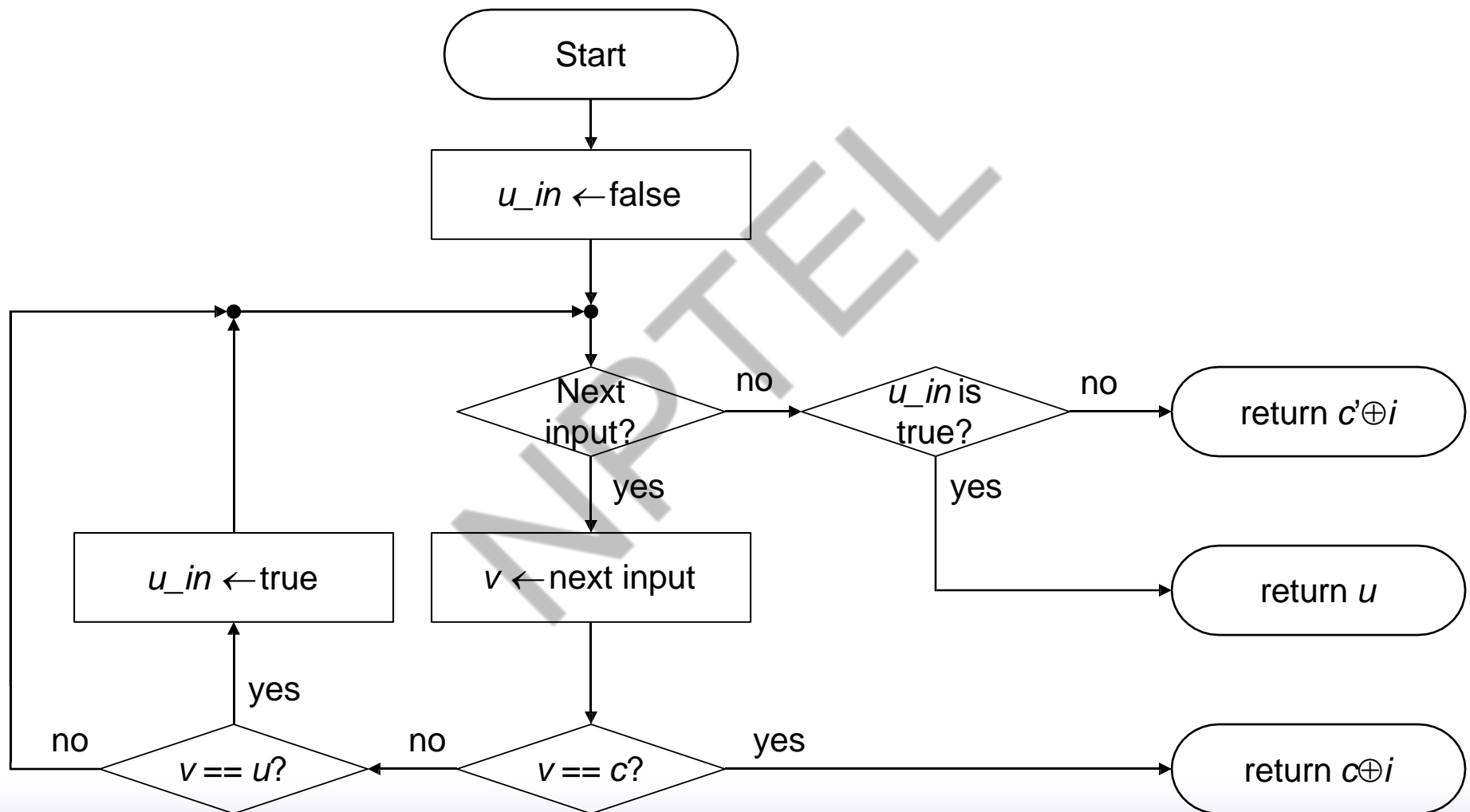


## *Input Counting*

- ▷ Keep the counts of controlling and unknown inputs
  - *c\_count*: the number of controlling inputs
  - *u\_count*: the number of unknown inputs
- ▷ Update counts during logic simulation
  - Example:  
One input of a NAND switches from 0 to *u*
    - *c\_count* --
    - *u\_count* ++
- ▷ Same rules as input scanning used to evaluate gate outputs
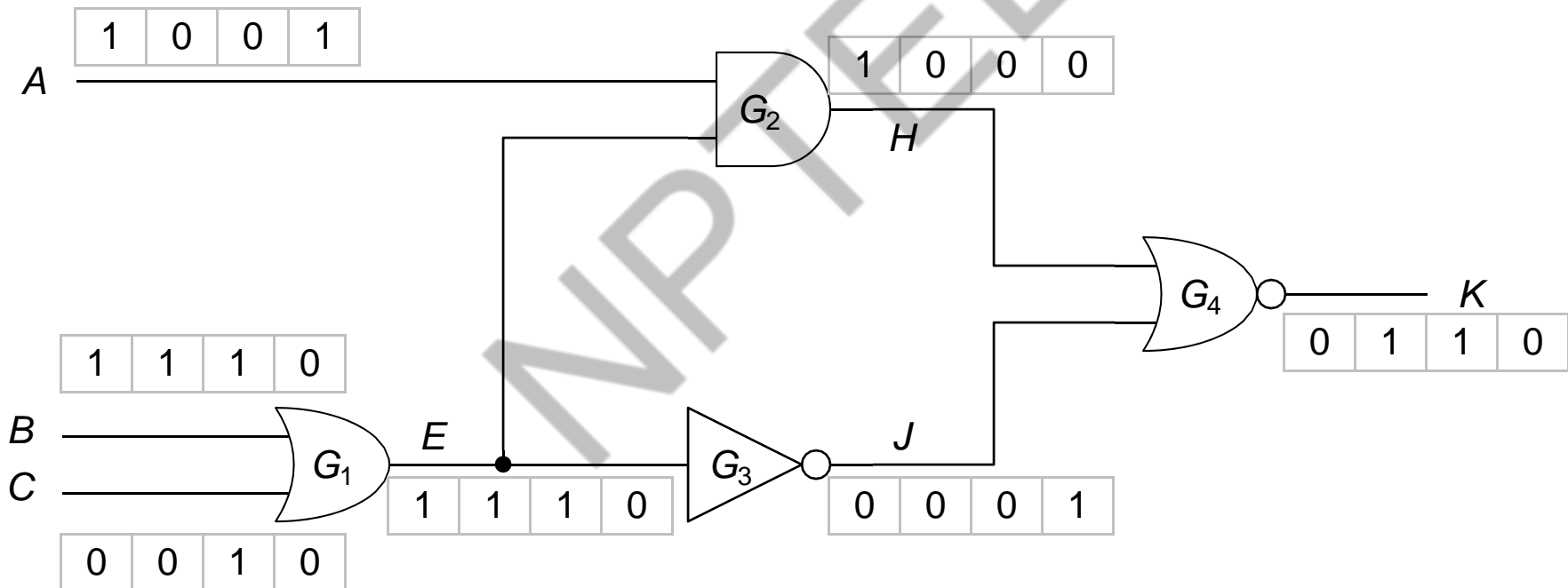
## Parallel Gate Evaluation

- Exploit the inherent concurrency in the host computer
  - A 32-bit computer can perform 32 logic operations in parallel



# *Logic and Fault Simulation (contd.)*

## *Lecture 12*

NPTEL

# *Multi-Valued Parallel Gate Evaluation*

## ▷ Use ternary logic as example


- Assume
  - $w$ -bit wide word
  - Symbol encoding:  $v_0 = (00)$ ,  $v_1 = (11)$ ,  $v_u = (01)$
- Associate with each signal  $X$  two words,  $X_1$  and  $X_2$ 
  - $X_1$  stores the first bits and  $X_2$  the second bits of the  $w$  copies of the same signal
- AND and OR operations are realized by applying the same bitwise operations to both words
  - $C = \text{OR}(A, B) \implies C_1 = \text{OR}(A_1, B_1)$  and  $C_2 = \text{OR}(A_2, B_2)$
- Complement requires inversion
  - $C = \text{NOT}(A) \implies C_1 = \text{NOT}(A_2)$  and  $C_2 = \text{NOT}(A_1)$

## *Timing Models*

- Transport delay
- Inertial delay
- Wire delay
- Function element delay model

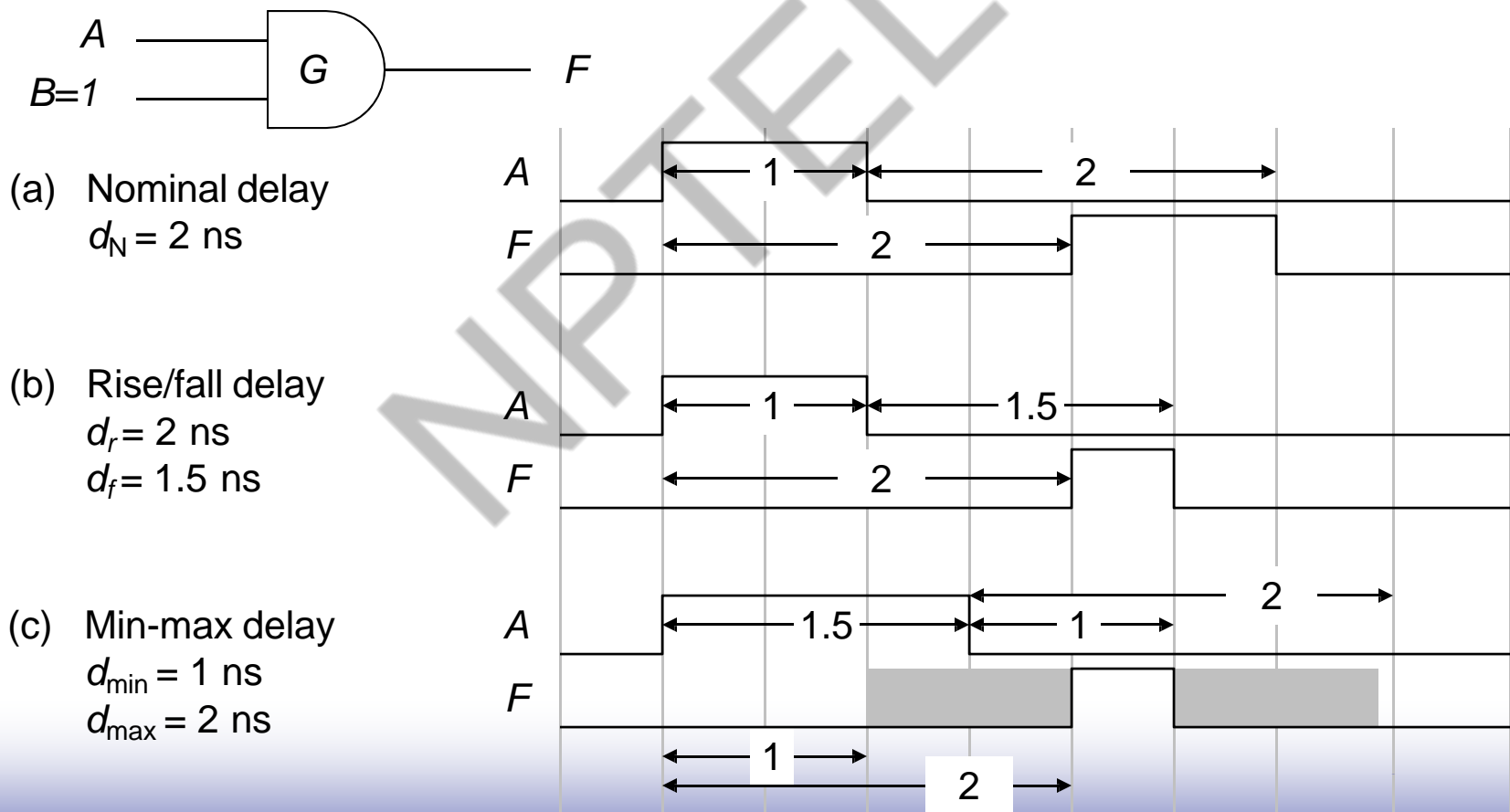
# Transport Delay

- D The time duration it takes for the effect of gate input changes to appear at gate outputs


 
## Inertial Delay


- D The minimum input pulse duration necessary for the output to switch states



(a) Pulse duration less than  $d_I$




(b) Pulse duration longer than  $d_I$

 


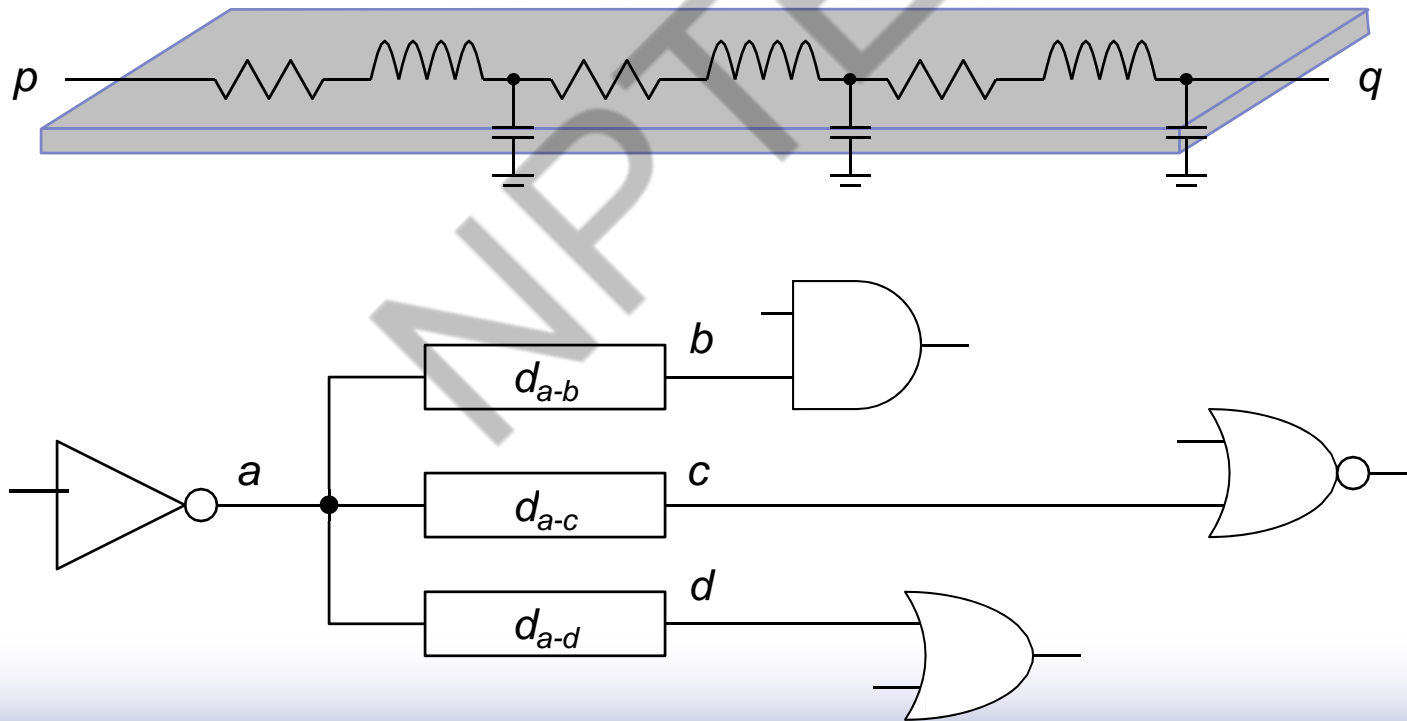
## Wire Delay

- Wires are inherently resistive and capacitive
- It takes finite time for a signal to propagate along a wire



## Functional Element Delay Model

- For more complicated functional elements like flip-flops

Table 3.3: The D flip-flop I/O delay model

Input condition				Present state	Outputs		Delays (ns)		Comments
$D$	$Clock$	$Preset\bar{B}$	$Clear\bar{B}$	$q$	$Q$	$Q\bar{B}$	to $Q$	to $Q\bar{B}$	
$X$	$X$	$\downarrow$	0	0	$\uparrow$	$\downarrow$	1.6	1.8	Asynchronous preset
$X$	$X$	0	$\downarrow$	1	$\downarrow$	$\uparrow$	1.8	1.6	Asynchronous clear
1	$\uparrow$	0	0	0	$\uparrow$	$\downarrow$	2	3	$Q: 0 \rightarrow 1$
0	$\uparrow$	0	0	1	$\downarrow$	$\uparrow$	3	2	$Q: 1 \rightarrow 0$


$X$  indicates don't care

# *Logic and Fault Simulation*


- D Introduction
- D Simulation models
- D **Logic simulation**
- D Fault simulation
- D Concluding remarks
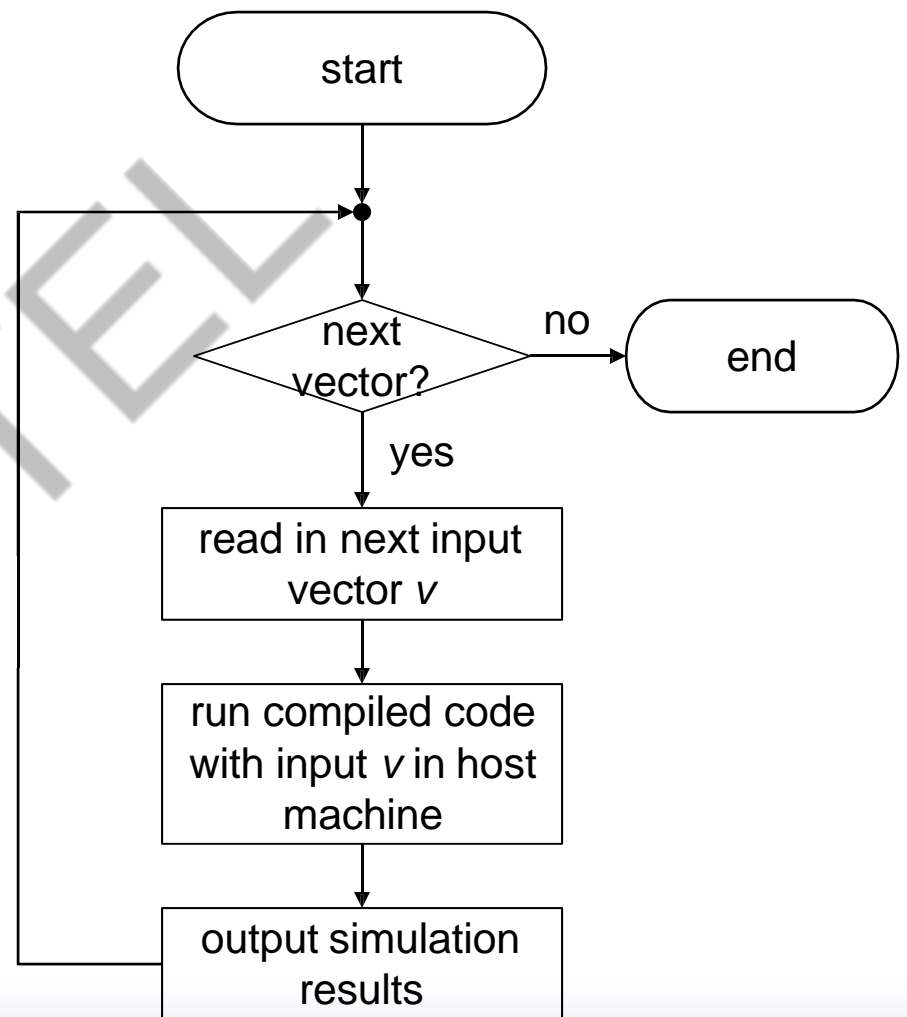
# *Compiled Code Simulation*

- Translate the logic network into a series of machine instructions that model the gate functions and interconnections




# *Compiled Code Generation Flow*

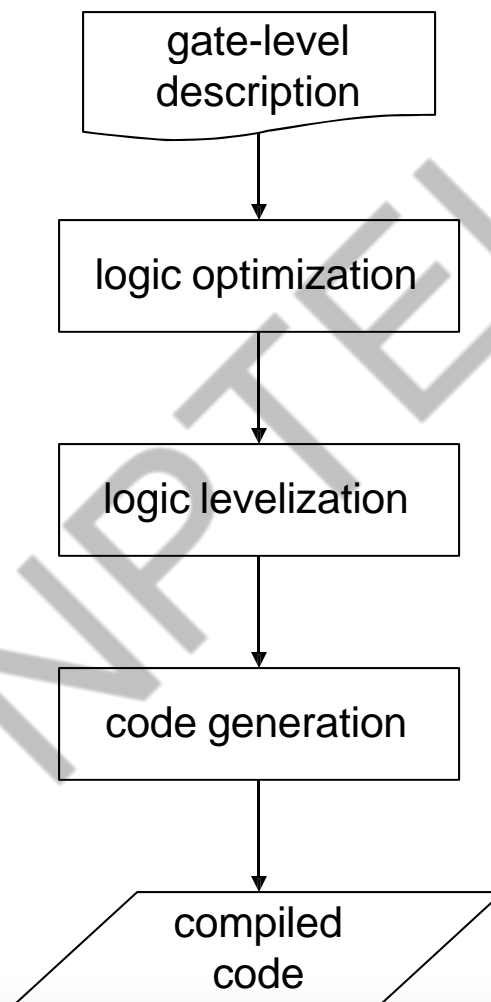


# Logic Optimization

## D Enhance the simulation efficiency

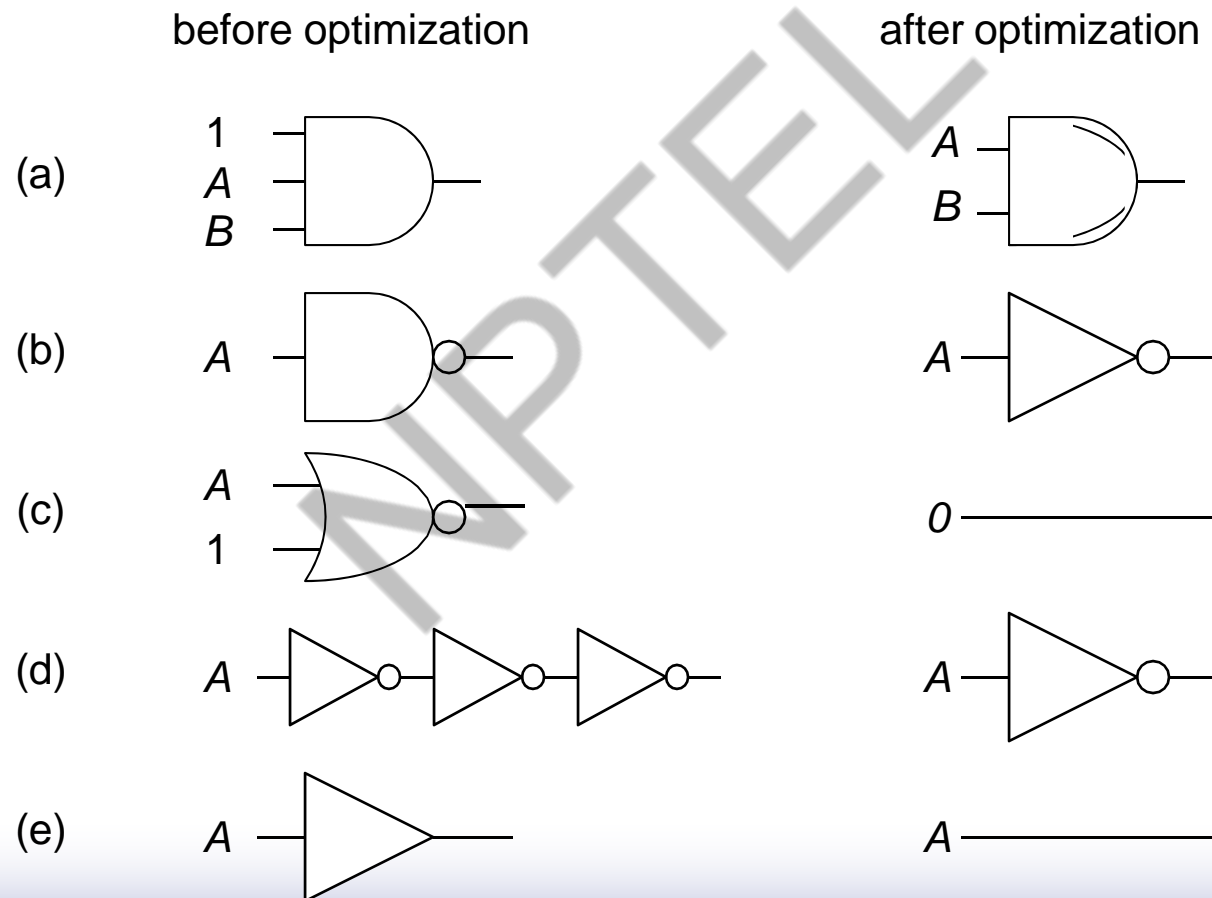
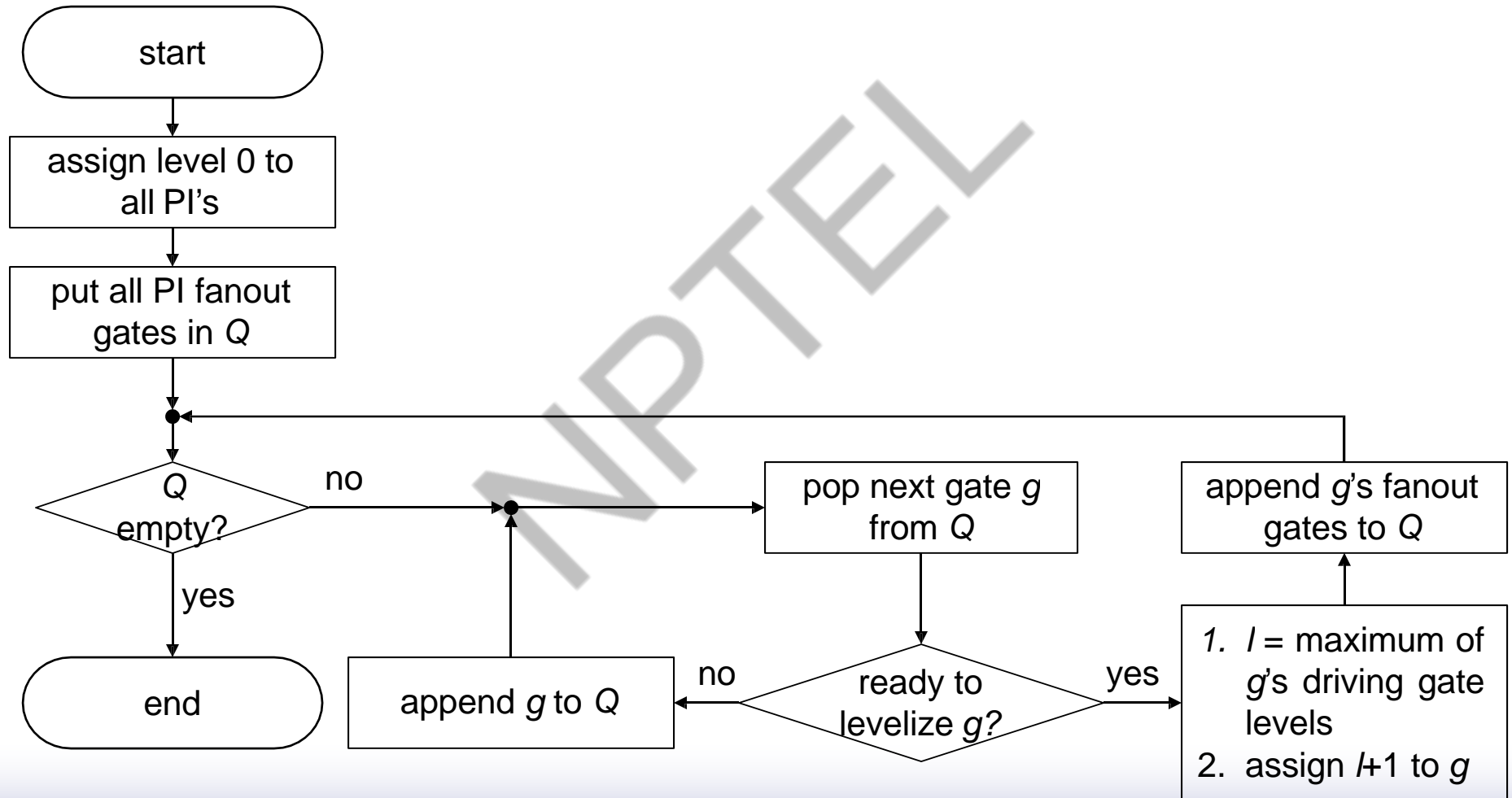
# Logic Levelization

▷ Determine the order of gate evaluations



## Exempl

 


Table 3.4: The levelization process of circuit

step	A	B	C	$G_1$	$G_2$	$G_3$	$G_4$	$Q$
0	0	0	0					$\langle G_2, G_1 \rangle$
1	0	0	0					$\langle G_1, G_2 \rangle$
2	0	0	0	1				$\langle G_2, G_3 \rangle$
3	0	0	0	1	2			$\langle G_3, G_4 \rangle$
4	0	0	0	1	2	2		$\langle G_4 \rangle$
5	0	0	0	1	2	2	3	$\langle \rangle$

D The following orders are produced

- $G_1 \Rightarrow G_2 \Rightarrow G_3 \Rightarrow G_4$
- $G_1 \Rightarrow G_3 \Rightarrow G_2 \Rightarrow G_4$



# *Code Generation*

- ▮ High-level programming language source code
  - Easier to debug
  - Can be ported to any target machine that has the compiler
  - Limited in applications due to long compilation times
- ▮ Native machine code
  - Generate the target machine code directly
  - Higher simulation efficiency
  - Not as portable

## *Code Generation - cont'd*

### ▮ Interpreted code


- The target machine is a software emulator
- The codes are interpreted and executed one at a time
- Best portability and maintainability
- Reduced performance

# *Logic and Fault Simulation (contd.)*

## *Lecture 13*

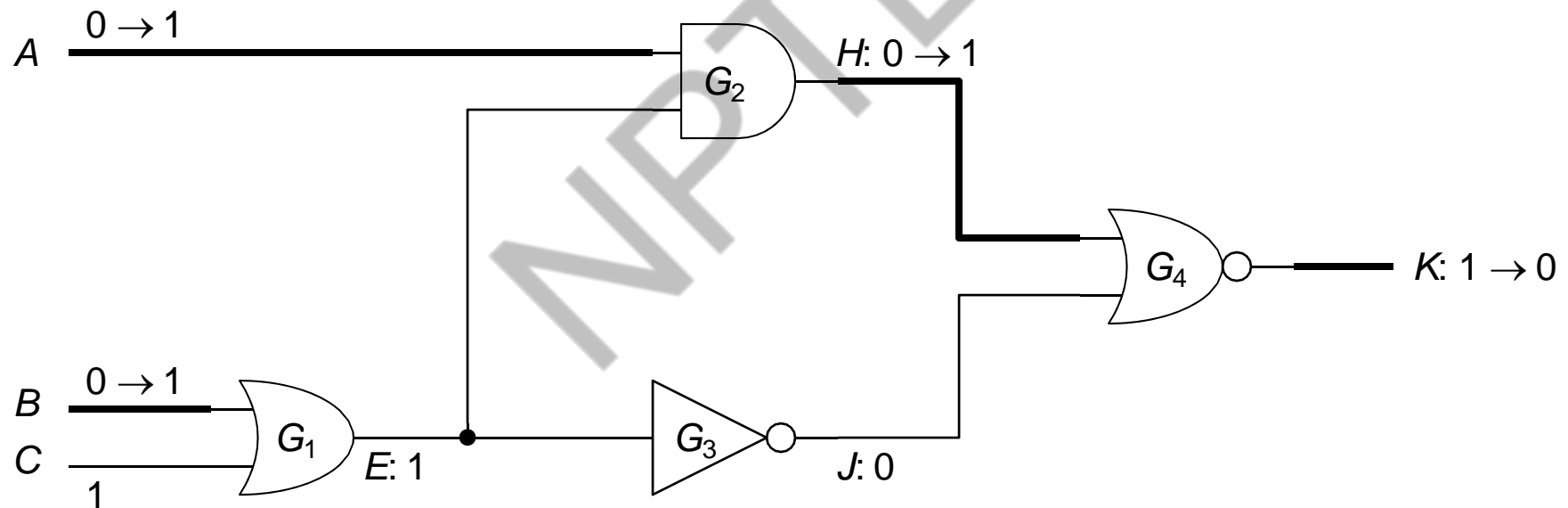
## Event-Driven Simulation

- Event: the switching of a signal's value
- An event-driven simulator monitors the occurrences of events to determine which gates to evaluate



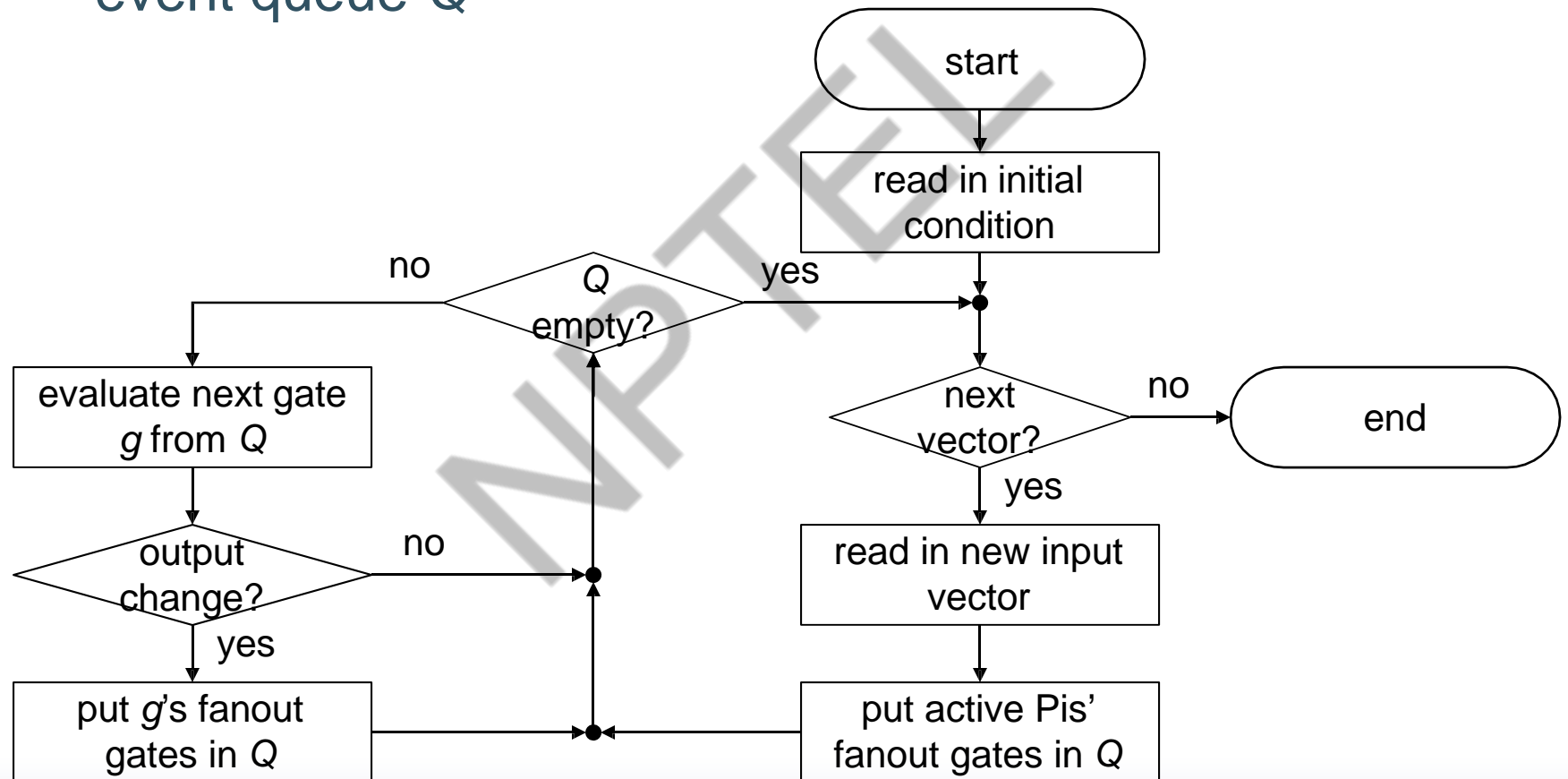
# Zero-Delay Event-Driven Simulation

- Gates with events at their inputs are places in the event queue  $Q$



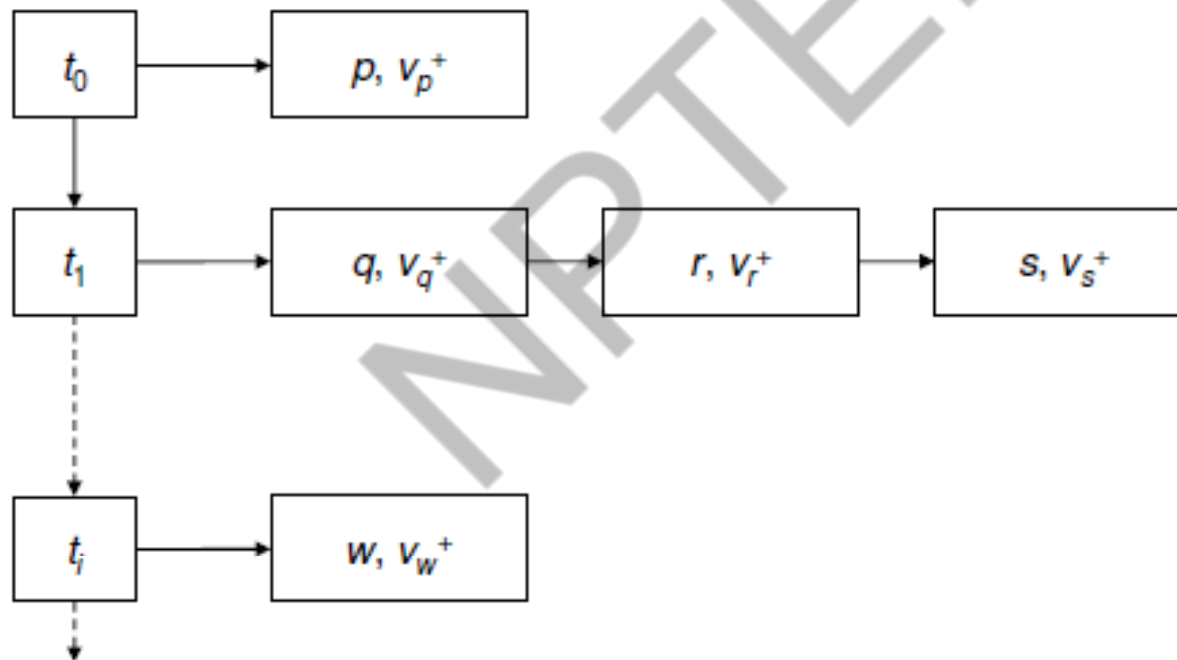
# *Nominal-Delay Event-Driven Simulation*


- Need a smarter scheduler than the event queue
  - Not only which gates but also when to evaluate



# Two-Pass Event-Driven Simulation

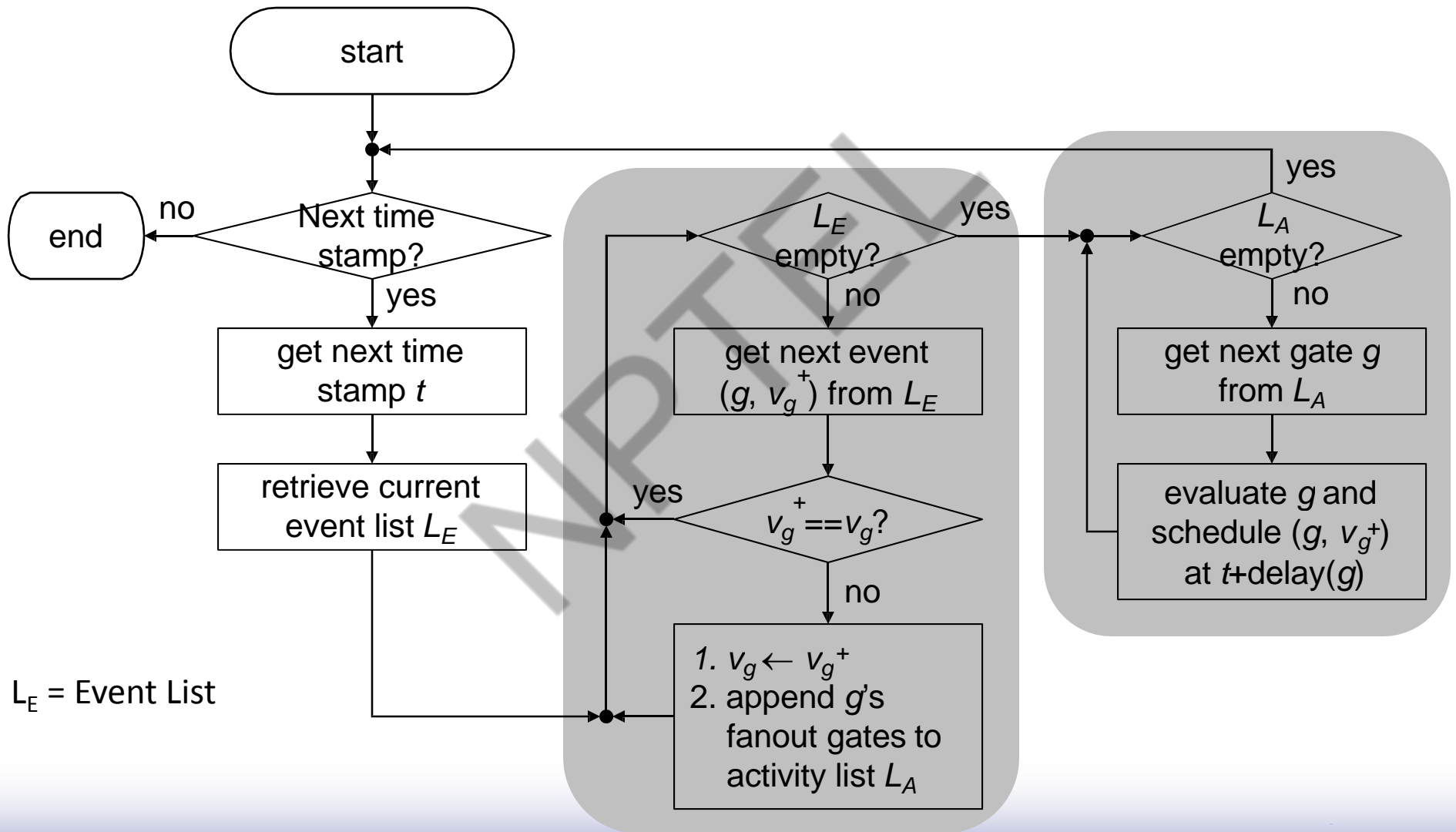

# Example

 


Nominal delays  
of  $G_1, G_2, G_3, G_4$   
are 8, 8, 4, 6 ns

Table 3.5: Two-pass event-driven simulation

Time	$L_E$	$L_A$	Scheduled events
0	$\{(A,1)\}$	$\{G_2\}$	$\{(H,1,8)\}$
2	$\{(C,0)\}$	$\{G_1\}$	$\{(E,1,10)\}$
4	$\{(B,0)\}$	$\{G_1\}$	$\{(E,0,12)\}$
8	$\{(A,0),(H,1)\}$	$\{G_2, G_4\}$	$\{(H,0,16),(K,0,14)\}$
10	$\{(E,1)\}$		
12	$\{(E,0)\}$	$\{G_2, G_3\}$	$\{(H,0,20),(J,1,16)\}$
14	$\{(K,0)\}$		
16	$\{(H,0),(J,1)\}$	$\{G_4\}$	$\{(K,0,22)\}$
20	$\{(H,0)\}$		
22	$\{(K,0)\}$		



## *Example - cont'd*

 

# *Compiled-Code vs. Event-Driven Simulation*

## ▮ Compiled-code



- Cycle-based simulation
- High switching activity circuits
- Parallel simulation
- Limited by compilation times

## ▮ Event-driven

- Implementing gate delays and detecting hazards
- Low switching activity circuits
- More complicated memory management

# Hazards

- Unwanted transient pulses or glitches

 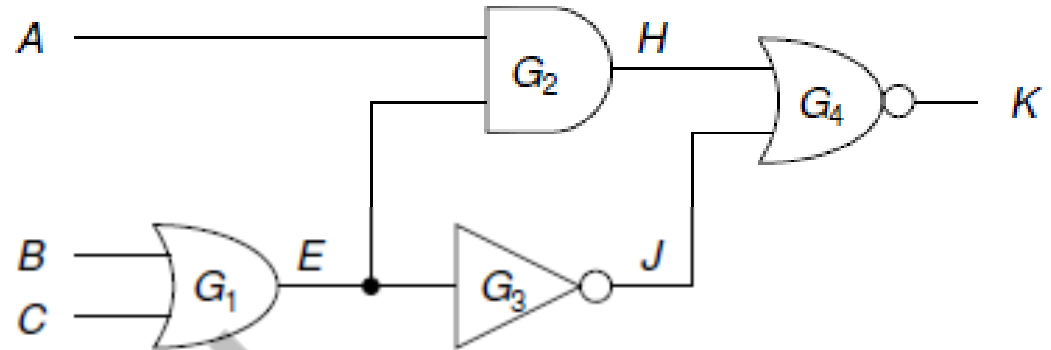


INV delay = 3ns  
Others = 2ns

# *Types of Hazards*

## D Static or dynamic

- A static hazard refers to the transient pulse on a signal line whose static value does not change
- A dynamic hazard refers to the transient pulse during a 0-to-1 or 1-to-0 transition


## D 1 or 0

 


Static 1-hazard



Static 0-hazard

 

Dynamic 1-hazard

 

Dynamic 0-hazard

## *Static Hazard Detection*

- ▮ Let  $V^1 = v_1^1 v_2^1 \cdots v_n^1$  and  $V^2 = v_1^2 v_2^2 \cdots v_n^2$  be two consecutive input vectors
- ▮ Add a new vector  $V^+ = v_1^+ v_2^+ \cdots v_n^+$  according to the following rule
$$v_i^+ = \begin{cases} v_i^1 & \text{if } v_i^1 = v_i^2 \\ u & \text{if } v_i^1 \neq v_i^2 \end{cases}$$
- ▮ Simulate the  $V^1 V^+ V^2$  sequence using ternary logic
- ▮ Any signal that is  $1u1$  or  $0u0$  indicates the possibility of a static hazard.

## *Multi-Valued Logic for Hazard Detection*

- ▯ 6-valued logic for static hazard detection
- ▯ 8-valued logic for dynamic hazard detection
- ▯ Worst case analysis

Table 3.6: Multi-valued logic for hazard detection

Symbol	Interpretation	6-valued logic	8-valued logic
0	Static 0	{000}	{0000}
1	Static 1	{111}	{1111}
R	Rise transition	{001,011}=0u1	{0001,0011,0111}
F	Fall transition	{100,110}=1u0	{1110,1100,1000}
0*	Static 0-hazard	{000,010}=0u0	{0000,0100,0010,0110}
1*	Static 1-hazard	{111,101}=1u1	{1111,1011,1101,1001}
R*	Dynamic 1-hazard		{0001,0011,0101,0111}
F*	Dynamic 0-hazard		{1000,1010,1100,1110}

# *Logic and Fault Simulation*

- D Introduction
- D Simulation models
- D Logic simulation
- D **Fault simulation**
- D Concluding remarks

# *Logic and Fault Simulation (contd.)*

## *Lecture 14*

NPTEL



# *Fault Simulation*

- D Introduction
- D Serial Fault Simulation
- D Parallel Fault Simulation
- D Deductive Fault Simulation
- D Concurrent Fault Simulation
- D Differential Fault Simulation
- D Fault Detection
- D Comparison of Fault Simulation Techniques
- D Alternative to Fault Simulation
- D Conclusion

# *Introduction*

## □ What is fault simulation?

- Given
  - A circuit
  - A set of test patterns
  - A fault model
- Determine
  - Faulty outputs
  - Undetected faults
  - Fault coverage

# *Time Complexity*

## □ Proportional to


- $n$ : Circuit size, number of logic gates
- $p$ : Number of test patterns
- $f$ : Number of modeled faults

□ Since  $f$  is roughly proportional to  $n$ , the overall time complexity is  $O(pn^2)$

## *Serial Fault Simulation*


- ▷ First, perform fault-free logic simulation on the original circuit
  - Good (fault-free) response
- ▷ For each fault, perform fault injection and logic simulation
  - *Faulty* circuit response

## Algorithm Flow

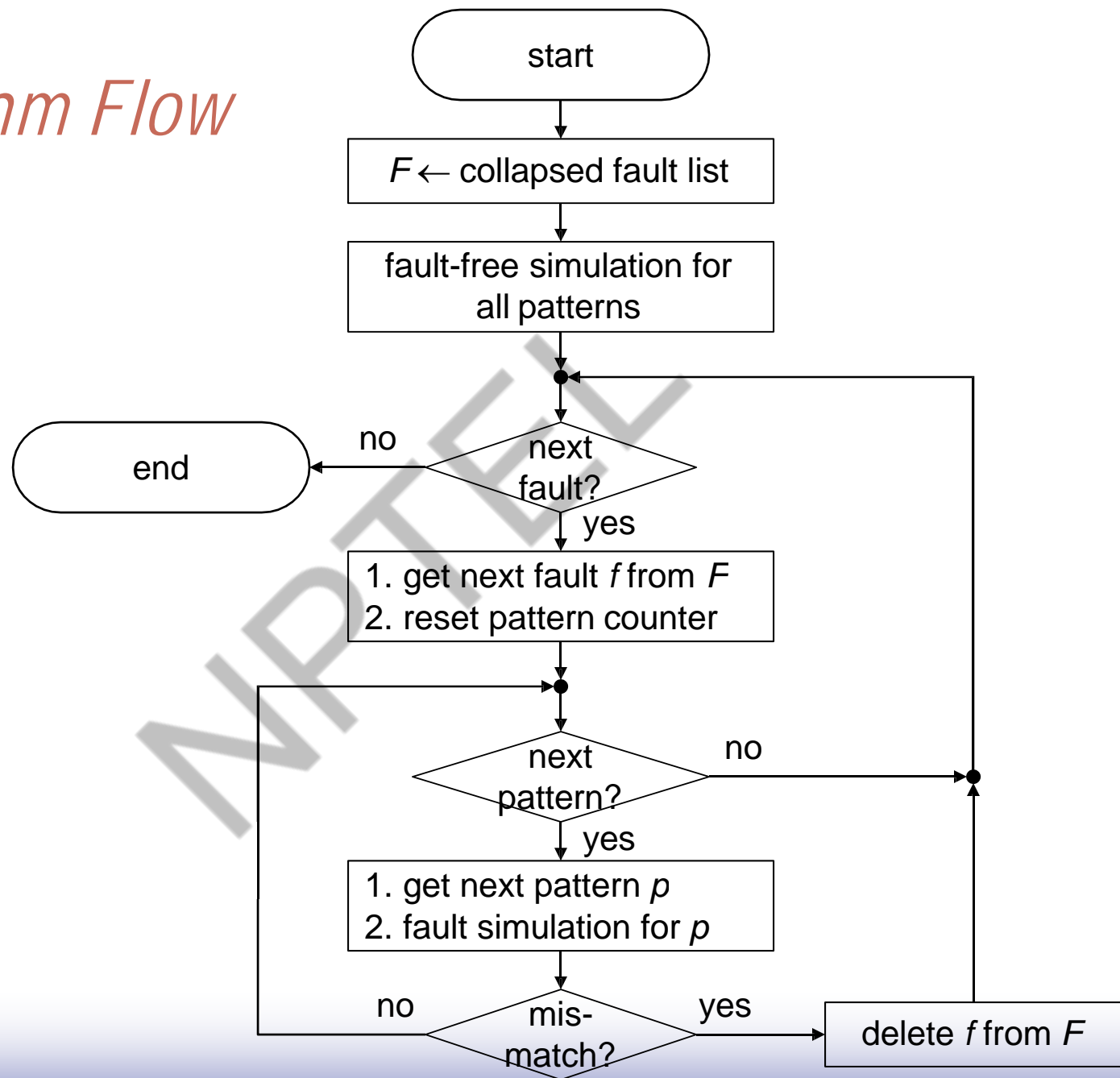

# Exempl

e

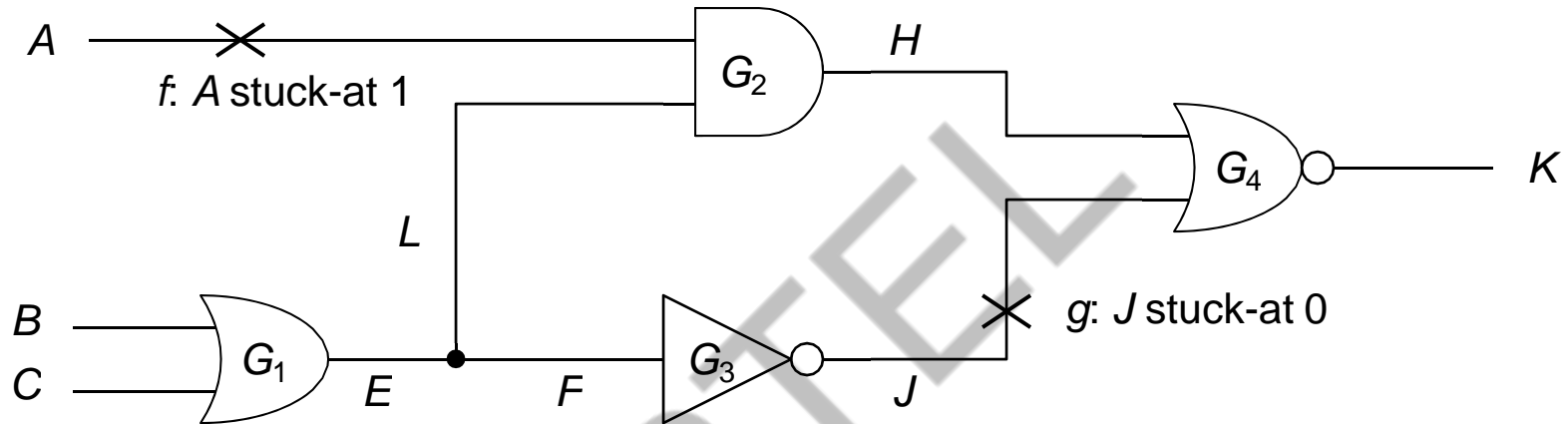

Pat. #	Input			Internal					Output		
	A	B	C	E	F	L	J	H	$K_{good}$	$K_f$	$K_g$
P1	0	1	0	1	1	1	0	0	1	0	1
P2	0	0	1	1	1	1	0	0	1	0	1
P3	1	0	0	0	0	0	1	0	0	0	1

## *Fault Dropping*

□ Halting simulation of the detected fault

□ Example

- Suppose we are to simulate  $P_1, P_2, P_3$  in order
- Fault  $f$  is detected by  $P_1$
- Do not simulate  $f$  for  $P_2, P_3$

□ For fault grading

- Most faults are detected after relatively few test patterns have been applied

□ For fault diagnosis

- Avoided to obtain the entire fault simulation results

# *Pro and Con*

## ▮ Advantages

- Easy to implement
- Ability to handle a wide range of fault models  
(stuck-at, delay, Br, ...)

## ▮ Disadvantages

- Very slow



## *Parallel Fault Simulation*

- ▷ Exploit the inherent parallelism of bitwise operations
- ▷ Parallel fault simulation
  - Parallel in faults
- ▷ Parallel pattern fault simulation
  - Parallel in patterns

# *Parallel Fault Simulation*

## D Assumption


- Use binary logic: one bit is enough to store logic signal
- Use  $w$ -bit wide data word

## D Parallel simulation

- $w-1$  bit for faulty circuits
- 1 bit for fault-free circuit

## D Process faulty and fault-free circuit in parallel using bitwise logic operations

# Fault Injection

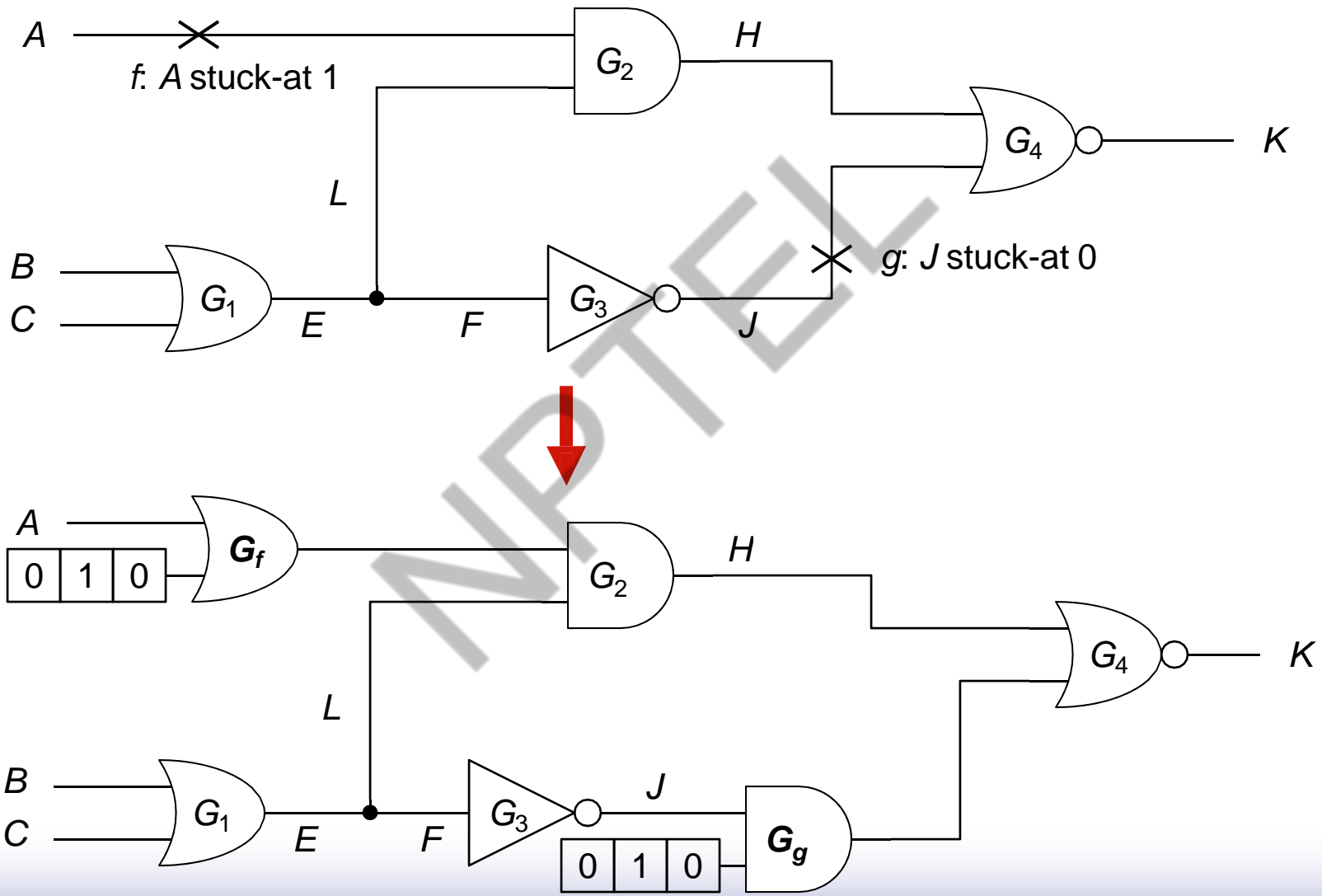

# Example

Pat #	Input					Internal						Output
		<i>A</i>	<i>A<sub>f</sub></i>	<i>B</i>	<i>C</i>	<i>E</i>	<i>F</i>	<i>L</i>	<i>J</i>	<i>J<sub>g</sub></i>	<i>H</i>	<i>K</i>
<i>P<sub>1</sub></i>	FF	0	0	1	0	1	1	1	0	0	0	1
	f	0	1	1	0	1	1	1	0	0	1	0
	g	0	0	1	0	1	1	1	0	0	0	1
<i>P<sub>2</sub></i>	FF	0	0	0	1	1	1	1	0	0	0	1
	f	0	1	0	1	1	1	1	0	0	1	0
	g	0	0	0	1	1	1	1	0	0	0	1
<i>P<sub>3</sub></i>	FF	1	1	0	0	0	0	0	1	1	0	0
	f	1	1	0	0	0	0	0	1	1	0	0
	g	1	1	0	0	0	0	0	1	0	0	1

## *Pro and Con*

### ▮ Advantages

- A large number of faults are detected by each pattern when simulating the beginning of test sequence


### ▮ Disadvantages

- Only applicable to the unit or zero delay models
- Faults cannot be dropped unless all  $(w-1)$  faults are detected

## *Parallel Pattern Fault Simulation*

- ▷ Parallel pattern single fault propagation (PPSFP)
- ▷ Parallel pattern
  - With a  $w$ -bit data width,  $w$  test patterns are packed into a word and simulated for the fault-free or faulty circuit
- ▷ Single fault
  - First, fault-free simulation
  - Next, for each fault, fault injection and faulty circuit simulation

# Algorithm Flow

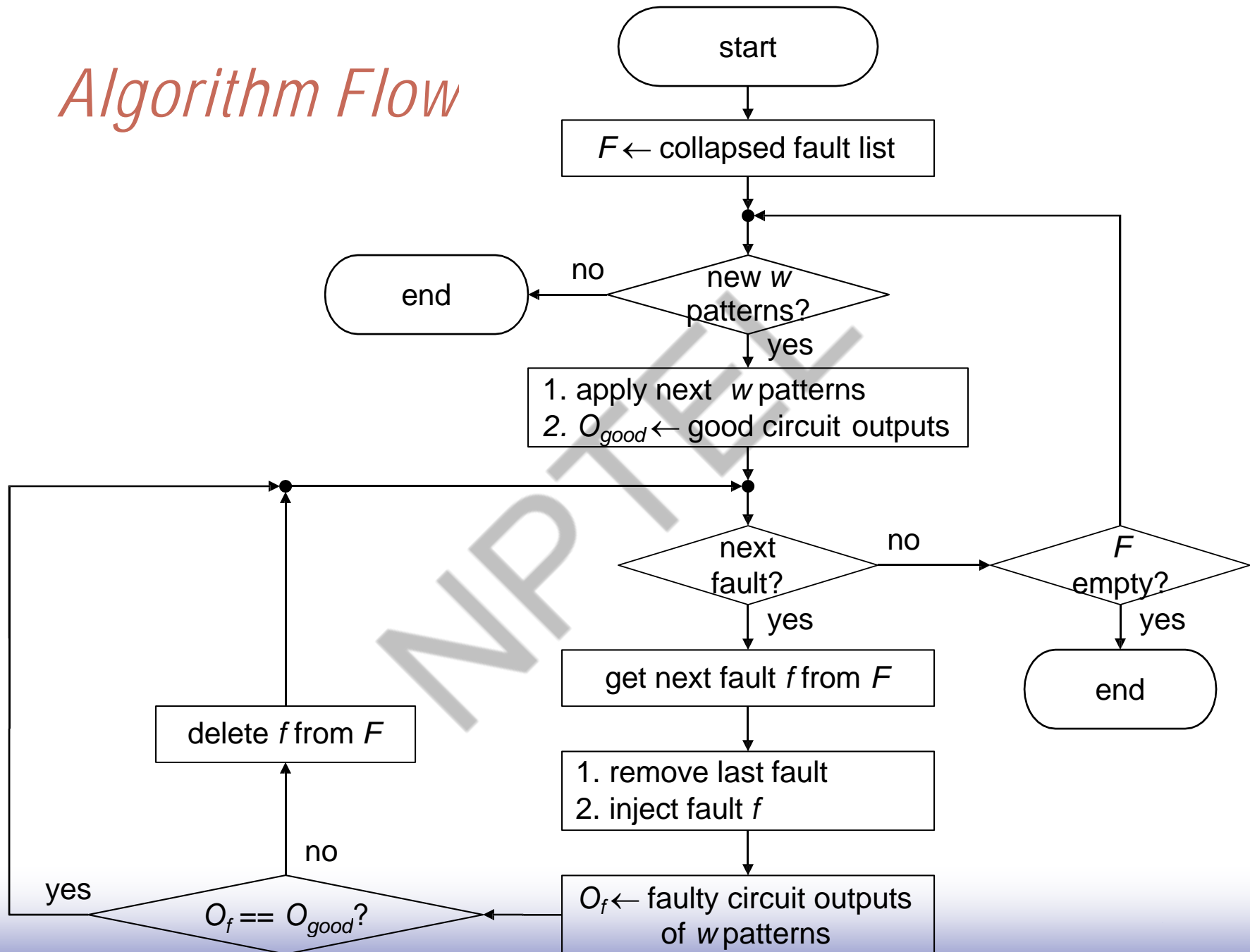


# *Logic and Fault Simulation (contd.)*

## *Lecture 15*

NPTEL



# Example

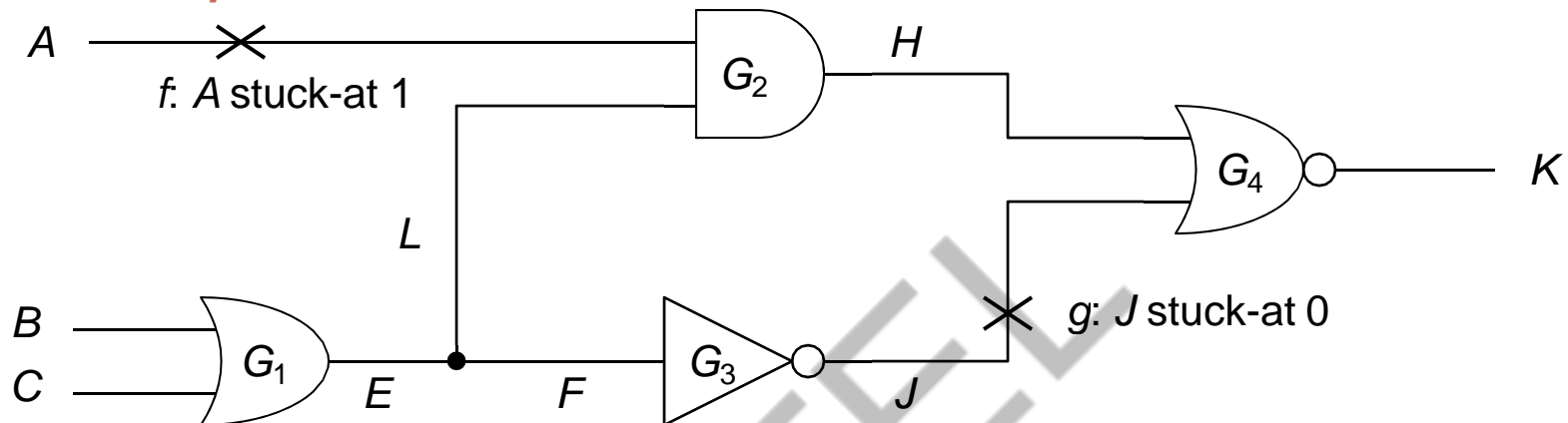

		Input			Internal					Output
		A	B	C	E	F	L	J	H	K
Fault Free	P <sub>1</sub>	0	1	0	1	1	1	0	0	1
	P <sub>2</sub>	0	0	1	1	1	1	0	0	1
	P <sub>3</sub>	1	0	0	0	0	0	1	0	0
f	P <sub>1</sub>	1	1	0	1	1	1	0	1	0
	P <sub>2</sub>	1	0	1	1	1	1	0	1	0
	P <sub>3</sub>	1	0	0	0	0	0	1	0	0
g	P <sub>1</sub>	0	1	0	1	1	1	0	0	1
	P <sub>2</sub>	0	0	1	1	1	1	0	0	1
	P <sub>3</sub>	1	0	0	0	0	0	0	0	1

## *Pro and Con*

### ▯ Advantages

- Fault is dropped as soon as detected
- Best for simulating test patterns that come later, where fault dropping rate per pattern is lower

### ▯ Disadvantages

- Not suitable for sequential circuits

## *Deductive Fault Simulation*

- ▷ Based on logic reasoning rather than simulation
- ▷ Fault list attached with signal  $x$  denoted as  $L_x$ 
  - Set of faults causing  $x$  to differ from its fault-free value
- ▷ Fault list propagation
  - Derive the fault list of a gate output from those of the gate inputs based on logic reasoning

# Fault List Propagation Rules

$c$  : controlling value

$i$  : inversion value

$I$  : set of gate inputs

$z$  : gate output

$S$  : inputs holding controlling value

	$c$	$i$
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

- All gate inputs hold non-controlling value


$$L_z = \left( \bigcup_{j \in I} L_j \right) \cup \{ z / (c \oplus i) \}$$

Z stuck-at c XOR i

- At least one input holds controlling value

$$L_z = \left[ \left( \bigcap_{j \in S} L_j \right) - \left( \bigcup_{j \in I-S} L_j \right) \right] \cup \{ z / c \oplus i' \}$$


## Algorithm Flow

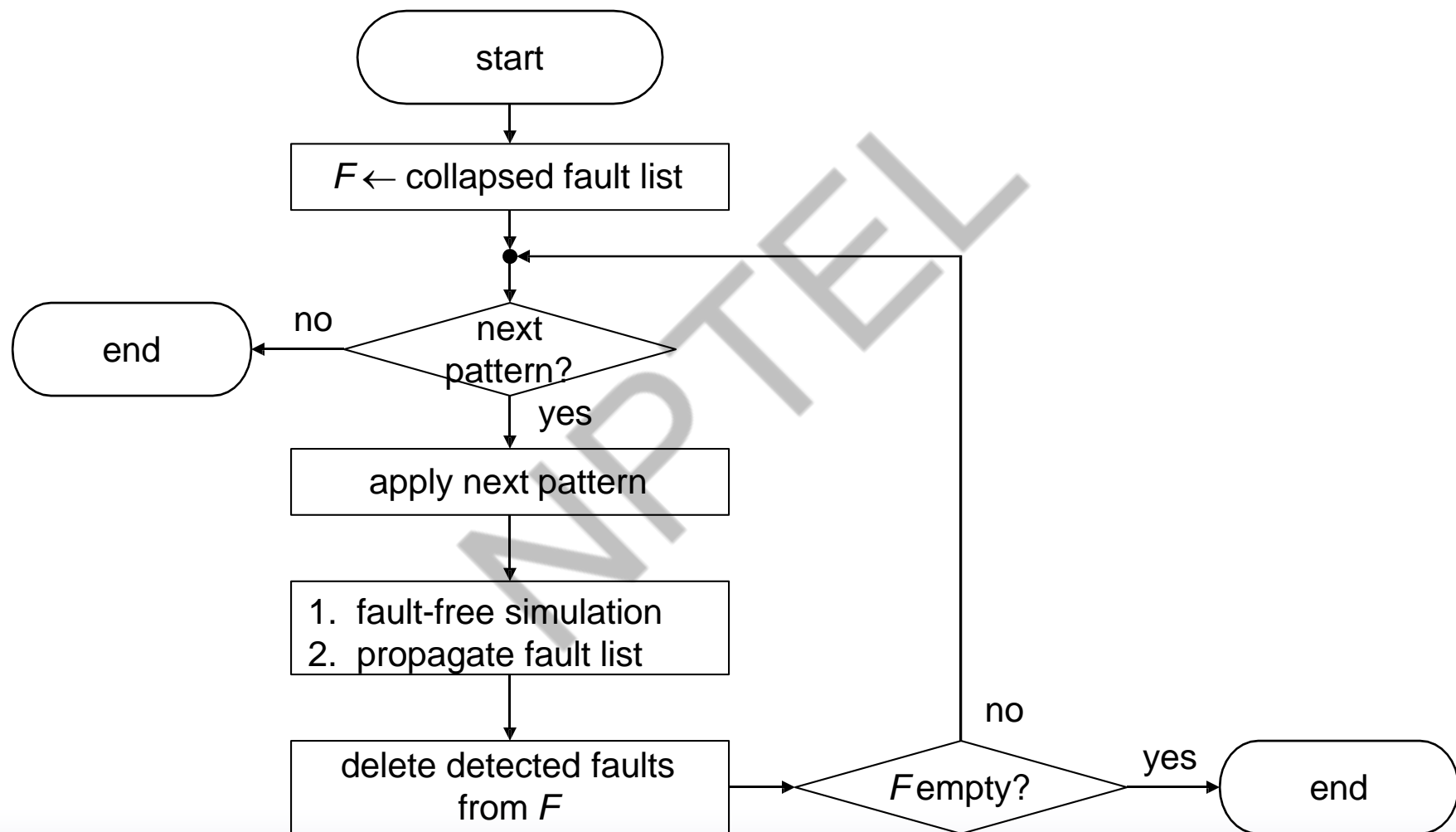
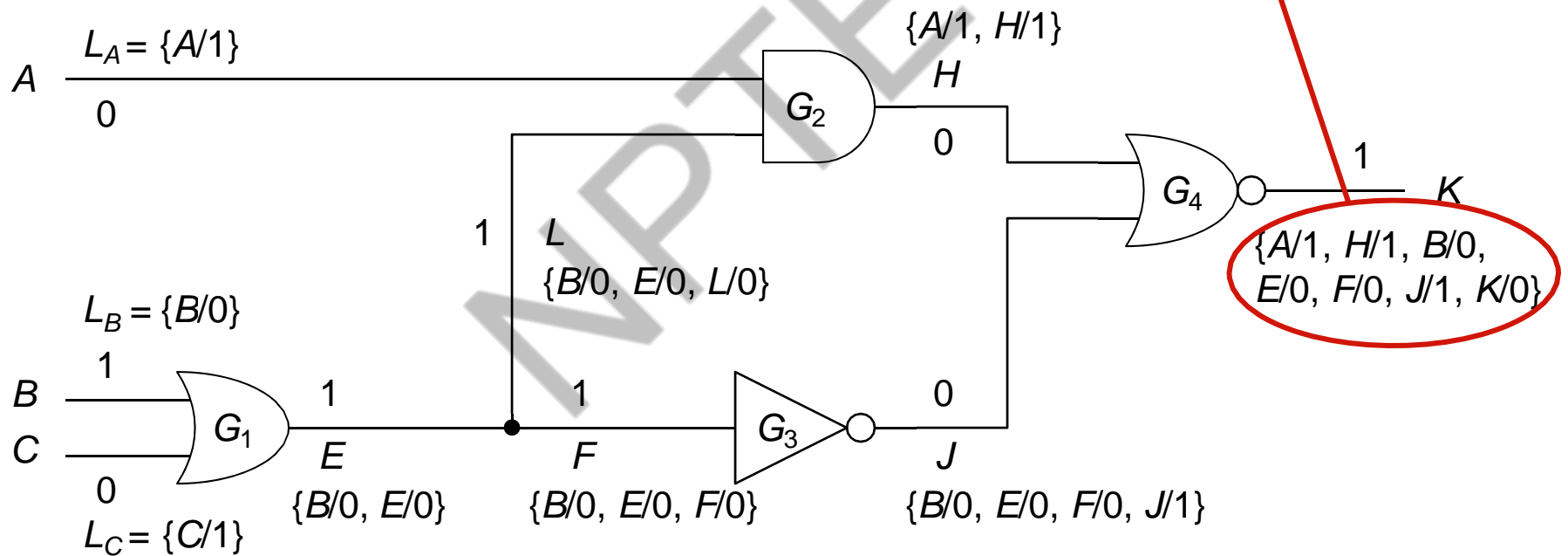
# Example


D  $P_1$

$$L_K = L_H \cup L_J \cup \{K/0\} \quad \text{by first Eq.}$$



## Example (cont'd)


D  $P_2$

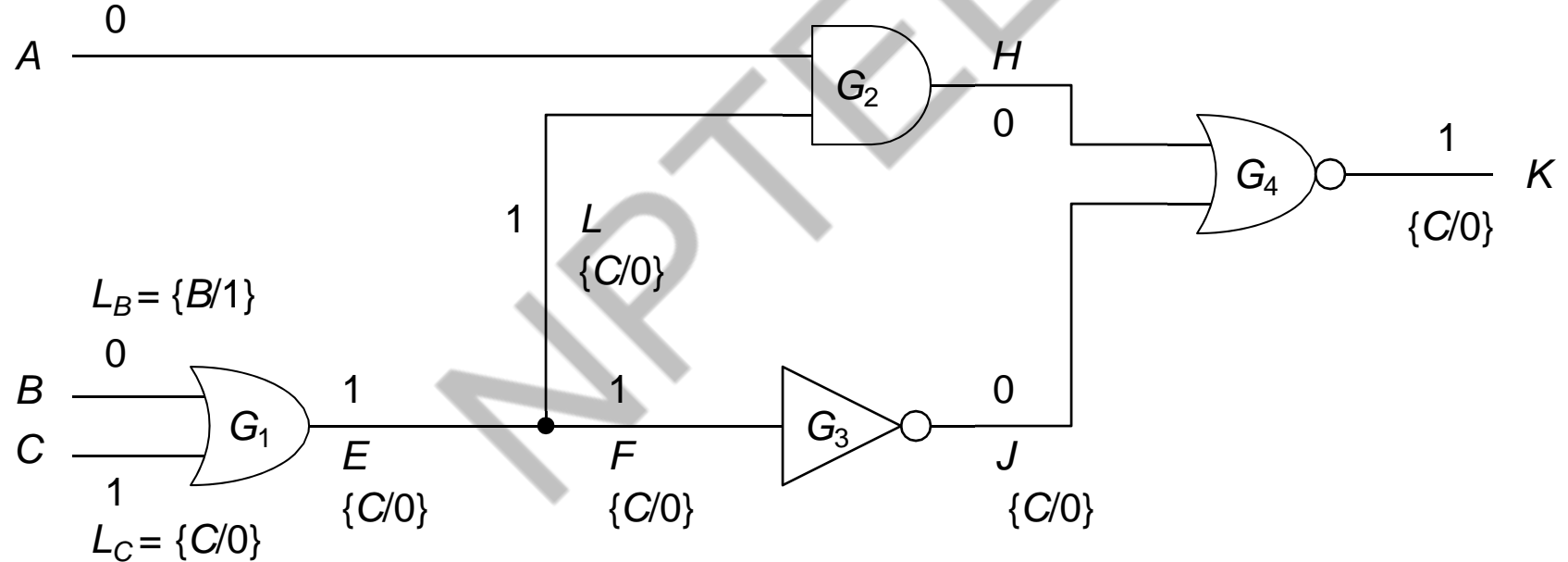
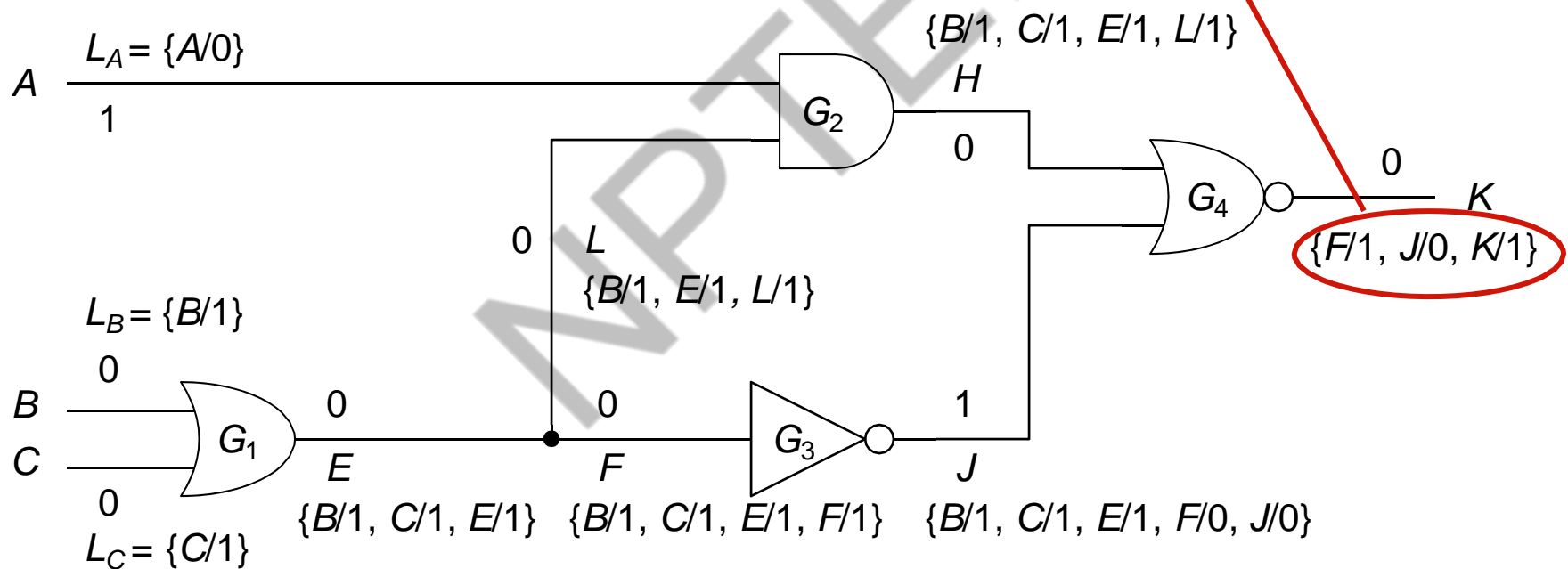
## Example (cont'd)

D  $P_3$

$$L_K = (L_J - L_H) \cup \{K/1\} \text{ by second Eq.}$$





# *Pro and Con*

## ▮ Advantages

- Very efficient
- Simulate all faults in one pass

## ▮ Disadvantages

- Not easy to handle unknowns
- Only for zero-delay timing model
- Potential memory management problem

## *Concurrent Fault Simulation*

- ▷ Simulate only differential parts of whole circuit
- ▷ Event-driven simulation with fault-free and faulty circuits simulated altogether
- ▷ Concurrent fault list for each gate
  - Consist of a set of bad gates
    - Fault index & associated gate I/O values
  - Initially only contains local faults
  - Fault propagate from previous stage

## *Good Event and Bad Event*

### D Good event

- Events that happen in good circuit
- Affect both good gates and bad gates

### D Bad event

- Events that occur in the faulty circuit of corresponding fault
- Affect only bad gates


### D Diverge

- Addition of new bad gates

### D Converge


- Removal of bad gates whose I/O signals are the same as corresponding good gates

## Algorithm Flow

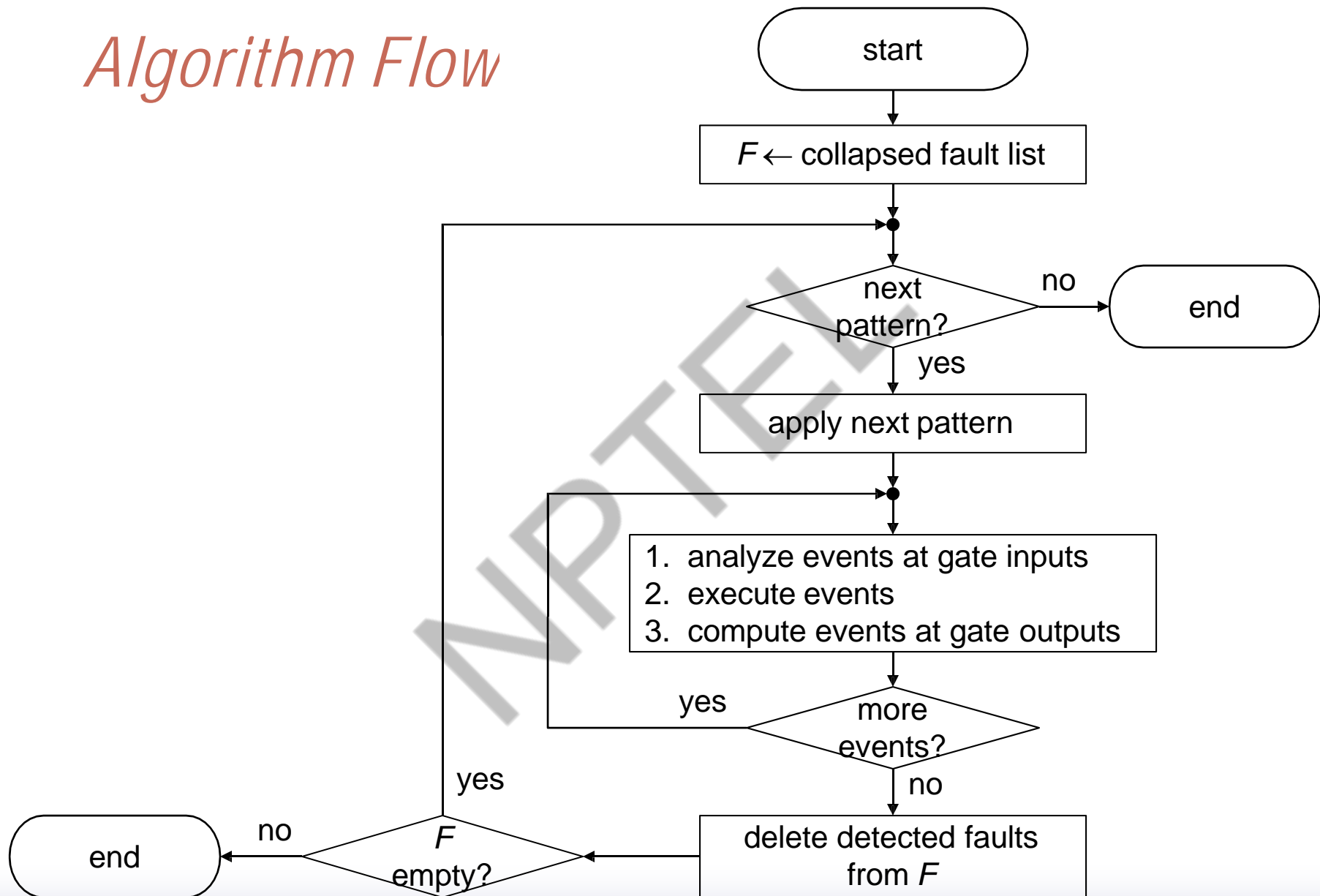


# Example

D  $P_1$

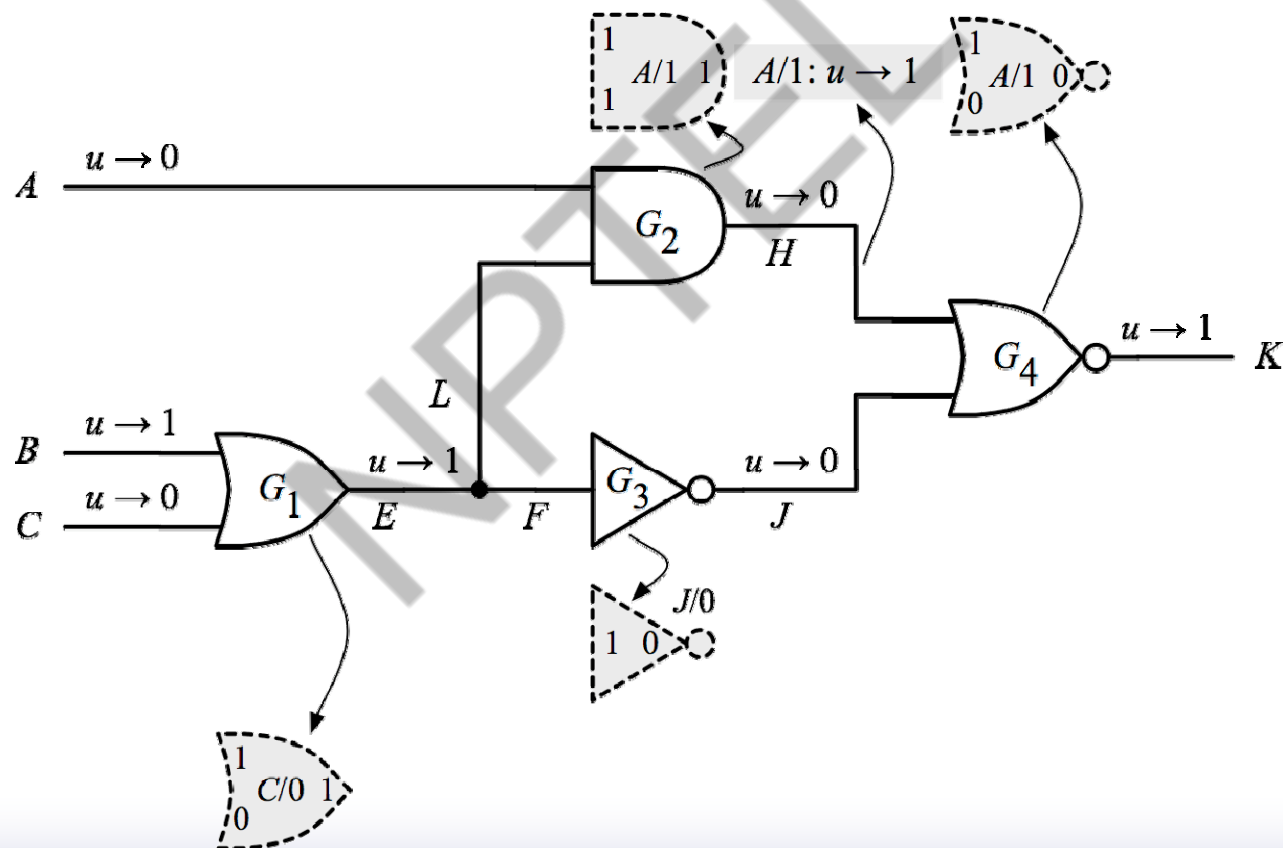


## Example (cont'd)

D  $P_2$

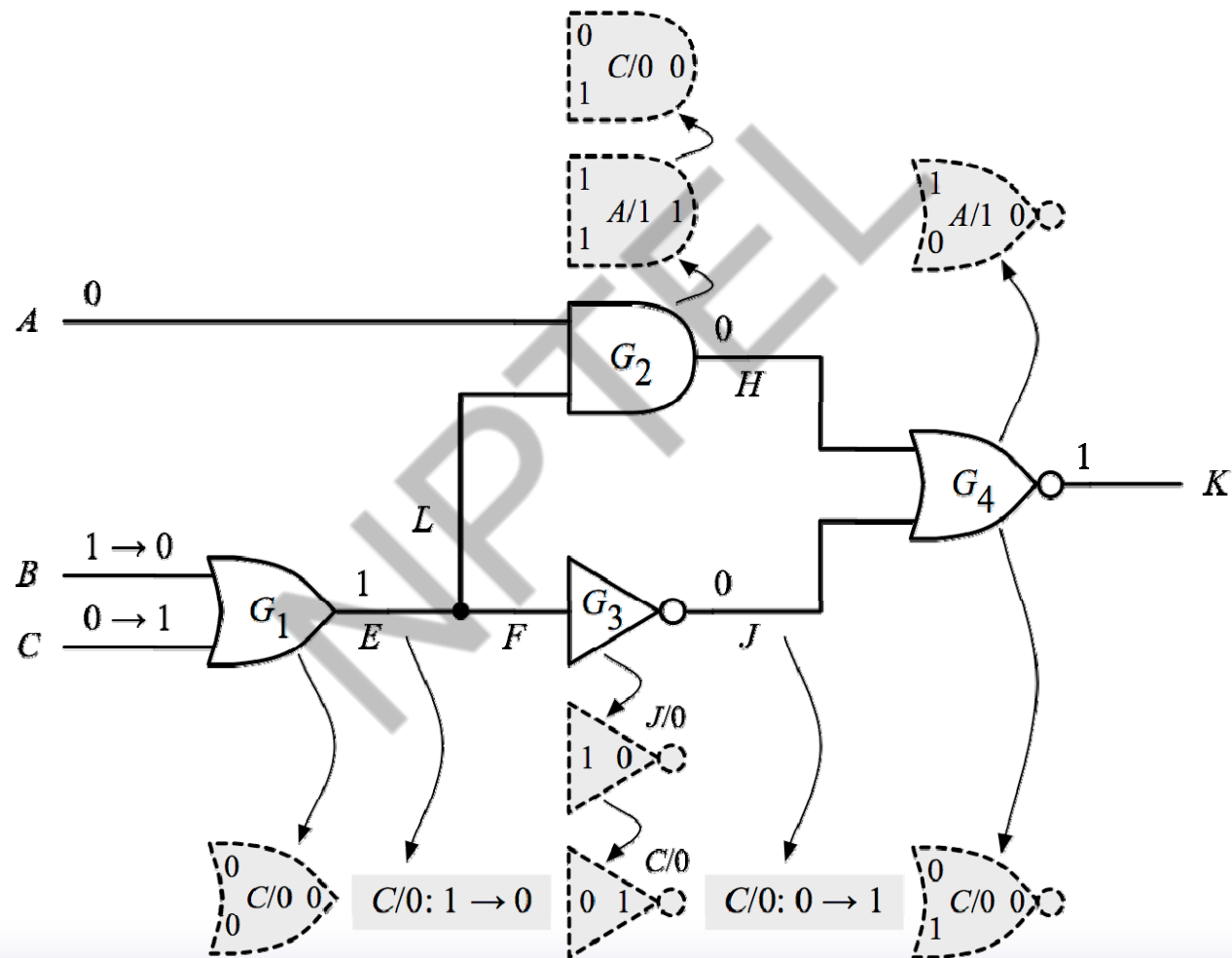

## Example (cont'd)

D  $P_3$

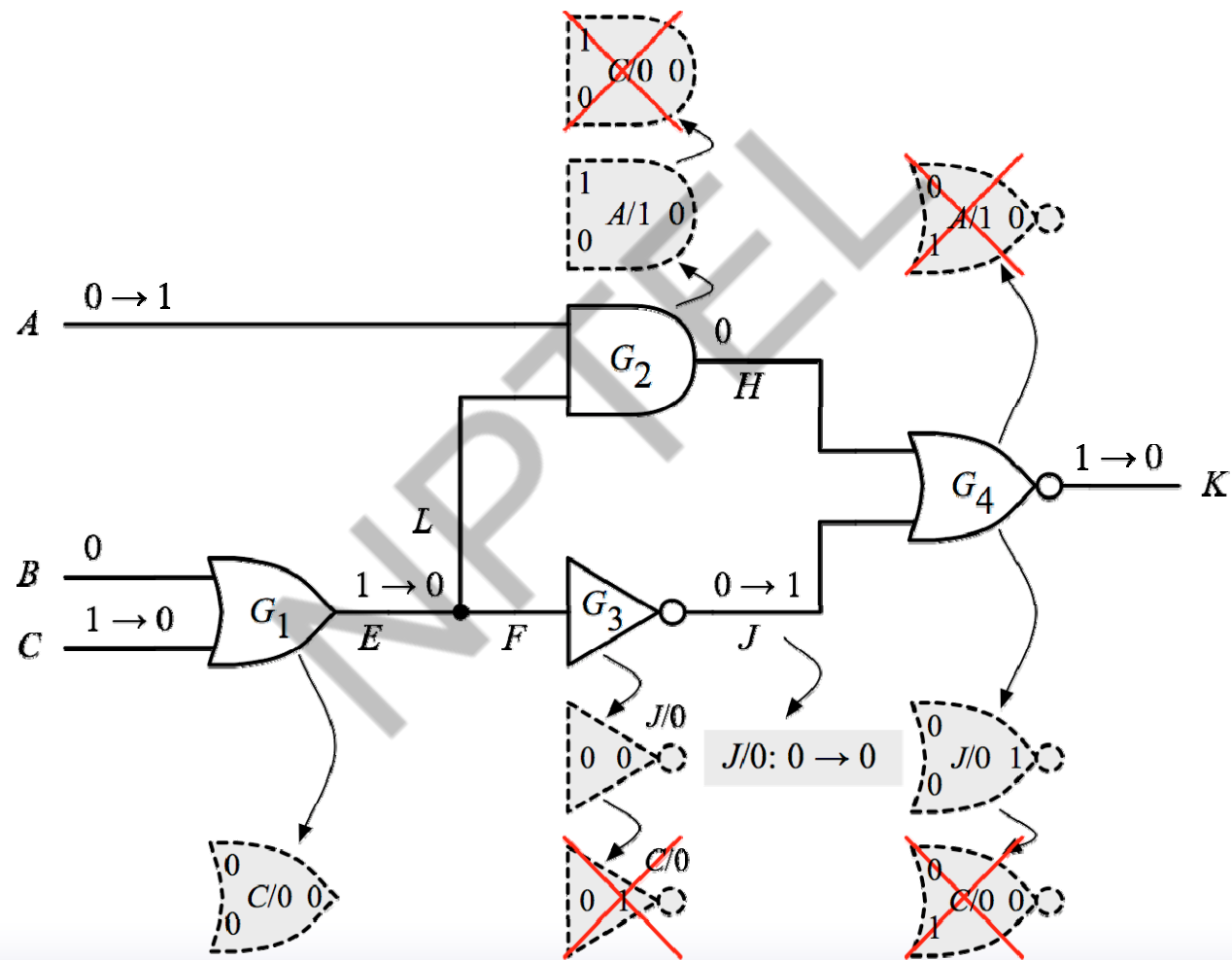

# *Pro and Con*

## ▮ Advantages

- Efficient

## ▮ Disadvantages

- Potential memory problem
  - Size of the concurrent fault list changes at run time




# *Differential Fault Simulation*

- ▷ [Cheng 1989]
- ▷ Combines the merits of two techniques
  - Concurrent fault simulation
  - PPSFP
- ▷ Idea
  - Simulate in turn every fault circuit
  - Track only difference between faulty circuit and last simulated one
  - Inject differences as events
  - Easily implemented by event-driven simulator

# Simulation Sequence

	$P_1$	$P_2$	...	$P_i$	$P_{i+1}$	...	$P_n$
<i>Good</i>	$G_1$	$G_2$	...	$G_i$	$G_{i+1}$	...	$G_n$
$f_1$	$F_{1,1}$	$F_{1,2}$	...	$F_{1,i}$	$F_{1,i+1}$	...	$F_{1,n}$
$f_2$	$F_{2,1}$	$F_{2,2}$	...	$F_{2,i}$	$F_{2,i+1}$	...	$F_{2,n}$
.	.	.	...	.	.	...	.
$f_k$	$F_{k,1}$	$F_{k,2}$	...	$F_{k,i}$	$F_{k,i+1}$	...	$F_{k,n}$
$f_{k+1}$	$F_{k+1,1}$	$F_{k+1,2}$	...	$F_{k+1,i}$	$F_{k+1,i+1}$	...	$F_{k+1,n}$
.	.	.	...	.	.	...	.
$f_m$	$F_{m,1}$	$F_{m,2}$	...	$F_{m,i}$	$F_{m,i+1}$	...	$F_{m,n}$

## Algorithm Flow

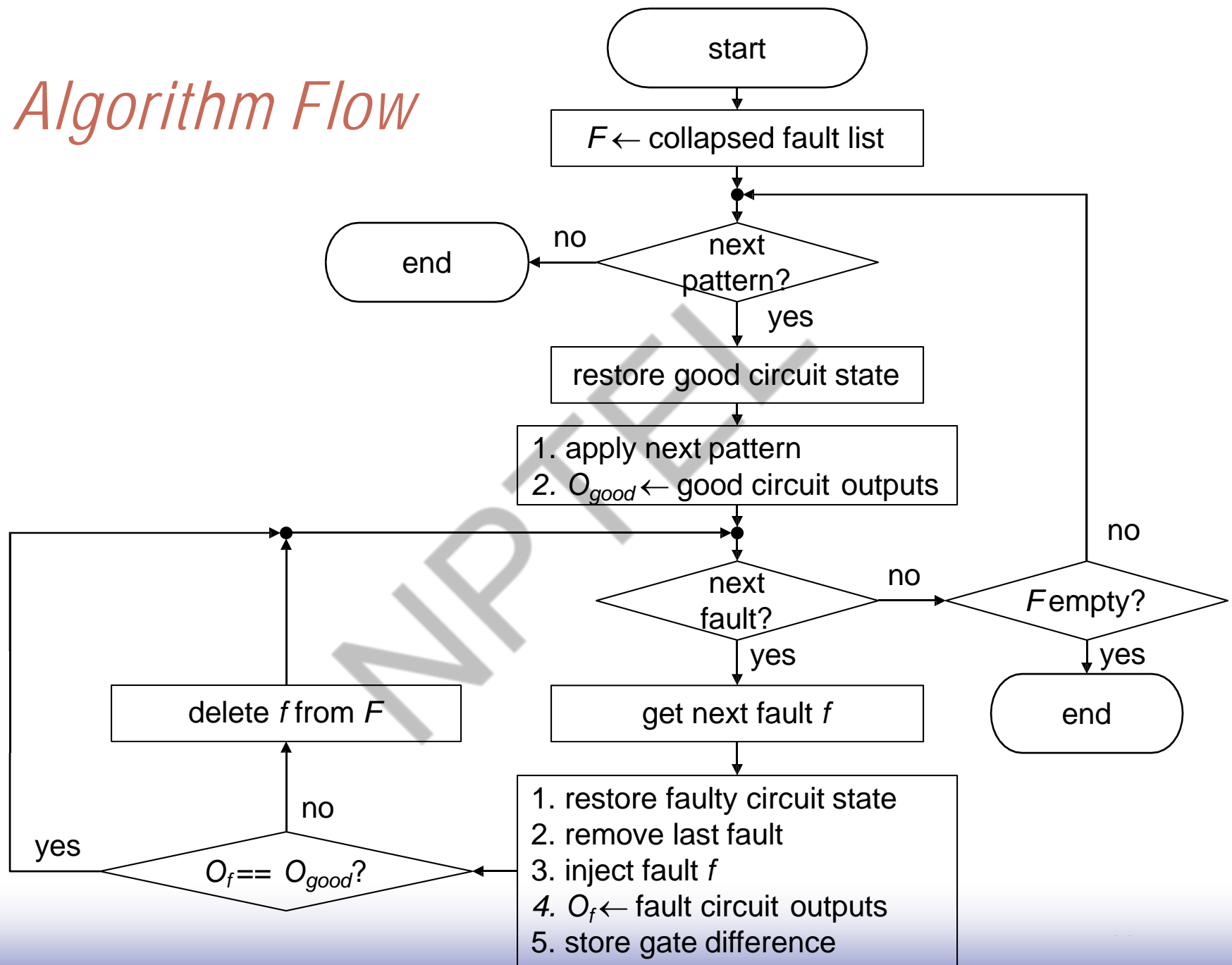

## *Pro and Con*

### ▮ Advantages

- Suitable for sequential fault simulation

### ▮ Disadvantages

- Order of events caused by faulty sites is NOT the same as the order of the timing of their occurrence

# *Logic and Fault Simulation (contd.)*

## *Lecture 16*

NPTEL

# *Fault Detection*

## □ Hard detected fault

- Outputs of fault-free and faulty circuit are different
  - 1/0 or 0/1
  - No unknowns, no Z

## □ Potentially detected fault

- Whether the fault is detected is unclear
- Example: stuck-at-0 on enable signal of tri-state buffer

## *Fault Detection (cont'd)*

### ▮ Oscillation faults

- Cause circuit to oscillate
- Impossible to predict faulty circuit outputs

### ▮ Hyperactive faults

- Catastrophic fault effect
  - Fault simulation is time and memory consuming
- Example: stuck-at fault on clock
- Usually counted as detected
  - Save fault simulation time

# *Comparison of Fault Simulation Techniques (1)*

## D Speed

- Serial fault simulation: slowest
- Parallel fault simulation:  $O(n^3)$ ,  $n$ : num of gates
- Deductive fault simulation:  $O(n^2)$
- Concurrent fault is faster than deductive fault simulation
- Differential fault simulation: even faster than concurrent fault simulation and PPSFP

## D Memory usage

- Serial fault simulation, parallel fault simulation: no problem
- Deductive fault simulation: dynamic allocate memory and hard to predict size
- Concurrent fault simulation: more severe than deductive fault simulation
- Differential fault simulation: less memory problem than concurrent fault simulation



## *Comparison of Fault Simulation Techniques (2)*

- ▮ Multi-valued fault simulation to handle unknown ( $X$ ) and/or high-impedance ( $Z$ )
  - Serial fault simulation, concurrent fault simulation, differential fault simulation: easy to handle
  - Parallel fault simulation: difficult
- ▮ Delay and functional modeling capability
  - Serial fault simulation: no problem
  - Parallel fault simulation, deductive fault simulation: not capable
  - Concurrent fault simulation: capable
  - Differential fault simulation: capable

## *Comparison of Fault Simulation Techniques (3)*

### D Sequential circuit

- Serial fault simulation, parallel fault simulation, concurrent fault simulation, differential fault simulation: no problem
- PPSFP: difficult
- Deductive fault simulation: difficult due to many unknowns

## *Comparison of Fault Simulation Techniques (4)*

- ▮ PPSFP and concurrent fault simulation are popular for combinational (full-scan) circuits
- ▮ Differential fault simulation and concurrent fault simulation is popular for sequential circuits
- ▮ Multiple-pass fault simulation
  - Prevent memory explosion problem
- ▮ Distributed fault simulation
  - Reduce fault simulation time

# *Summary*

- ▮ Fault simulation is very important for
  - ATPG
  - Diagnosis
  - Fault grading
- ▮ Popular techniques
  - Serial, Parallel, Deductive, Concurrent, Differential
- ▮ Requirements for fault simulation
  - Fast speed, efficient memory usage, modeling functional blocks, sequential circuits

# *Logic and Fault Simulation*

- D Introduction
- D Simulation models
- D Logic simulation
- D Fault simulation
- D **Concluding remarks**

## *Conclusions*

- ▮ Logic and fault simulations, two fundamental subjects in testing, are presented
- ▮ Into the nanometer age, advanced techniques are required to address new issues
  - High performance
  - High capacity
  - New fault models