

Digital Electronic Circuits

Live Session Week 1
NPTEL Online Certification Course

29 January 2022

Brief Summary of Lecture 1 and 2

Lecture 1 : Introduction

- Why 'Digital' ?
- Switching and logic operation
- Diode as a switch.

Lecture 2 : Transistor as a switch

- Transistor as an inverter
- Input-output characteristics
- Noise margin, transition width, logic swing
- Fan-out

Brief Summary of Lecture 3, 4 and 5

Lecture 3 : Performance Issues and Introduction to TTL

- Propagation delay and power dissipation
- RTL NOR and NAND gate
- DTL NAND gate
- TTL NAND gate

Lecture 4 : Transistor Transistor Logic (TTL)

- TTL Transfer Characteristics and operating parameters
- TTL Open Collector configuration and TTL Tristate
- Schottky TTL

Lecture 5 : CMOS Logic

- CMOS Logic gate and its characteristics, CMOS Tristate and Open-drain
- CMOS – TTL Interface

Q 1. Considering the propagation delay of transistors, which of the following statements are true?

- (1) Propagation delay occurs due to finite switching speed of transistor and circuit capacitor.
 - (2) Propagation delay is directly proportional to power dissipation.
 - (3) Propagation delay is associated with rise time and fall time.
 - (4) Propagation delay is quantified by averaging the time taken for high to low and low to high transitions.
-


- a. (1), (2), (3)
- b. (1), (2), (4)
- c. (2), (3), (4)
- d. (1), (3), (4)

Q 2. The role of level-shifter diodes in DTL is to:

- a. Increase V_{IH}
- b. Increase V_{IL}
- c. Decrease V_{IL}
- d. Decrease V_{IH}

NPTTEL

 Q 2. The role of level-shifter diodes in DTL is to:



Q 3. For a given logic family, consider $V_{OL} = 0.9V$ and $V_{OH} = 4.5V$. For a given circuit, $V_{IL} = 1.2V$ and $V_{IH} = 3.2V$. Find the noise margins (NM_L and NM_H). Is it functionally better than a circuit with $V_{IL} = 1.5V$ and $V_{IH} = 3V$? (Yes/No)

- a. 0.3, 1.3, Yes
- b. 1.3, 0.3, No
- c. 0.3, 1.3, No
- d. 1.3, 0.3, Yes

Q 3. For a given logic family, consider $V_{OL} = 0.9V$ and $V_{OH} = 4.5V$. For a given circuit, $V_{IL} = 1.2V$ and $V_{IH} = 3.2V$. Find the noise margins (NM_L and NM_H). Is it functionally better than a circuit with $V_{IL} = 1.5V$ and $V_{IH} = 3V$? (Yes/No)

For first circuit

$$NM_L = V_{IL} - V_{OL} = 1.2 - 0.9 = 0.3V$$

$$NM_H = V_{OH} - V_{IH} = 4.5 - 3.2 = 1.3V$$

For second circuit

$$NM_L = V_{IL} - V_{OL} = 1.5 - 0.9 = 0.6V$$


$$NM_H = V_{OH} - V_{IH} = 4.5 - 3 = 1.5V$$

Q 4. Which of the following statements are FALSE about CMOS logic?

- (1) CMOS has very high input resistance and hence draws very low current.
 - (2) CMOS has high fan-out as compared to TTL.
 - (3) CMOS is generally faster than TTL.
 - (4) CMOS has low packing density.
 - (5) CMOS exhibits low power consumption.
-


- a. (1), (3), (4)
- b. (1), (2), (3), (5)
- c. (1), (2), (5)
- d. (3), (4)

 Q 5. In the given circuit, $V_{CE(sat)} = 0.2V$, $\beta_F = 50$, $V_{BE(sat)} = 0.7V$, $V_{IH} = 2V$. Also consider the noise margin high $NM_H = 1V$. What is fanout without and with noise margin?



- a. 23, 8
- b. 33, 11
- c. 23, 9
- d. 33, 12

 Q 5. In the given circuit, $V_{CE(sat)} = 0.2V$, $\beta_F = 50$, $V_{BE(sat)} = 0.7V$, $V_{IH} = 2V$. Also consider the noise margin high $NM_H = 1V$. What is fanout without and with noise margin?




Without noise margin $V_{IH} = 2V$

$$I_{C(driver)} = (V_{CC} - V_{out})/R_C = (5 - 2)/1 = 3mA$$

$$I_{B(load)} = (V_{out} - V_{BE(sat)})/R_B = (2 - 0.7)/10 = 0.13mA$$

$$N = I_{C(driver)}/I_{B(load)} = 3/0.13 = 23.08 \approx 23$$

 Q 5. In the given circuit, $V_{CE(sat)} = 0.2V$, $\beta_F = 50$, $V_{BE(sat)} = 0.7V$, $V_{IH} = 2V$. Also consider the noise margin high $NM_H = 1V$. What is fanout without and with noise margin?



With noise margin $NM_H = 1V$


$$V_{OH} = V_{IH} + NM_H = 2 + 1 = 3V$$

$$I_{C(driver)} = (V_{CC} - V_{out})/R_C = (5 - 3)/1 = 2mA$$

$$I_{B(load)} = (V_{out} - V_{BE(sat)})/R_B = (3 - 0.7)/10 = 0.23mA$$


$$N = I_{C(driver)}/I_{B(load)} = 2/0.213 = 8.696 \approx 8$$

Q 6. Identify the following circuit?

 

- a. Tristate buffer
- b. Tristate inverter
- c. Open collector logic
- d. Totem pole logic

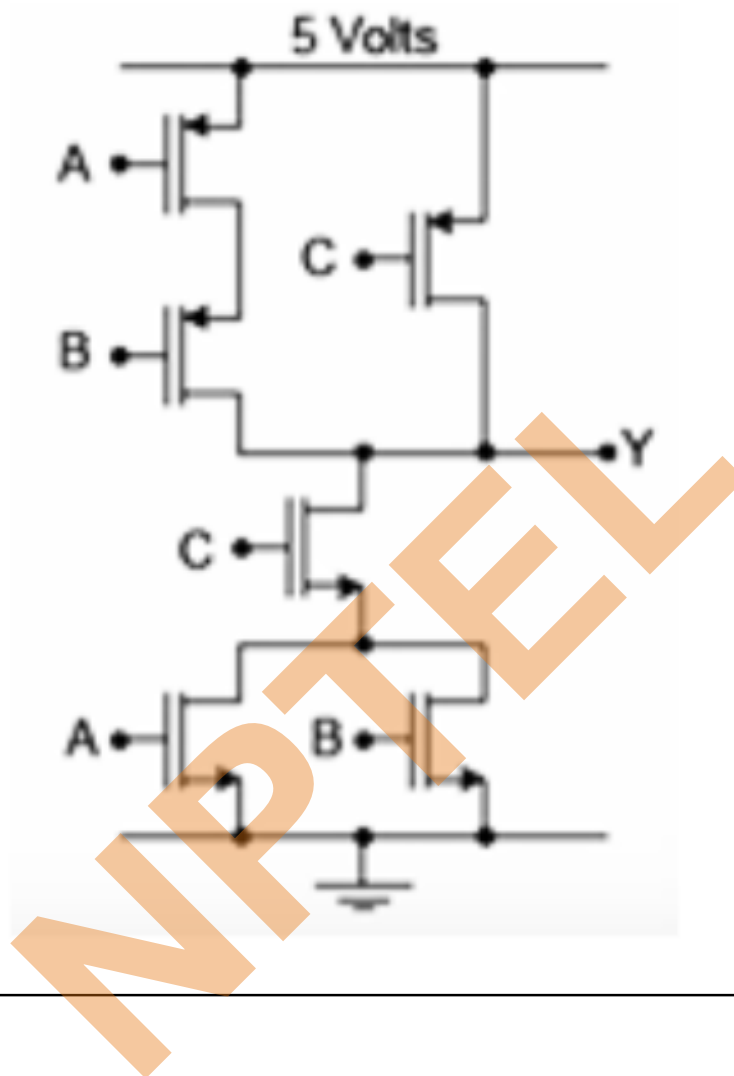Q 7. Find out the output expression of 'Y' from the circuit given below.




a. $Y = (A + B)C$

b. $Y = \bar{A} \bar{B} + \bar{C}$

c. $Y = AB + C$

d. $Y = (\bar{A} + \bar{B})\bar{C}$

 Q 7. Find out the output expression of 'Y' from the circuit given below.




DeMorgan's rule

$$\overline{E + F} = \overline{E} \overline{F},$$

$$\overline{EF} = \overline{E} + \overline{F}$$


$$\begin{aligned} Y &= \overline{(A + B)C} \\ &= \overline{(A + B)} + \overline{C} \\ &= \overline{A} \overline{B} + \overline{C} \end{aligned}$$

 Q 8. The given CMOS circuit implements the logic:



-
- a. $Y = \bar{A}B + A\bar{B}$
b. $Y = \bar{A} \bar{B} + AB$
c. $Y = \overline{AB}$
d. $Y = \overline{A + B}$

 Q 8. The given CMOS circuit implements the logic:



DeMorgan's rule:

$$\overline{E + F} = \overline{E} \overline{F}, \quad \overline{EF} = \overline{E} + \overline{F}$$

$$\begin{aligned} Y &= \overline{(A + \overline{B})(\overline{A} + B)} \\ &= \overline{(A + \overline{B})} + \overline{(\overline{A} + B)} \\ &= \overline{A} \overline{\overline{B}} + \overline{\overline{A}} \overline{B} = \overline{A} B + A \overline{B} \end{aligned}$$

Thank You

NPTEL