



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Computer aided power system analysis

AC- DC Load Flow (Contd.)

Prof. Biswarup Das

Department of Electrical Engineering



Case - i)

Specified quantities: d , P_{dr} , r , V_{di}

Steps

1. $P_{dr} = V_{dr} I_d = V_{dr} \frac{V_{dr} - V_{di}}{R_{dc}}$

$$\Rightarrow P_{dr} R_{dc} = V_{dr}^2 - V_{dr} V_{di}$$

$$\Rightarrow V_{dr}^2 - V_{dr} V_{di} - \underbrace{P_{dr}}_{\checkmark} \underbrace{R_{dc}}_{\checkmark} = 0$$

$\Rightarrow V_{dr}$ can be calculated.

2. Calculate $I_d = \frac{V_{dr} - V_{di}}{R_{dc}}$

To calculate
 Q_{dr} ✓
 P_{di} ✓
 Q_{di} ✓
6 other
quantities



$$3. \quad V_{dr} = \frac{V_{dr} + \frac{3}{\pi} X_{cr} N_r I_d}{\cos \alpha} \quad \left| \quad \text{as } V_{dr} = V_{dor} \cos \alpha - \frac{3}{\pi} X_{cr} N_r I_d \right.$$

$\Rightarrow V_{dor}$ is known (calculated)

$$4. \quad V_{dr} = V_{dor} \cos \phi_r \quad \Rightarrow \quad \cos \phi_r = \frac{V_{dr}}{V_{dor}} \rightarrow \text{known}$$

$$5. \quad Q_{dr} = P_{dr} \tan \phi_r \rightarrow \text{calculated.}$$

$$6. \quad V_{dor} = \frac{3\sqrt{2}}{\pi} N_r a_r E_{tr} \rightarrow a_r \text{ is calculated.}$$

$$7. \quad P_{di} = V_{di} I_d \rightarrow P_{di} \text{ is calculated}$$



$$8. \quad V_{di} = \frac{V_{di} + \frac{3}{\pi} X_{ci} N_i I_d}{\cos \gamma} \rightarrow V_{di} \text{ is calculated}$$

$$9. \quad \cos \phi_i = \frac{V_{di}}{V_{doi}} \rightarrow \cos \phi_i \text{ is calculated}$$

$$10. \quad Q_{di} = P_{di} \tan \phi_i \rightarrow Q_{di} \text{ is calculated.}$$

$$11. \quad V_{doi} = \frac{3\sqrt{2}}{\pi} N_i a_i E_{xi} \rightarrow a_i \text{ is calculated}$$

Therefore, P_{di} , Q_{di} , P_{di} , Q_{di} are known. Utilising these values, we carry out one iteration of AC load flow and therefore, updated values of E_{xi} and E_{xi} are obtained.



Case - ii) $\alpha, r, P_{di}, V_{dr}$ are specified.

Steps

i)

$$P_{di} = V_{di} I_d = V_{di} \frac{V_{dr} - V_{di}}{R_{dc}}$$

$$\Rightarrow R_{dc} P_{di} = V_{di} V_{dr} - V_{di}^2 \Rightarrow V_{di}^2 - V_{di} V_{dr} + R_{dc} P_{di} = 0$$

V_{di} is calculated

ii) $I_d = \frac{V_{dr} - V_{di}}{R_{dc}} \rightarrow I_d$ is calculated



Schematic (overall) algorithm for AC-DC load flow

- i) Assume flat start for the AC system.
- ii) Solve the DC equations to calculate P_{dr} , Q_{dr} , P_{di} , Q_{di}
- iii) Run one iteration of AC load flow
- iv) Go to step (ii) till convergence is achieved.



Example of AC-DC load flow in 5 bus system

- One bipolar HVDC link is connected between bus 4 and 5 (rectifier at bus 4 and inverter at bus 5)
- Base voltage of the AC system is 132 kV

$$R_d = 10.0 \, \Omega;$$

$$N_r = N_i = 2; \quad \frac{3}{\pi} X_{cr} = \frac{3}{\pi} X_{ci} = 6.0 \, \Omega.$$

Example of AC-DC load flow in 5 bus system

Combination-1

$$\alpha = 5^\circ, P_{dr} = 100 \text{ MW}; \gamma = 18^\circ, V_{di} = 250 \text{ kV}$$

$$V_{dr} = 253.938 \text{ kV}; i_d = 393.8 \text{ Amp.}; Q_{dr} = 16.276 \text{ MVAR};$$

$$P_{di} = 98.45 \text{ MW}; Q_{di} = 35.024$$

$$P_4 = -1.15 - 1.0 = -2.15 \text{ p.u.}, Q_4 = -0.6 - 0.16276 = -0.76276 \text{ p.u.},$$

$$P_5 = -0.85 + 0.9845 = 0.1345$$

$$Q_5 = -0.4 - 0.35024 = -0.75024 \text{ p.u.}$$

Example of AC-DC load flow in 5 bus system

Bus no.	Without generator Q limit			
	$ V $ (p.u)	θ (deg)	P_{inj} (p.u)	Q_{inj} (p.u)
1	1.0	0	0.68984	0.46301
2	1.0	-0.63995	0.5	-0.17235
3	1.0	-4.91128	1.0	1.54134
4	0.82813	-17.48682	-2.15	-0.76277
5	0.91332	-3.89028	0.13449	-0.75025
	Total iteration = 5			

$$a_r = 0.8714$$

$$a_i = 0.8149.$$